

# **Lecture 9: Clocking, Clock Skew, Clock Jitter, Clock Distribution and some FM**

**Mark McDermott**


**Electrical and Computer Engineering  
The University of Texas at Austin**

# Why Clocking?

---

- **Synchronous systems use a clock to keep operations in sequence**
  - Distinguish *this cycle* from *previous cycle* or *next cycle*
  - Determine speed at which machine operates
  
- **Clock must be distributed to all the sequencing elements**
  - Flip-flops and latches
  
- **Also distribute clock to other elements**
  - Domino circuits and memories
  
- **Clocking overhead % increases as the frequency is increased.**

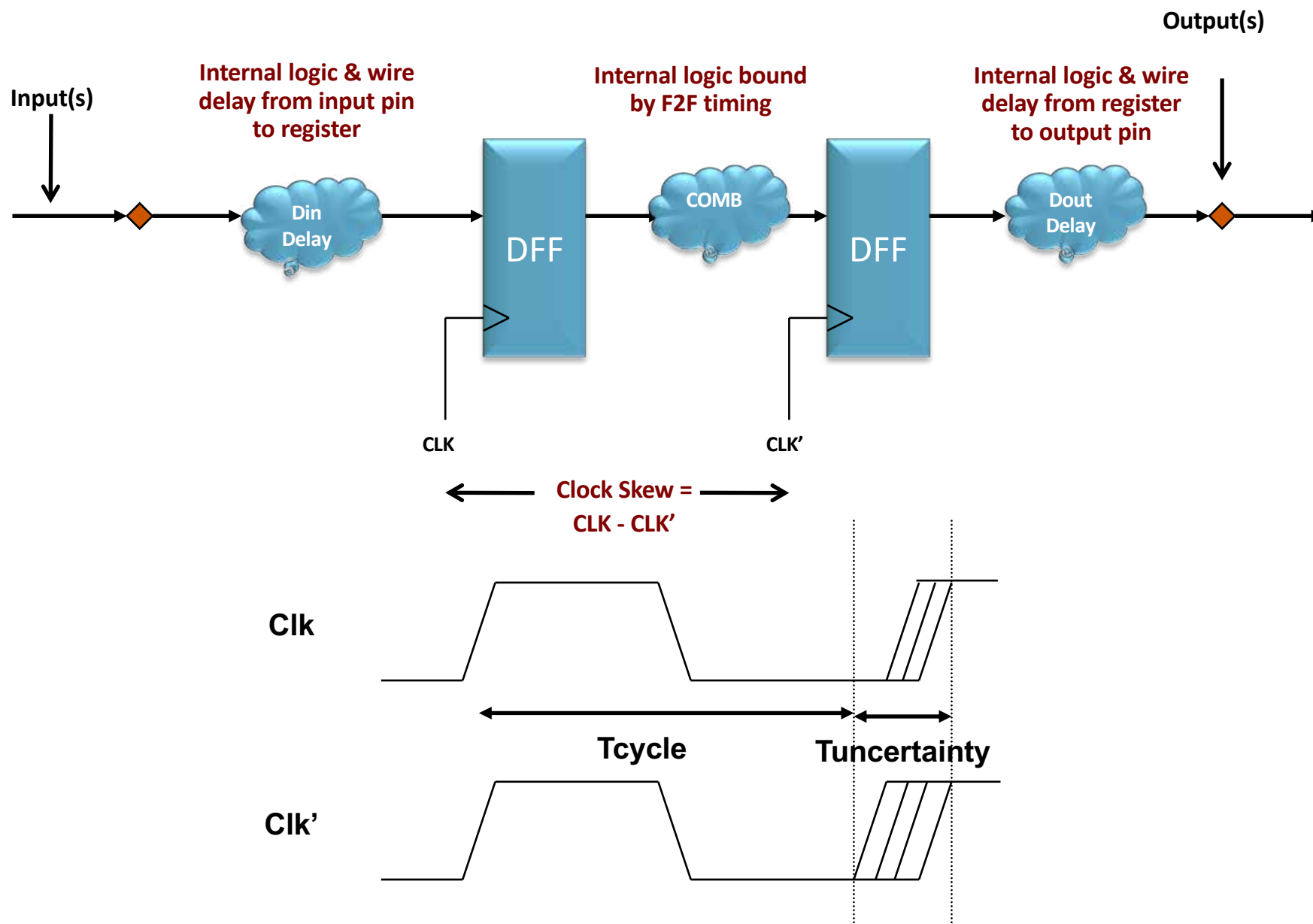
# Logic Transactions and Clock Dependence




# Clocking Overhead per Technology Generation

Clocking overhead ( skew and jitter ) is growing as we move to DSM processes. Careful design of the clock generation and distribution circuits is now required for all high performance processor designs.

Process Frequency Inv/Cycle

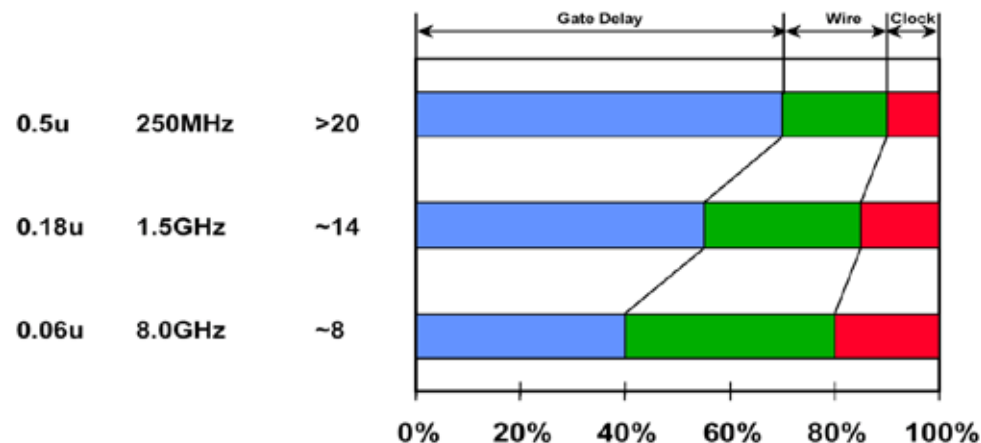

 Source: D. Luick, "Beyond Superscalar RISC", ISSCC'98




# Clock Distribution

---


- **On a small chip, the clock distribution network is just a wire**
  - And possibly an inverter for clk'
  
- **On practical chips, the RC delay of the wire resistance and gate load is very long**
  - Variations in this delay cause clock to get to different elements at different times
  - This is called **clock skew**
  
- **Most chips use repeaters to buffer the clock and equalize the delay**
  - Reduces but does not eliminate skew
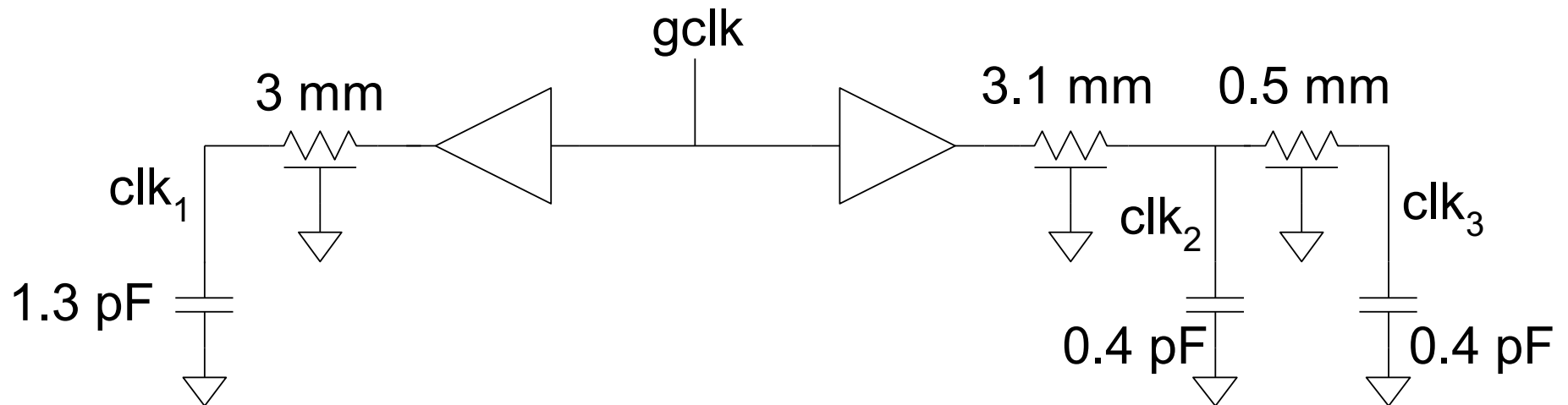
# Example

- **Skew comes from differences in gate and wire delay**
  - With right buffer sizing,  $\text{clk}_1$  and  $\text{clk}_2$  could ideally arrive at the same time.
  - But power supply noise changes buffer delays
  - $\text{clk}_2$  and  $\text{clk}_3$  will always see RC skew



# Sources of Clock Uncertainties

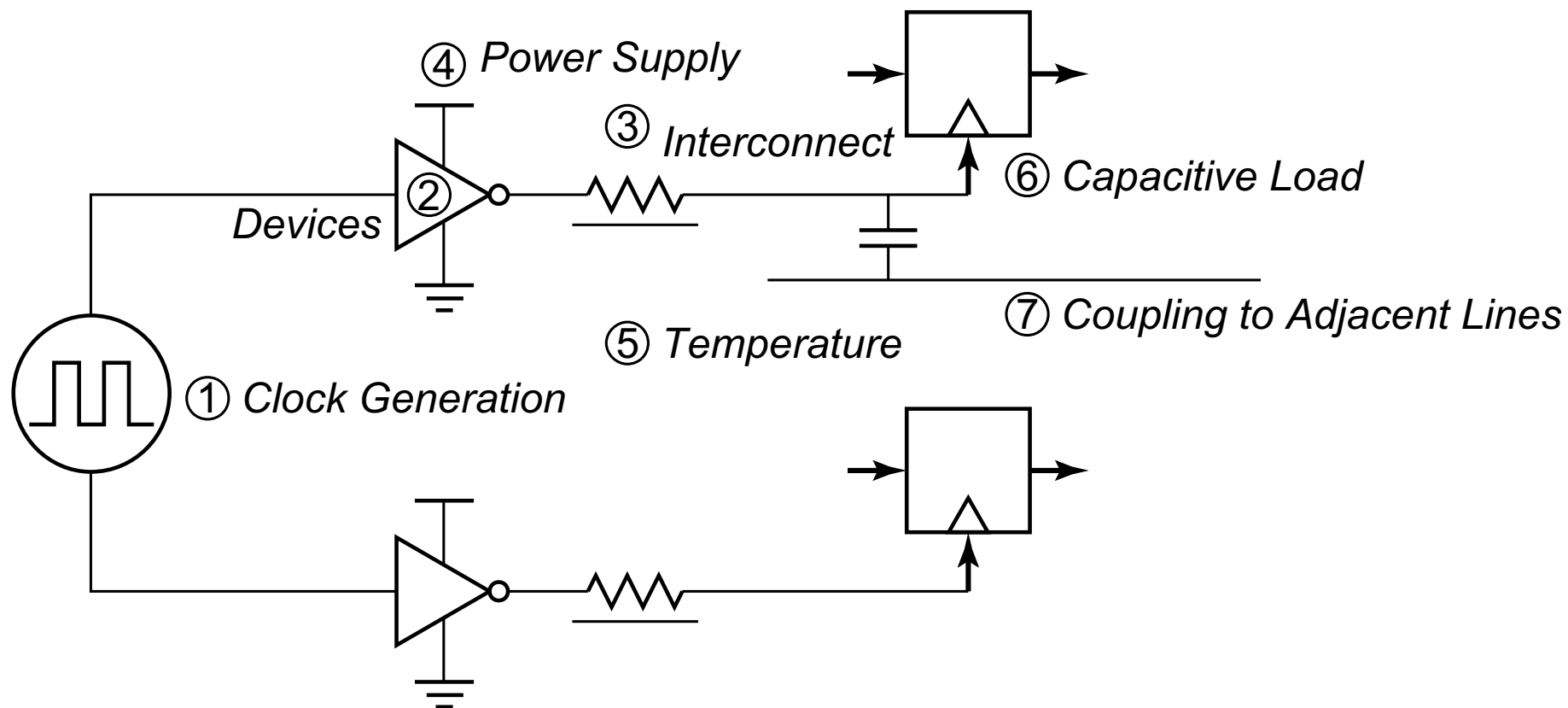

# Clock Non-idealities

---

## ■ Clock skew

- Spatial variation in temporally equivalent clock edges; deterministic + random,  $t_{SK}$

## ■ Clock jitter


- Temporal variations in consecutive edges of the clock signal; modulation + random noise
- Cycle-to-cycle (short-term)  $t_{JS}$
- Long term  $t_{JL}$

## ■ Variation of the pulse width

- Important for level sensitive clocking



# Clock Skew and Jitter

 


**Both skew and jitter affect the effective cycle time**

**Only skew affects the race margin assuming jitter tracks in the same direction**

© J. Rabaey, 2002
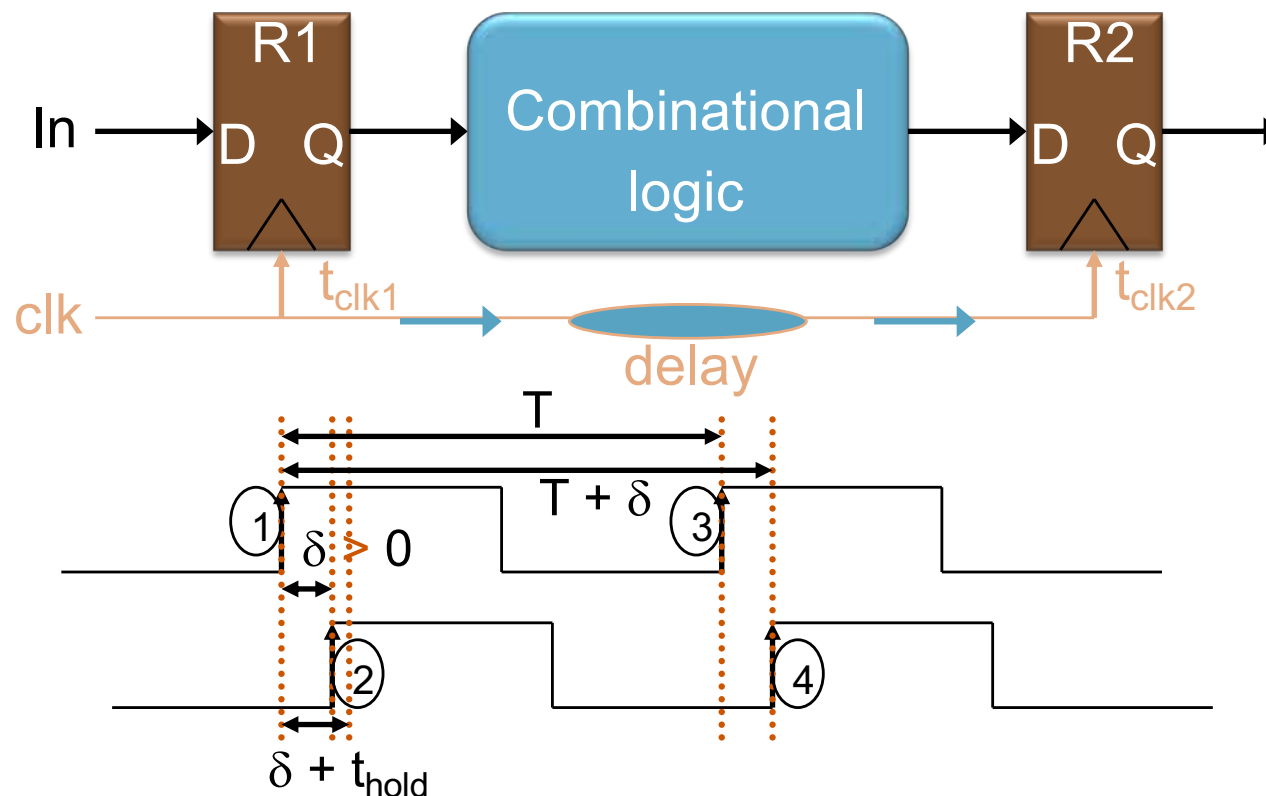
# Positive Clock Skew

Clock and data flow  
in the same direction



$$T: \quad T + \delta \geq t_{c-q} + t_{plogic} + t_{su} \quad \text{so} \quad T \geq t_{c-q} + t_{plogic} + t_{su} - \delta$$


$$t_{hold}: \quad t_{hold} + \delta \leq t_{cdlogic} + t_{cdreg} \quad \text{so} \quad t_{hold} \leq t_{cdlogic} + t_{cdreg} - \delta$$

**δ > 0: Improves performance, but makes t<sub>hold</sub> harder to meet. If t<sub>hold</sub> is not met (race conditions), the circuit malfunctions independent of the clock period!**

© J. Rabaey, 2002

# Negative Clock Skew

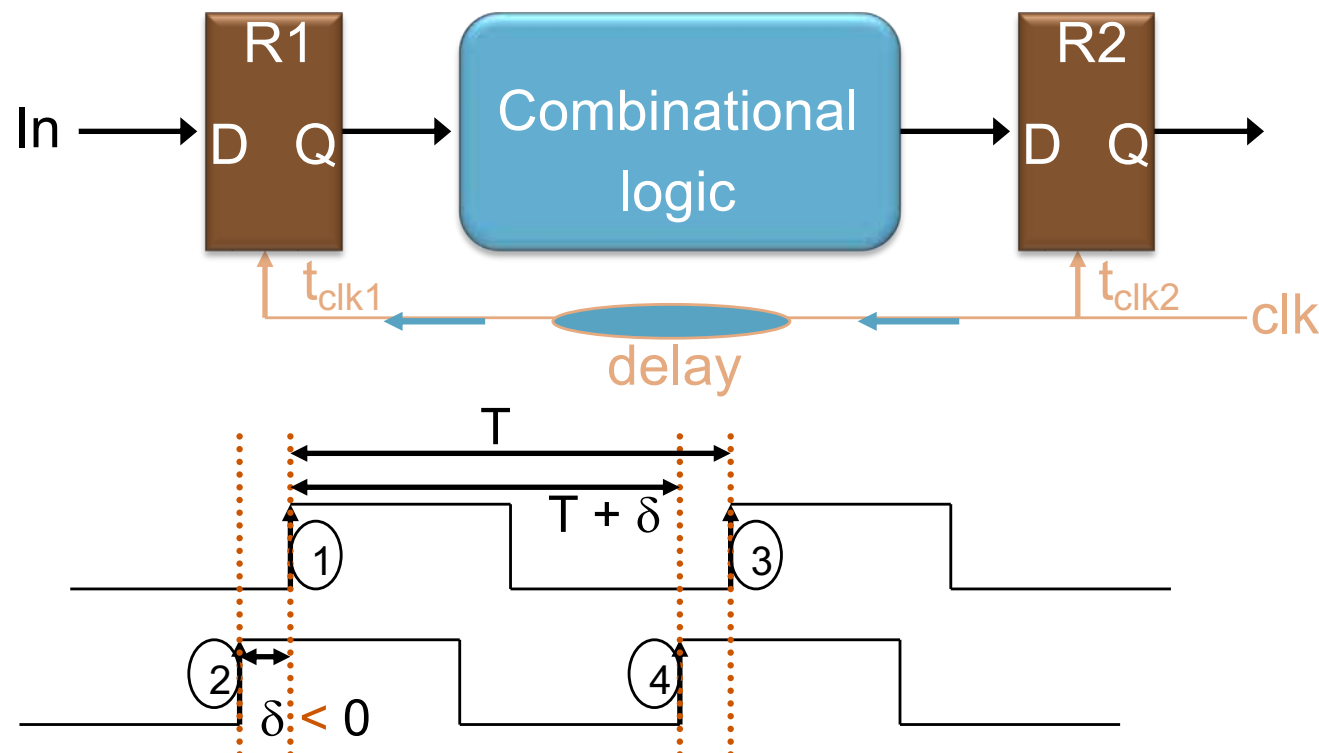**Clock and data flow in opposite directions**



$$T: \quad T + \delta \geq t_{\text{c-q}} + t_{\text{plogic}} + t_{\text{su}} \quad \text{so} \quad T \geq t_{\text{c-q}} + t_{\text{plogic}} + t_{\text{su}} - \delta$$


$$t_{\text{hold}}: \quad t_{\text{hold}} + \delta \leq t_{\text{cdlogic}} + t_{\text{cdreg}} \quad \text{so} \quad t_{\text{hold}} \leq t_{\text{cdlogic}} + t_{\text{cdreg}} - \delta$$

**$\delta < 0$ : Degrades performance ( $t_{\text{setup}}$ ), but  $t_{\text{hold}}$  is easier to meet (eliminating race conditions)**

© J. Rabaey, 2002

# Clock Jitter

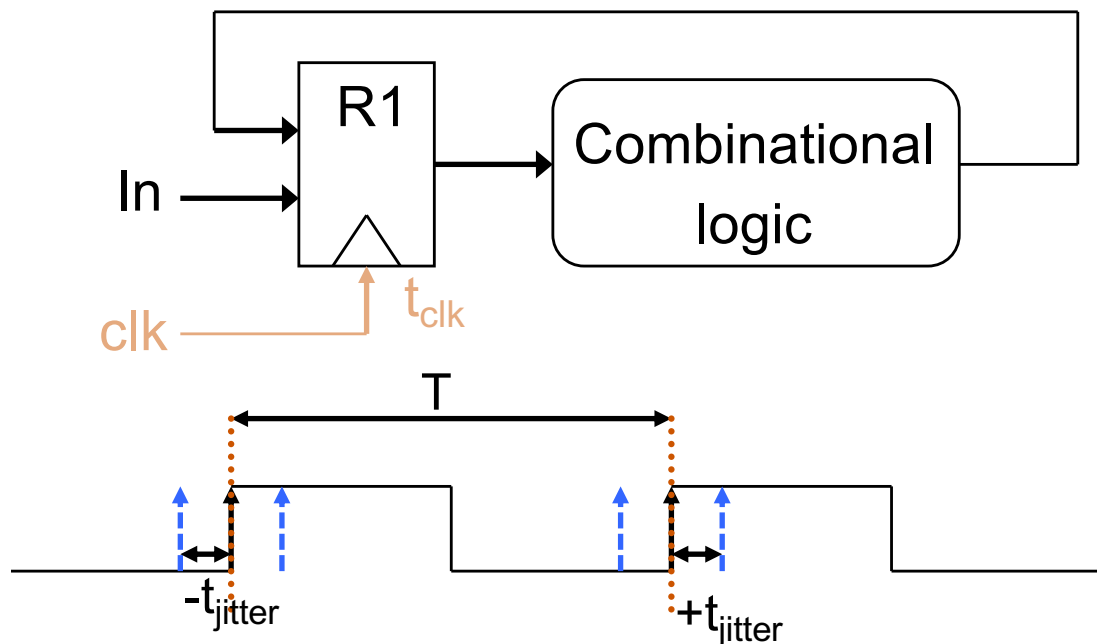**Jitter causes T to vary on a cycle-by-cycle basis**




$$T : T - 2t_{jitter} \geq t_{c-q} + t_{plogic} + t_{su} \quad \text{so} \quad T \geq t_{c-q} + t_{plogic} + t_{su} + 2t_{jitter}$$

**Jitter directly reduces the performance of a sequential circuit**

# Combined Impact of Skew and Jitter
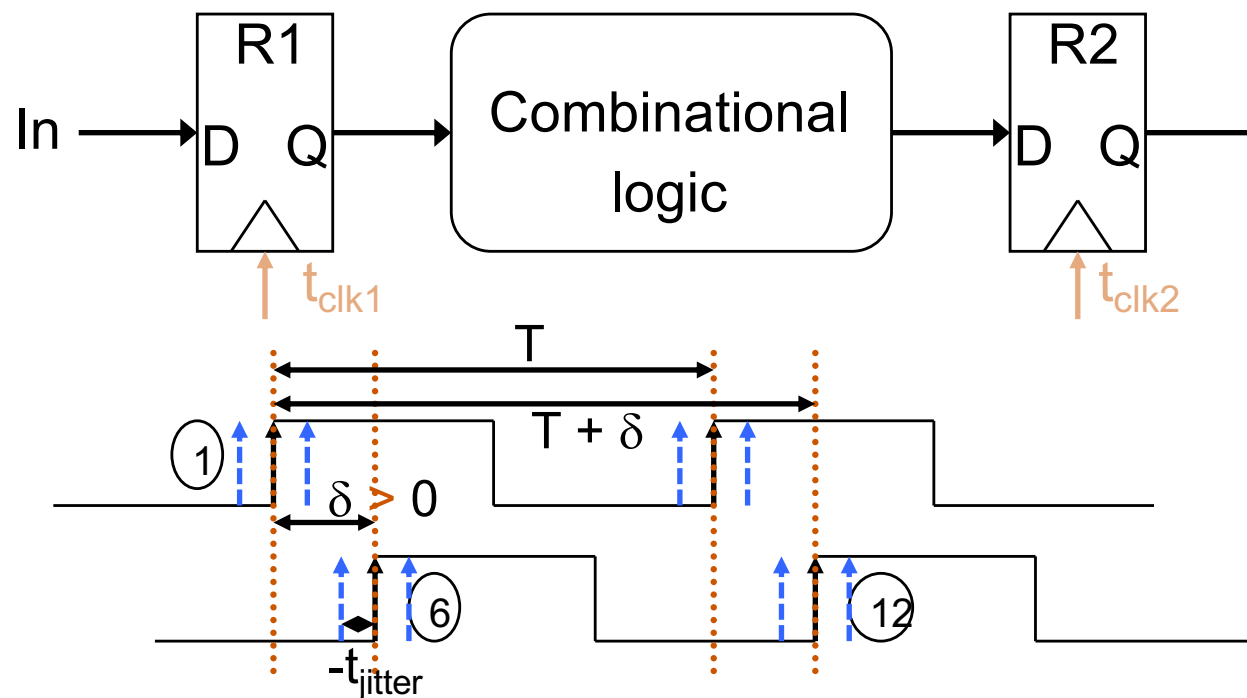
## Constraints on the minimum clock period ( $\delta > 0$ )



$$T \geq t_{c-q} + t_{plogic} + t_{su} - \delta + 2t_{jitter} \quad t_{hold} \leq t_{cdlogic} + t_{cdreg} - \delta - 2t_{jitter}$$

$\delta > 0$  with jitter: Degrades performance, and makes  $t_{hold}$  **even harder** to meet. (The acceptable skew is reduced by jitter.)


© J. Rabaey, 2002

# Clock Skew Solutions


---

- **Reduce clock skew**
  - Careful clock distribution network design
  - Plenty of metal wiring resources
  - Supply Filtering
  - Active de-skewing
  
- **Analyze clock skew**
  - Only budget actual, not worst case skews
  - Local vs. global skew budgets
  
- **Tolerate clock skew**
  - Choose circuit structures insensitive to skew
  - Take advantage of “**useful skew**”
 
# Jitter reduction using local supply filtering




Kurd, JSSC-2001

 

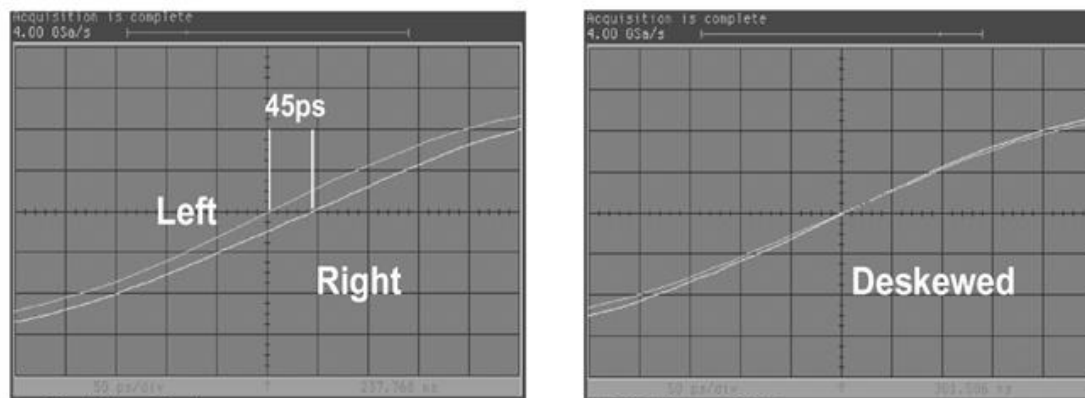
# Active Clock De-skewing

- Active clock de-skewing is accomplished by dynamically delaying the global clock signals.



 - This can result in clock jitter. Careful analysis is required to validate the benefits.





# Clock Distribution

- **There are four basic types of clock distribution networks used in high performance processor designs:**
  - Tree: IBM and Freescale PowerPC, HP PA-RISC
  - Grid: SPARC, Alpha
  - Serpentine: Pentium-III
  - Spine: Alpha, Pentium-4
- **Each technique has advantages and disadvantages:**

	Wire Cap	Delay	Skew
Grid	High – 15x	Low – sub100 ps	Low-Med
Trees	Low – 1x	High – 100's ps	Low
Serpentine	Very High – 30x	High – 100's ps	Low
Spine	High – 10x	Low-sub100ps	Med


# Clock Grids

---


- **Use grid on two or more levels to carry clock**
- **Make wires wide to reduce RC delay**
- **Ensures low skew between nearby points**
- **But possibly large skew across die**

# Alpha Clock Grids



Alpha 21064

 


Alpha 21164

 


Alpha 21264

  


gclk grid

 


gclk grid

 

Alpha 21064

 


Alpha 21164

 

Alpha 21264

 
# H-Trees

- **Fractal structure**
  - Gets clock arbitrarily close to any point
  - Matched delay along all paths
- **Delay variations cause skew**
- **A and B might see big skew**


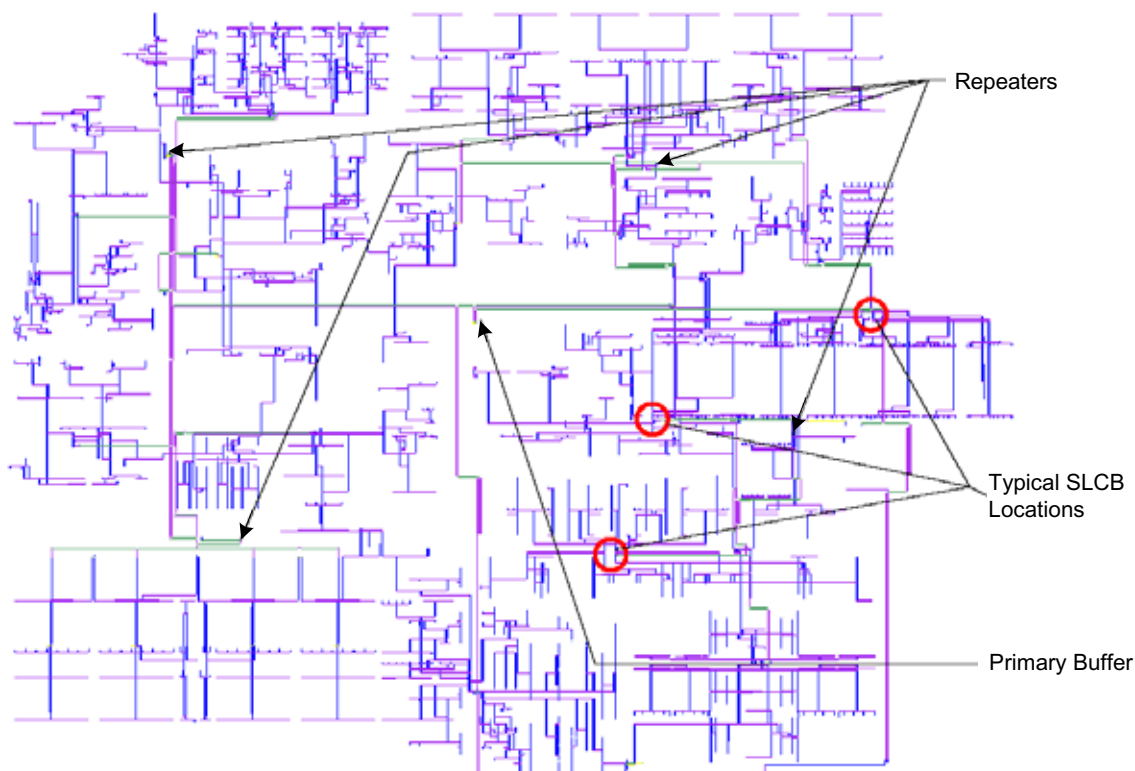
# Itanium 2 H-Tree

- **Four levels of buffering:**
  - Primary driver
  - Repeater
  - Second-level clock buffer
  - Gater
- **Route around obstructions**



# Hybrid Networks

---

- **Use H-tree to distribute clock to many points**
- **Tie these points together with a grid**
  
- **Ex: IBM Power4, PowerPC**
  - H-tree drives 16-64 sector buffers
  - Buffers drive total of 1024 points
  - All points shorted together with grid

# Dealing with Clock Skew and Jitter

---

- To minimize skew, balance clock paths using H-tree or matched-tree clock distribution structures.
- If possible, route data and clock in opposite directions; eliminates races at the cost of performance.
- The use of gated clocks to help with dynamic power consumption make jitter worse.
- Shield clock wires (route power lines – VDD or GND – next to clock lines) to minimize/eliminate coupling with neighboring signal nets.

© J. Rabaey, 2002

# Dealing with Clock Skew and Jitter

---


- **Use dummy fills to reduce skew by reducing variations in interconnect capacitances due to interlayer dielectric thickness variations.**
- **Beware of temperature and supply rail variations and their effects on skew and jitter. Power supply noise fundamentally limits the performance of clock networks.**

© J. Rabaey, 2002



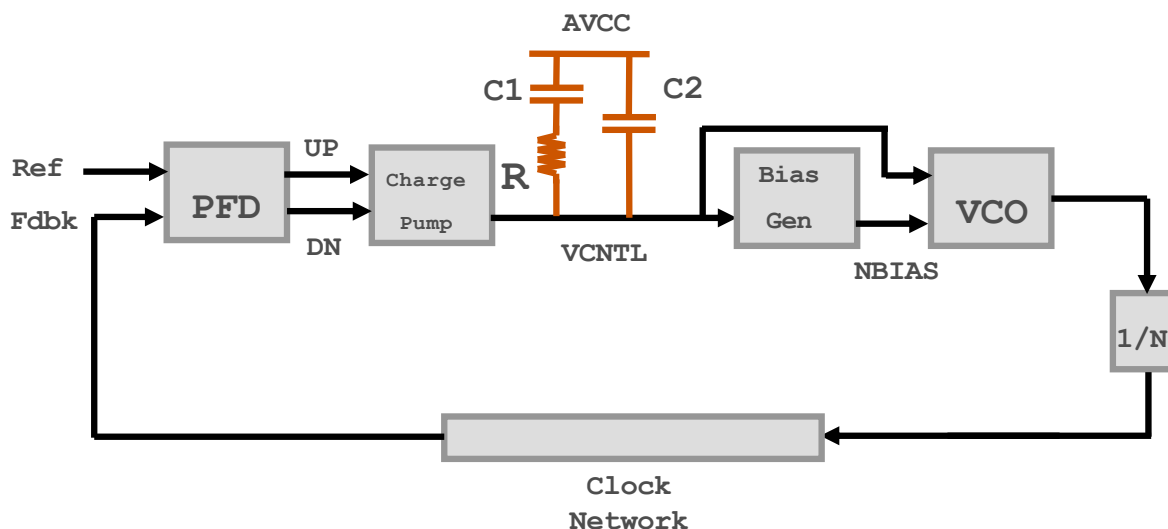
# PLL Synchronization

- There are two techniques used to synchronize the clocks in a high performance system: Phase Locked Loop (PLL) or a Delay Locked Loop (DLL)
- The PLL is used to “phase” synchronize (and probably multiply) the system clock WRT to a reference clock (internal or external).
  - PLL features:
    - Frequency Multiplication to run processor at faster speed than memory interface.
    - Skew reduction. The reference clock is “aligned” to the feedback clock.
    - Possible “stability” issues with PLL due to 2nd or 3rd order loop behavior.



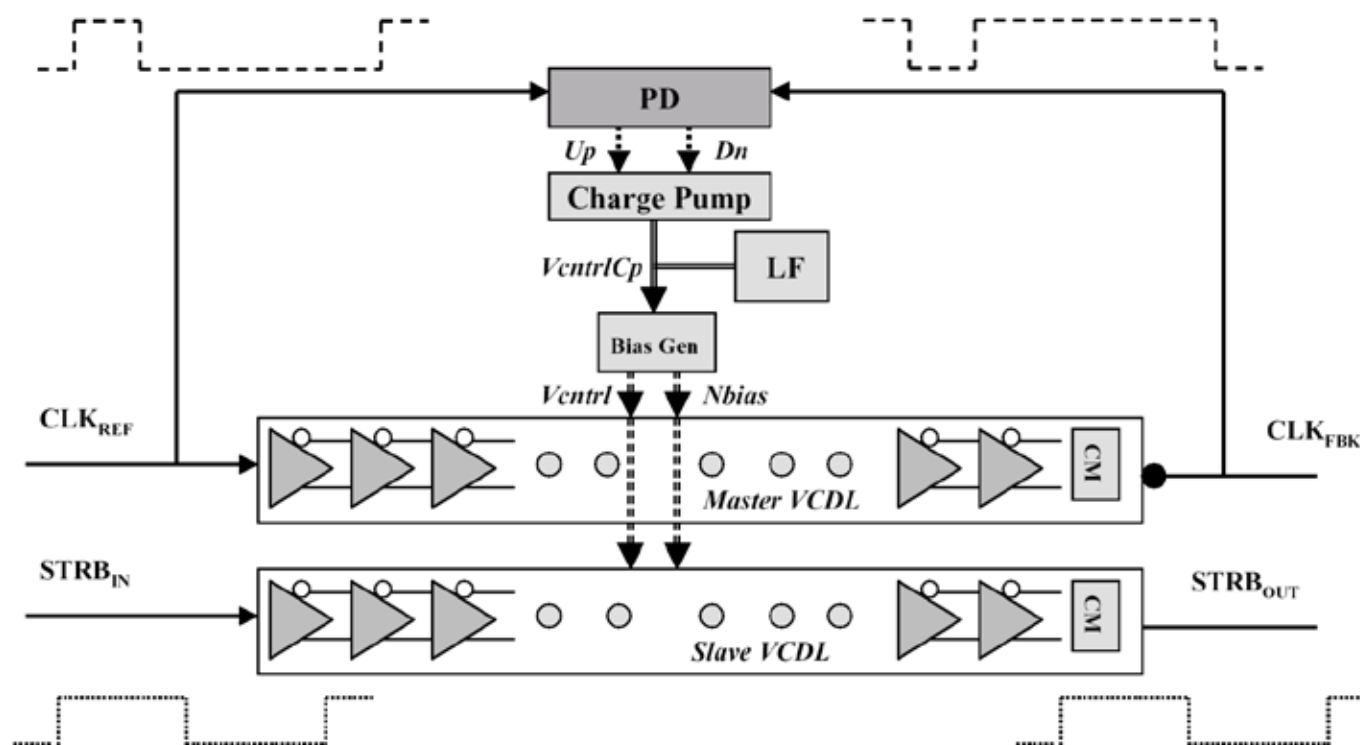
# DLL Synchronization

- The DLL is used to “delay” synchronize the system clock to a reference clock.
- Some high performance systems use a combination of both to generate the various clocks in a multiple clock domain design.
  - SOC designs can have many multiple frequency clock domains.




# Chip-2-Chip PLL Synchronization

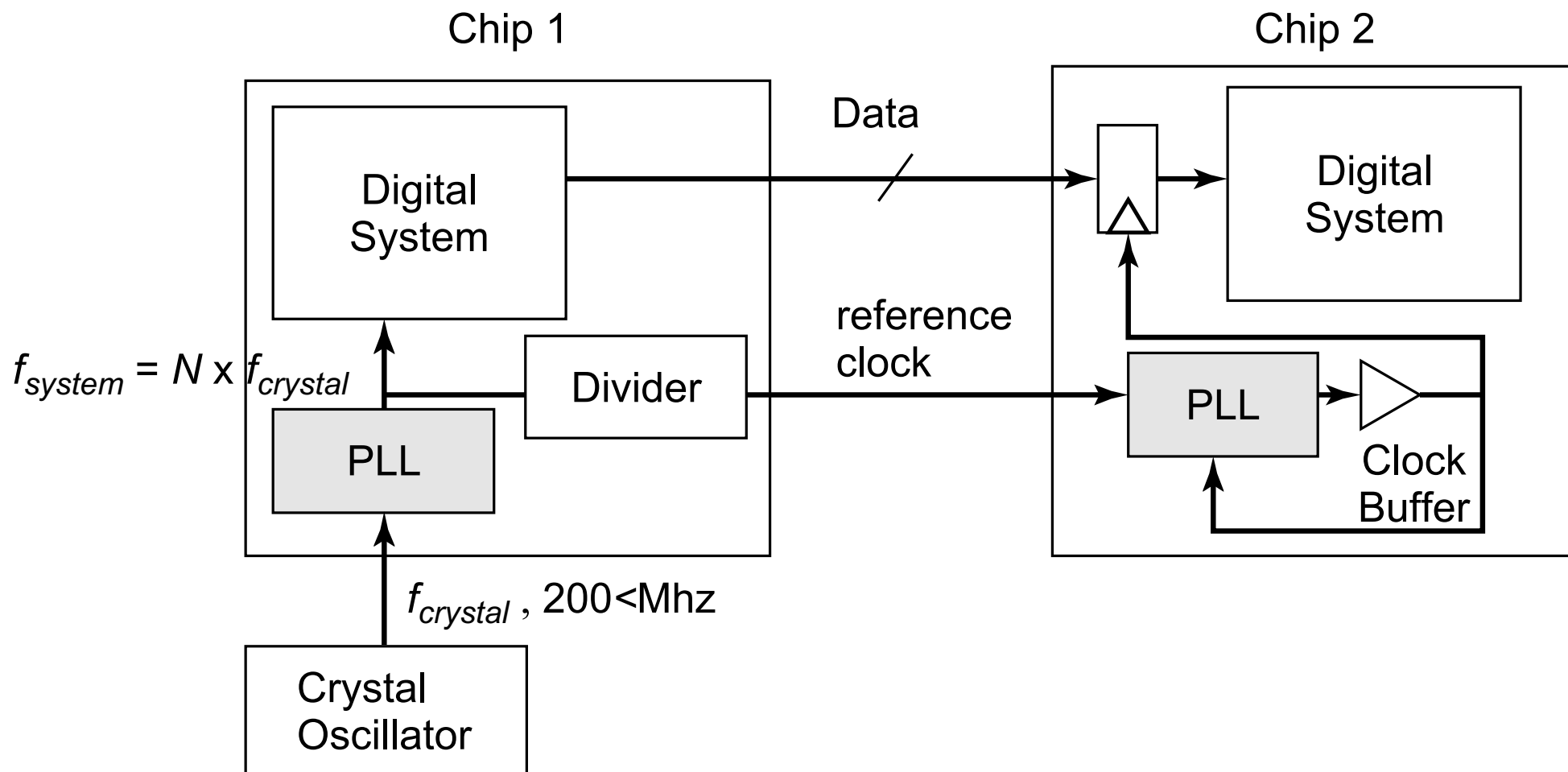


© J. Rabaey, 2002
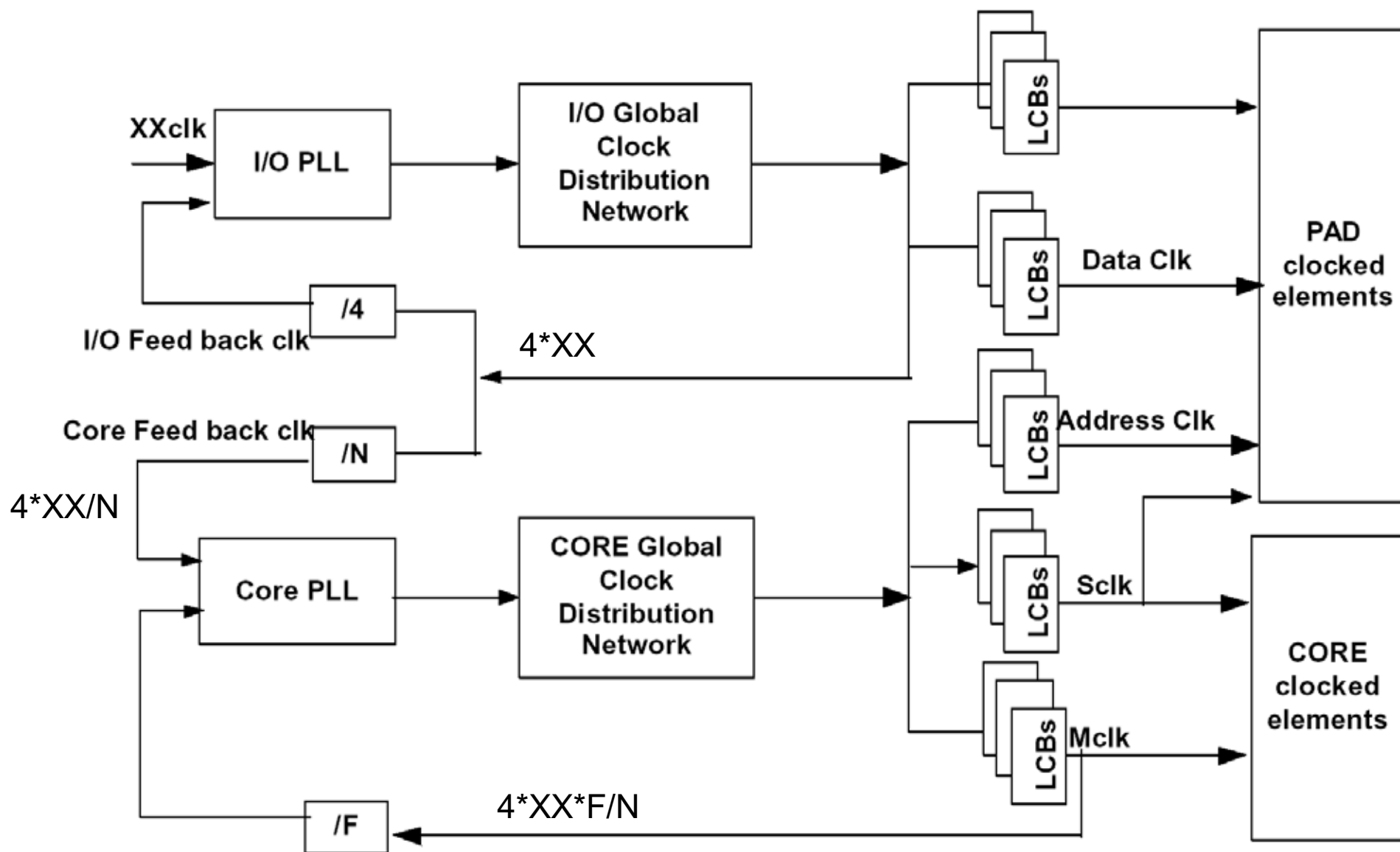
# High Performance Processor Clock Network



# Clock Distribution tree for a Datapath

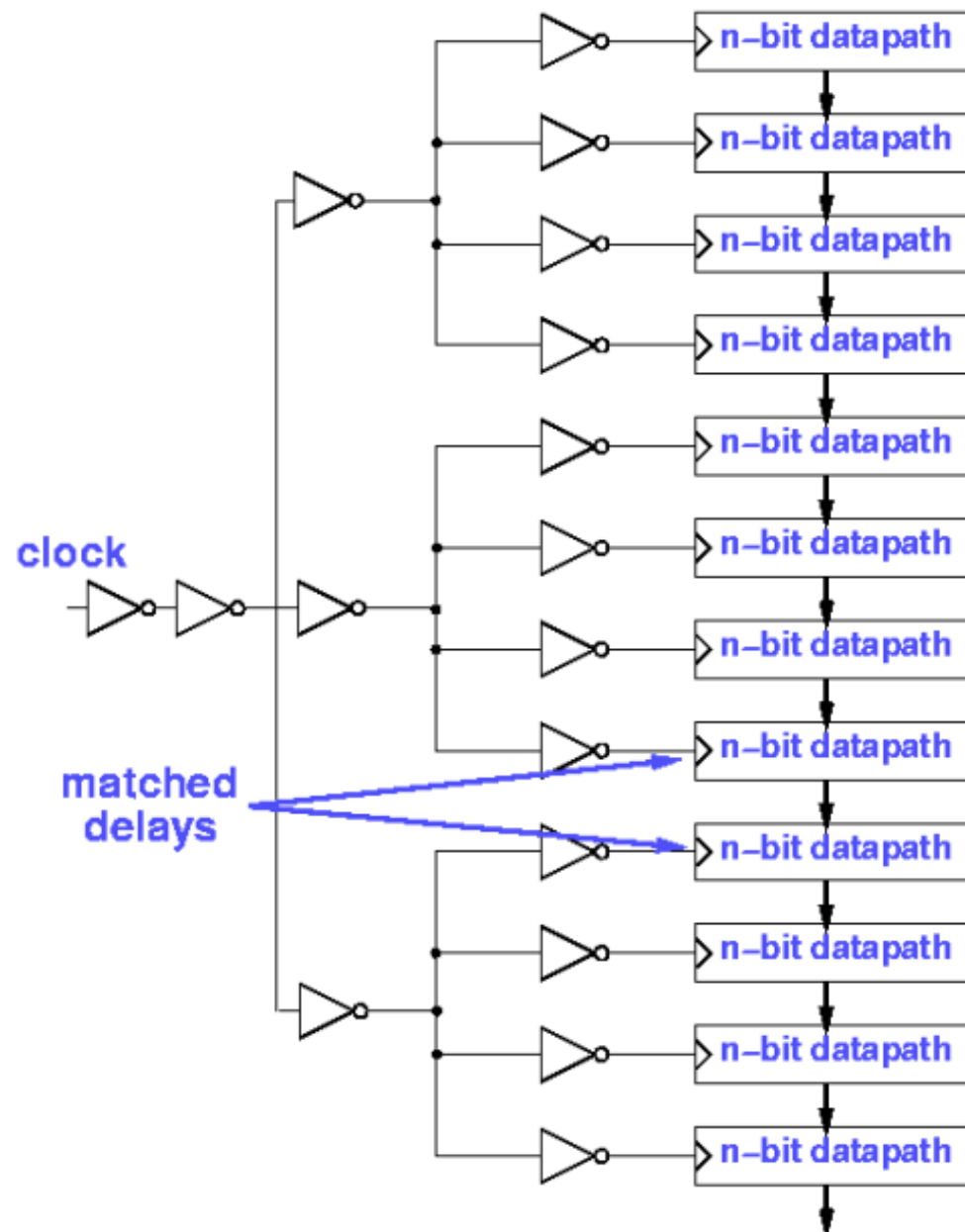

High peak currents to drive  
typical clock loads  
(¼ 1000 pF)

$$I_{peak} = C \frac{dV}{dt},$$

$$P_d = CV_{DD}^2 f$$

# Matching Delays in Clock Distribution


---

- **Balance delays of paths**
- **Match buffer and wire delays to minimize skew**
- **Issues**
  - Load of latch (driven by clock) is data-dependent (capacitance depends on source voltage)
  - Process variations
  - IR drops and temperature variations
- **Need tools to support clock tree design**


# Backup
 
# Variations of tree distribution networks


- *Target: Metallization and Gate topology uniformity*




Tree

 

X-Tree

 


H-Tree

 


• Tapered H-Tree



# Clock Generation

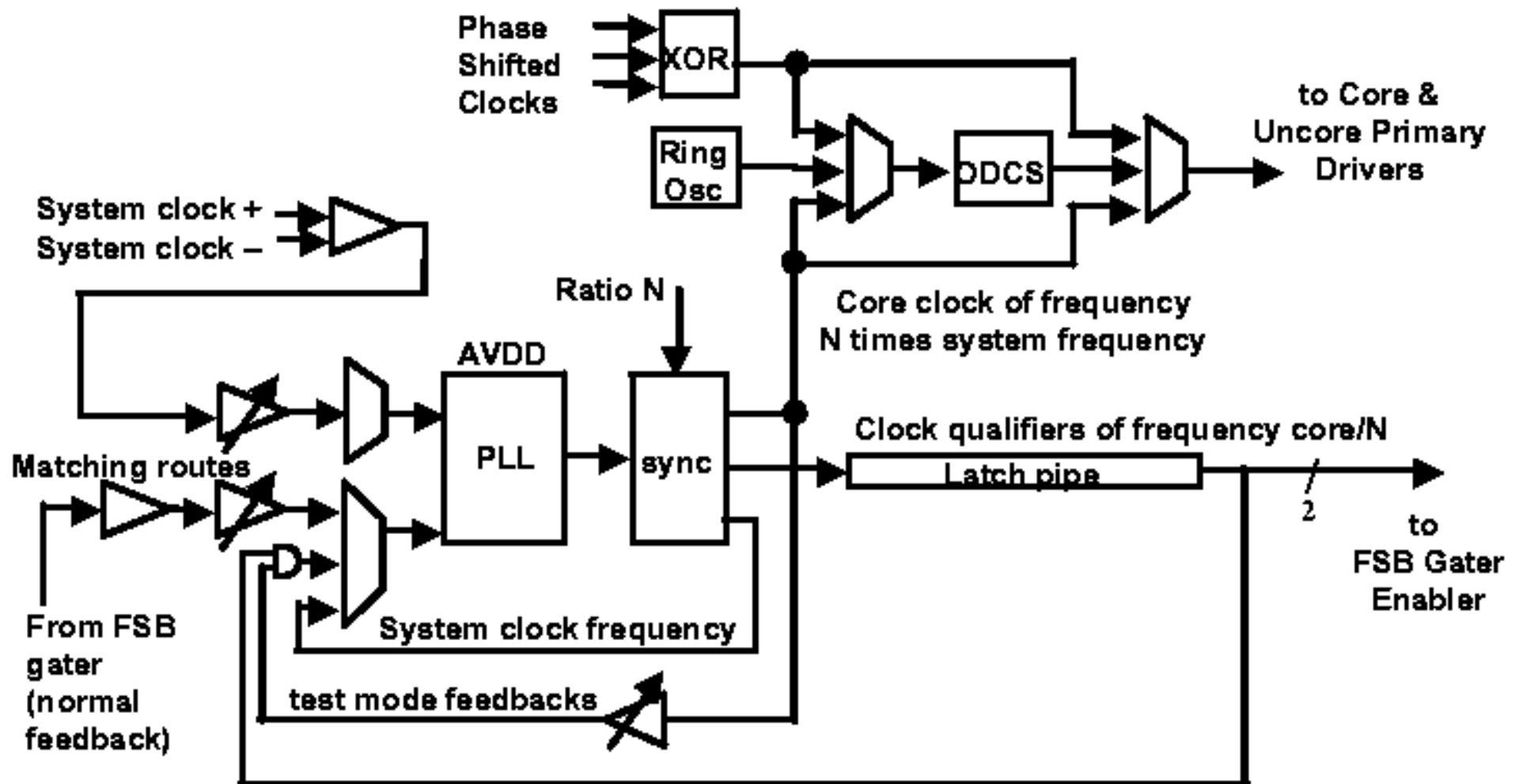


# Core Clock Distribution

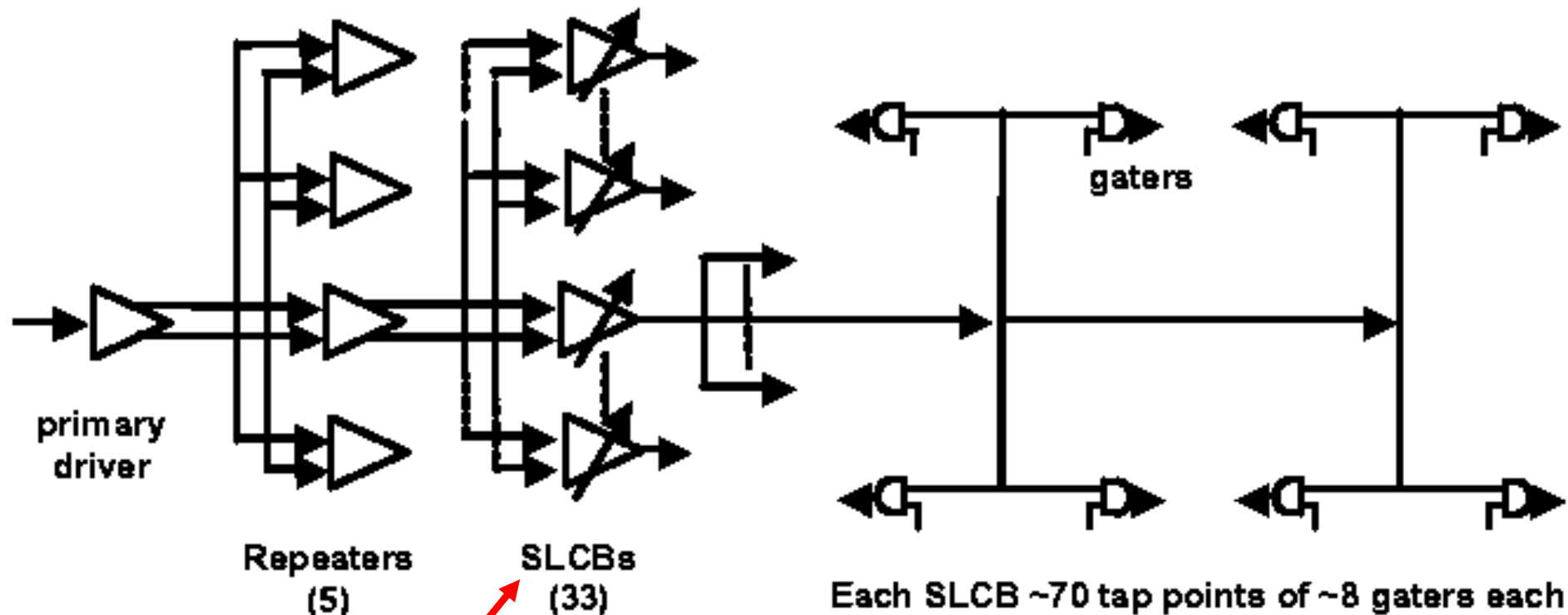


Adjustable delay buffer

# SLCB (Second Level Clock Buffer)

## SLCB Schematic

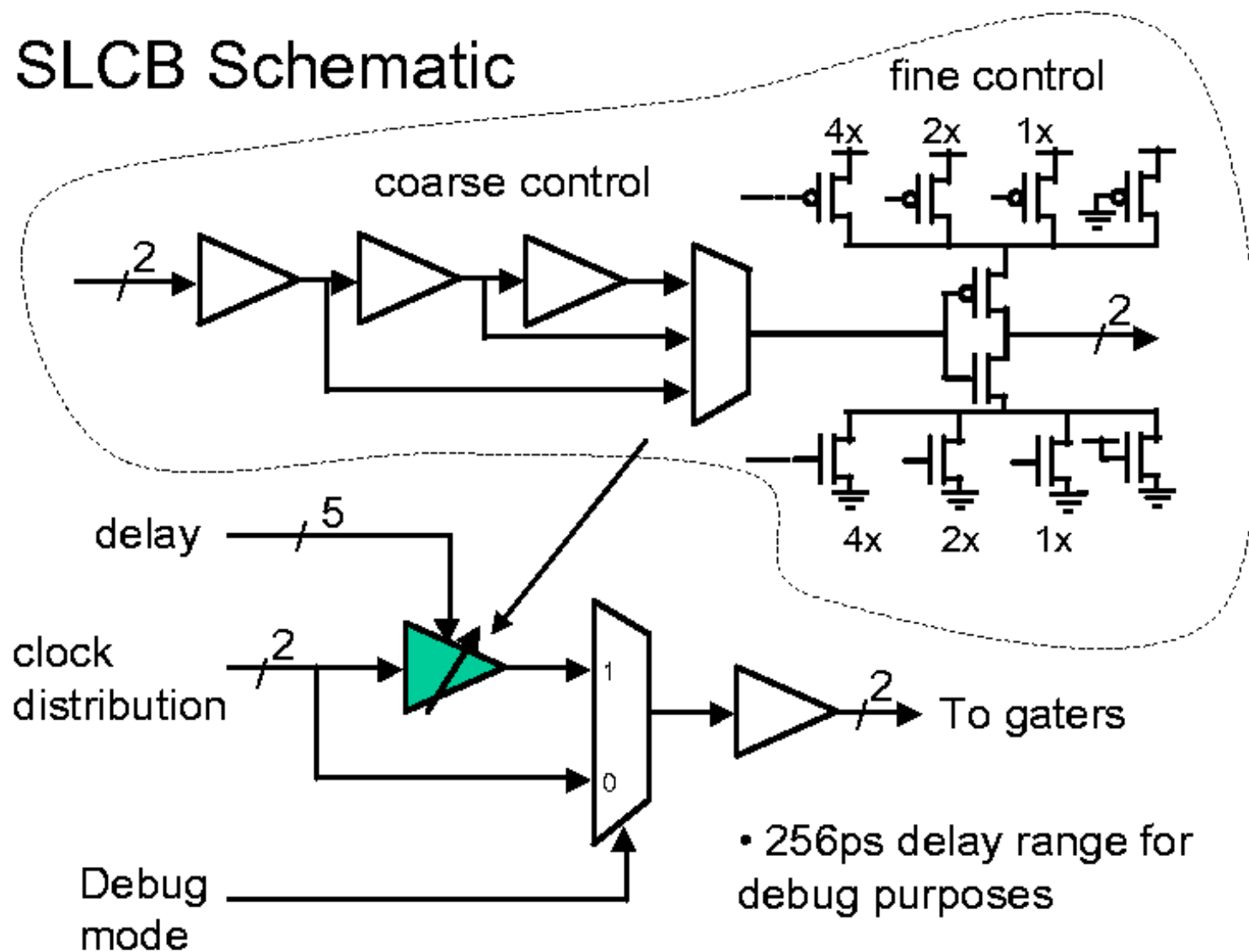


# First Level Route Geometry


 

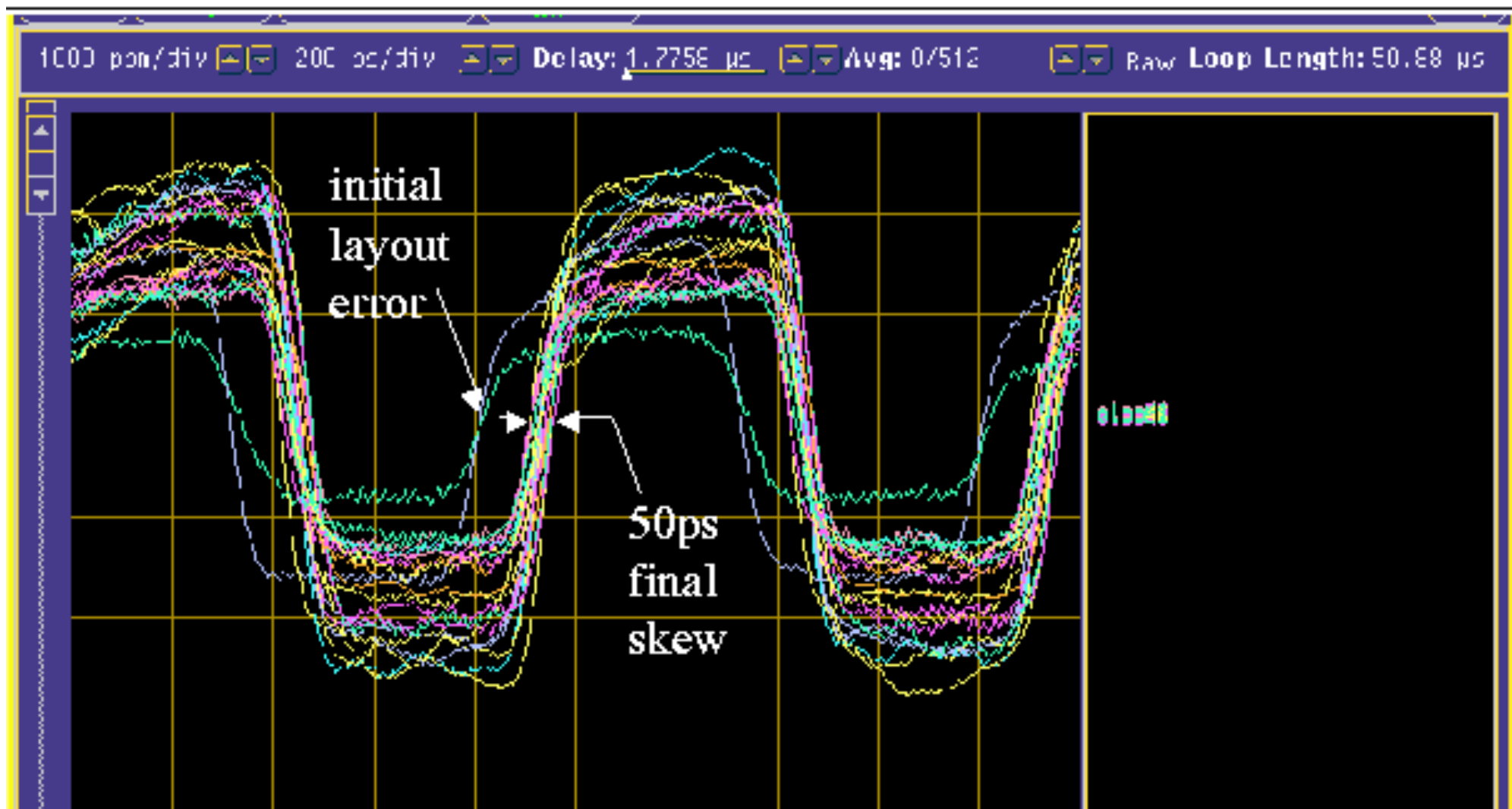
# Measured Skew

Laser probed SLCB skew (non-loading, valid DC levels)



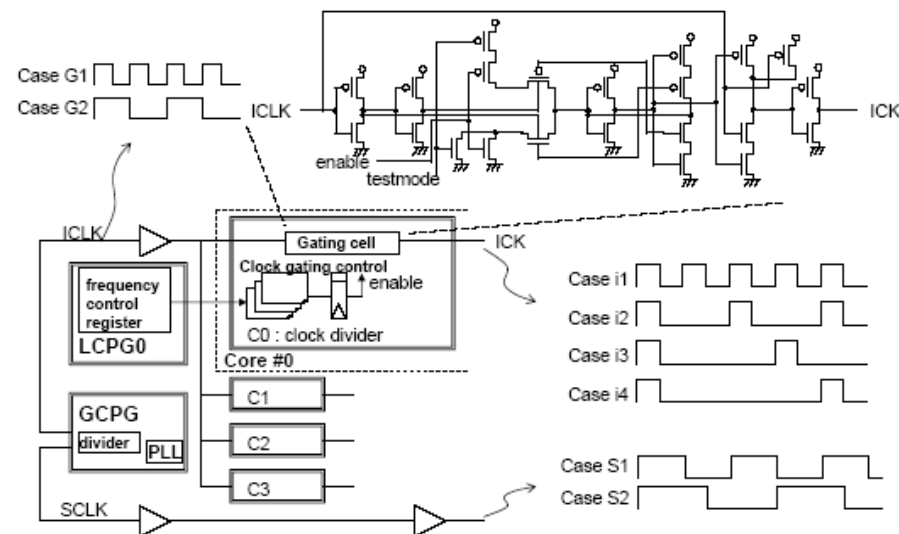
 
# ISSCC 2007: Multi-Core Clocking Approach Asynchronous Communication and Independent Core Frequencies



- Source: An Integrated Quad-Core Opteron™ Processor
- ISSCC 2007


- Source: A 4320MIPS Four-Processor Core SMP/AMP with
- Individually Managed Clock Frequency for Low
- Power Consumption, ISSCC 2007

# Non-overlapping clock generator

  
 
# HP PA-RISC Clock Distribution

- ◆ Plan the clock usage points to minimize the distribution area
- ◆ Large caches do not require the clock to be distributed over them
- ◆ Example from the HP RISC design:
  - ◆ 1 Receiver Buffer (R)
  - ◆ 3 Primary Buffers (P)
  - ◆ 19 Secondary Buffers (S)
  - ◆ Balanced Tree Distribution
  - ◆ Die Size 21.3 x 22.0 mm




Source: P. Barnes, A 500MHz 64b RISC CPU with 1.5MB On-Chip Cache, ISSCC'99




 
# IBM PowerPC Clock Distribution

- ◆ 0.22 $\mu$ m technology
- ◆ 17mm x 17mm die size
- ◆ 19M transistors
- ◆ 6 level metal with copper interconnect technology
- ◆ Clock tree on top 2 metal levels
- ◆ 1 GHz clock frequency
- ◆ Almost symmetric H-tree
- ◆ Simulated clock skew under 15ps



•Source: A 1GHz single-issue 64b PowerPC processor, ISSCC'2000

# Sun Microsystems UltraSparc III

 
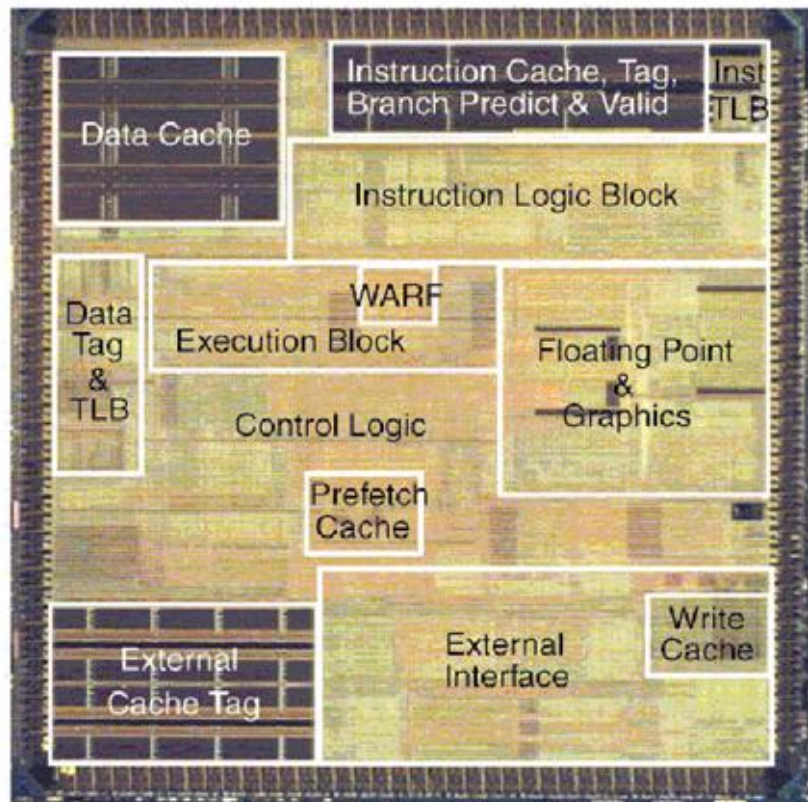


- ◆ 15.0 x 15.5 mm die size, 23M transistors
- ◆ Overall clock skew <80ps




  
# DEC Alpha 21164 Clock Distribution

- ◆ Clock Frequency: 300MHz
- ◆ 9.3 Million transistors
- ◆ Total Clock Load: 3.75nF
- ◆ Power in Clock Distribution network: 20W (out of 50 total)
- ◆ Uses two level clock distribution
  - ◆ Single 6-stage driver at center of chip
  - ◆ Secondary buffers drive left and right side clock grid in M3 and M4
  - ◆ Total driver size: 58cm !!



# DEC Alpha 21264 Clock Distribution

  



- ◆ 600MHz, 9.3M transistors, 0.35 $\mu$ m CMOS, 6 metals, 72W power dissipation at 2.0V
- ◆ Total clock load: 2.8nF

Gronowski, JSSC 1998



# Pentium® 4 Processor Clock Network



- 2GHz triple-spine clock distribution

  

Kurd, JSSC-2001
  
# IBM POWER-4 in .18u SOI


- H-Tree and Grid Distribution
- Clock skew: <25ps
- ~70% power in clock and
- Dual core, shared L2
- 174M transistors
- 115W at 1.1GHz, 1.5V



Source: Physical Design of a Fourth-Generation POWER GHz Microprocessor, ISSCC'2001



# IBM POWER-4 3D Skew Visualization

 

# Clock Skew across CELL Processor Global Clock Distribution

 


Figure 10.2.2: Clock-skew map.