


Avoiding Metastability in FPGA Devices

David Landoll
Applications Architect
Mentor Graphics Corp.

MAPLD 2009


**Mentor
Graphics®**

Today's FPGAs

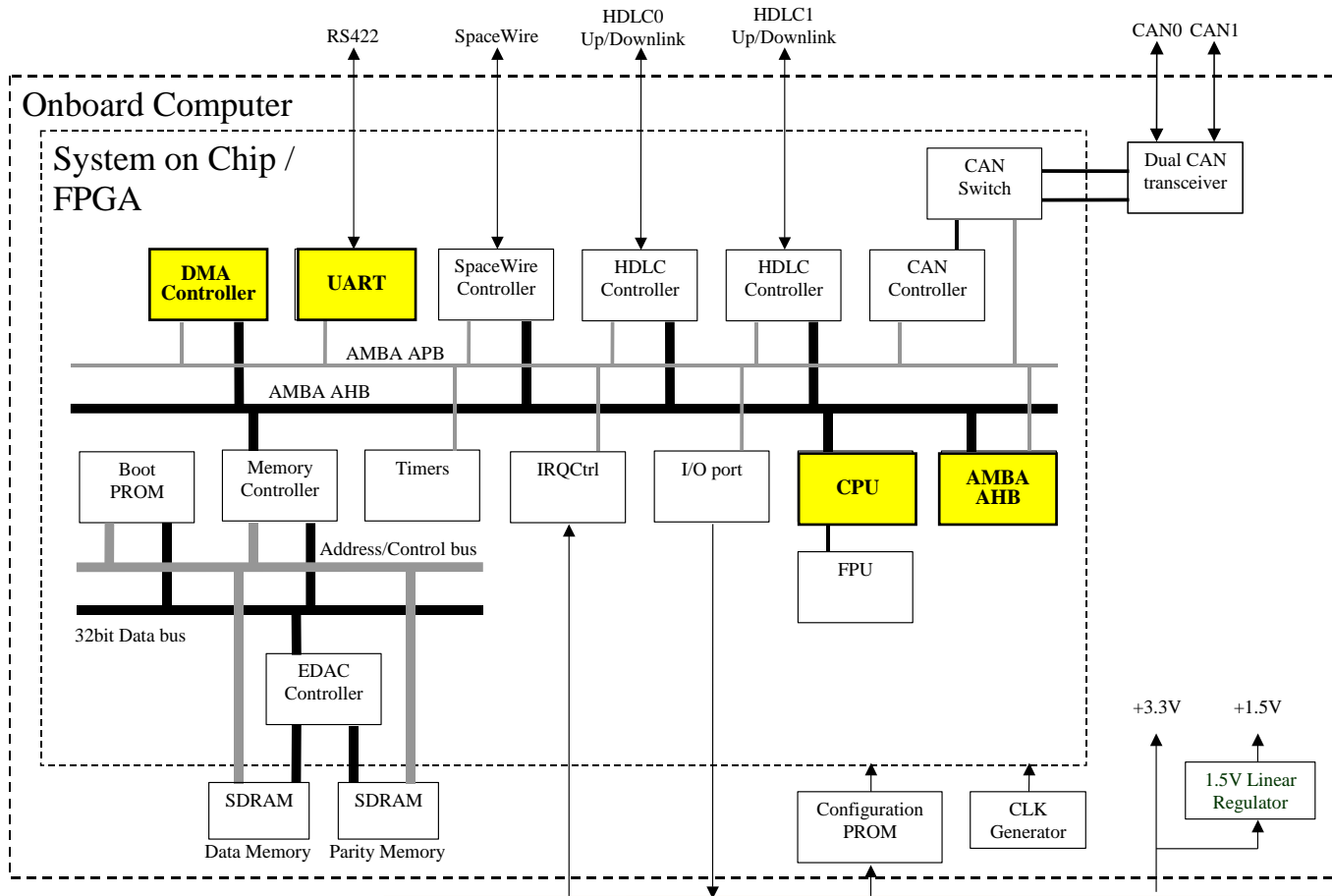

- Fabrication advances provide more available silicon area
- More functionality can weigh less and take up less space
- Integrating/reusing capabilities lowers cost

Integration Presents New Challenges

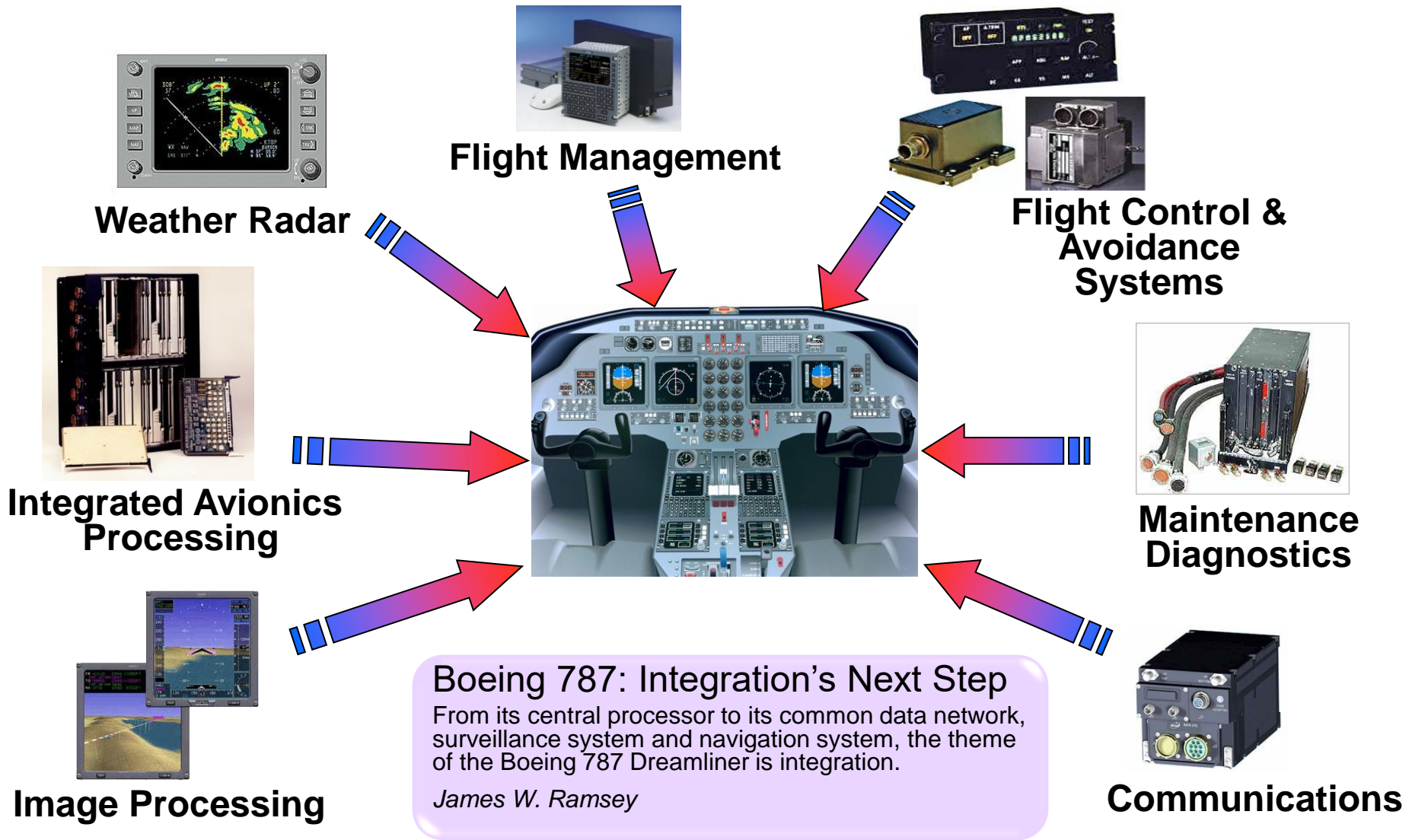

Such integration usually involves multiple independent clock domains, which leads to clock-domain crossings and metastability errors!

Clock Domain Crossing (CDC) Errors

Unpredictable Loss of Data

■ CDC problems

- corrupt control and data signals
- are subtle, intermittent, unpredictable
- are the 2nd major cause of respins
- are difficult to reproduce and debug
- are temperature, voltage, and process sensitive
- *will only* occur in hardware; often in the final design



■ Traditional verification techniques *do not* work for CDC signals


A CDC Verification methodology is needed to reduce the risk of CDC related data errors

Metastability

What the heck is it, anyway?

■ What is a clock?

 - Periodic pulsing signal
- Digital logic uniformly connected to this signal
- Acts as the Symphony Conductor – keeps logic in sync
- Action happens across the logic at one specific point
 - Typically the “rising edge”



Metastability

What the heck is it, anyway?

■ What's in a register?


- (Also known as a latch, flip-flop, etc)
- **Contain transistors that “trap” the input value at the appropriate time**
 - E.g. rising edge of the clock
- **How does this happen?**




Metastability

The Physics of a Register

 - Let's take a look at a register
 - CMOS D-type transmission gate flip-flop


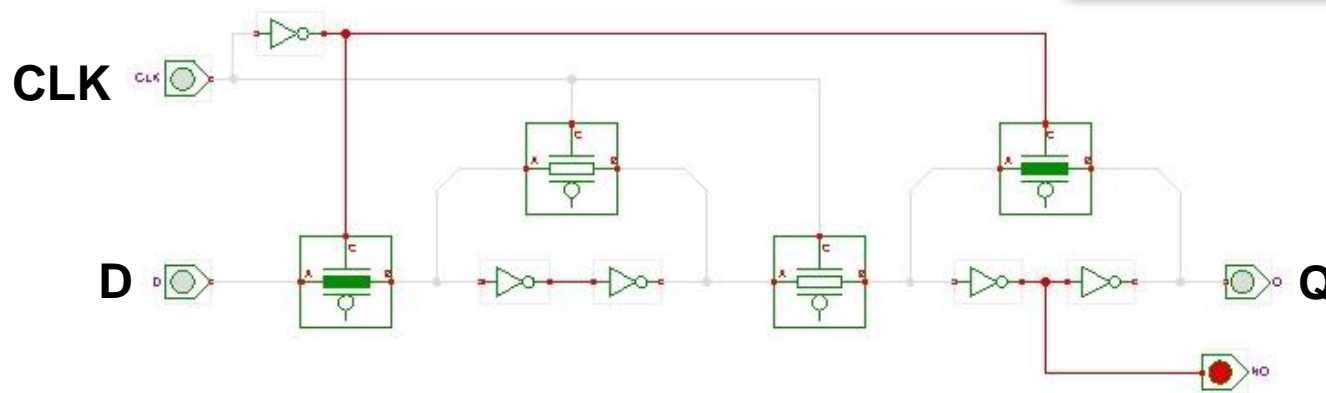
```
-- simple D-type flip-flop
process (CLK)
begin
    if rising_edge (CLK) then
        Q <= D;
    end if;
end process;
```




Transistor Model of a D Flip-Flop


Metastability

The Physics of a Register

 - Let's take a look at a register
 - CMOS D-type transmission gate flip-flop


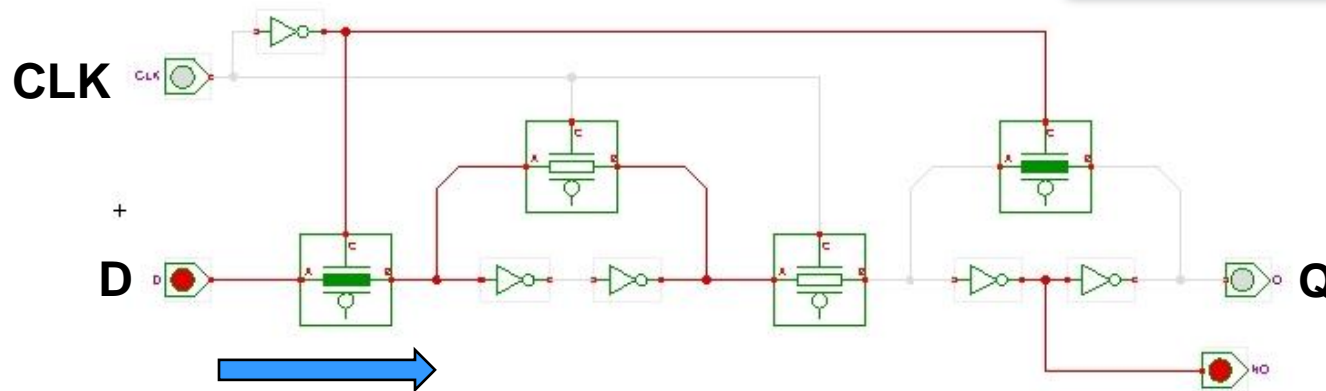
```
-- simple D-type flip-flop
process (CLK)
begin
    if rising_edge(CLK) then
        Q <= D;
    end if;
end process;
```




Transistor Model of a D Flip-Flop


Metastability

The Physics of a Register

 - Let's take a look at a register
 - CMOS D-type transmission gate flip-flop


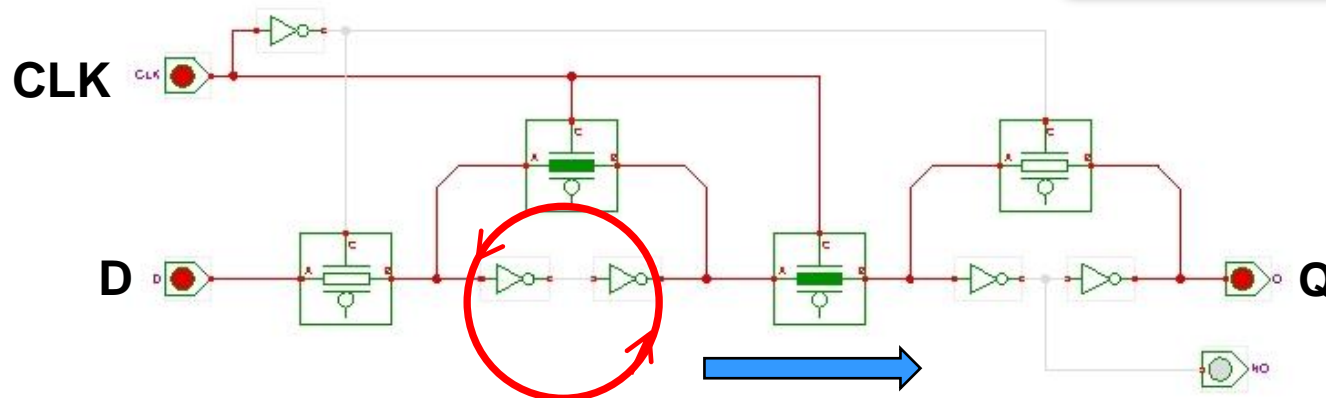
```
-- simple D-type flip-flop
process (CLK)
begin
    if rising_edge (CLK) then
        Q <= D;
    end if;
end process;
```




Transistor Model of a D Flip-Flop


Metastability

The Physics of a Register

 - Let's take a look at a register
 - CMOS D-type transmission gate flip-flop


 
```
-- simple D-type flip-flop
process (CLK)
begin
    if rising_edge (CLK) then
        Q <= D;
    end if;
end process;
```




**Only works if D has a “good value” at the rising edge of the clock
(no Set-up/hold time violations)**

Metastability

The Physics of a Register

 - When setup/hold conditions are violated, the output of a storage element becomes unpredictable





- This effect is called **metastability**
- If not contained, metastability can propagate...

Metastability is UNAVOIDABLE in designs with multiple asynchronous clocks

Clock Domain Crossings Guaranteed to Cause Metastability

When 2 or more designs run on disparate clocks:

  - The clocks will continually skew, guaranteeing setup/hold violations
- Signals from one design to another are “Clock Domain Crossings” (CDCs)



**Signals that cross
asynchronous clock
domains (CDC signals)
WILL violate setup and
hold conditions**

Mitigating Clock Domain Crossing Issues

Problem:


- Signals crossing a clock domain will violate set-up/hold
- **Impact:** Control/data signals will be dropped/corrupted
 - *Loss of Data*

Approaches:

- **Avoid having systems that have multiple clocks**
 - Although sensible, it's becoming impossible
- **Design around the problem**
 - Designer can add “synchronizers” to the design
 - Metastability still happens, but nobody else sees it
 - E.g. 2DFF, FIFO, etc.
 - “Fences in” metastability




Isolate Metastability: Synchronizers

 

- Designers add synchronizers to reduce the probability of metastable signals
- Synchronizers are sub-circuits that can prevent metastable values from being sampled across clock domains
 - Take unpredictable metastable signals and create predictable behavior

Mitigating Clock Domain Crossing Issues


Isolate Metastability: Synchronizers

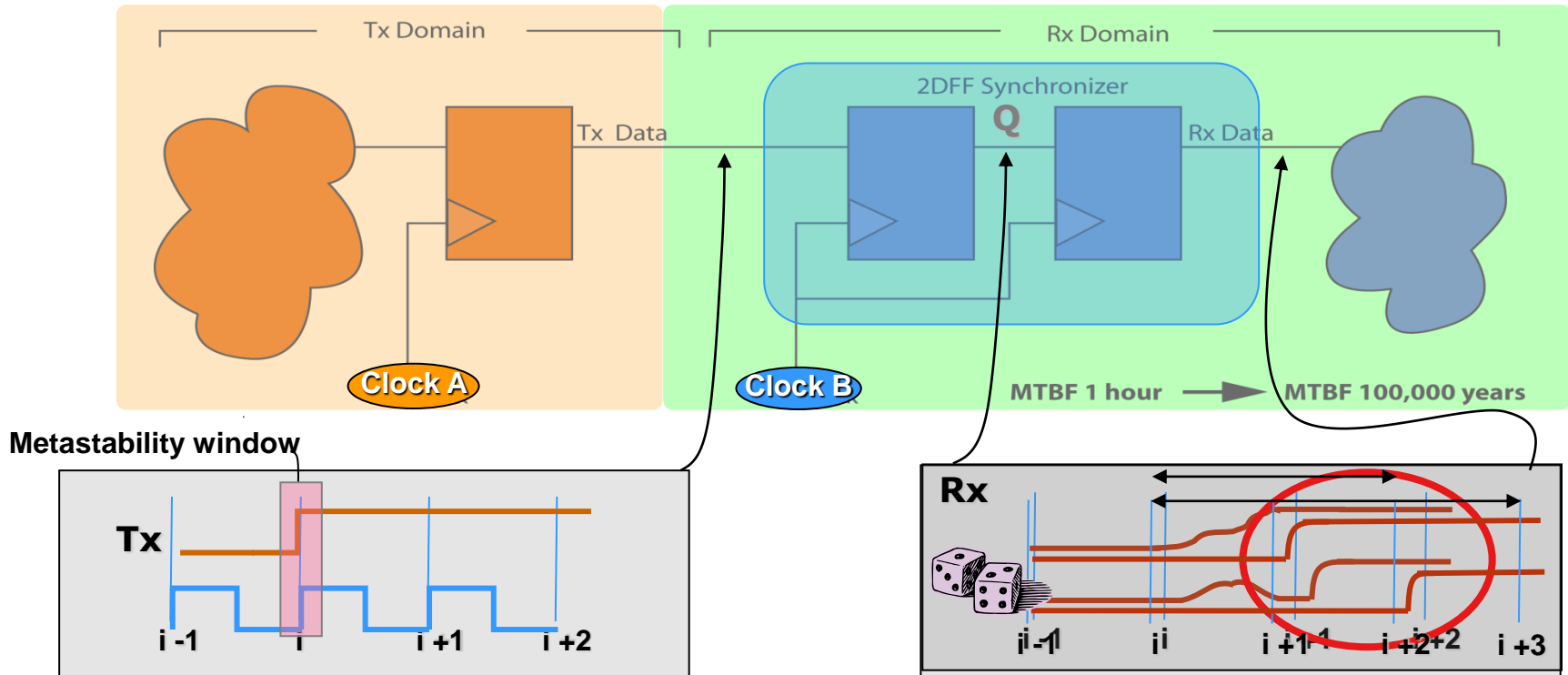

When metastability occurs, the delay through a synchronizer becomes unpredictable

Synchronizer Delays Can Reconverge *with unexpected results*


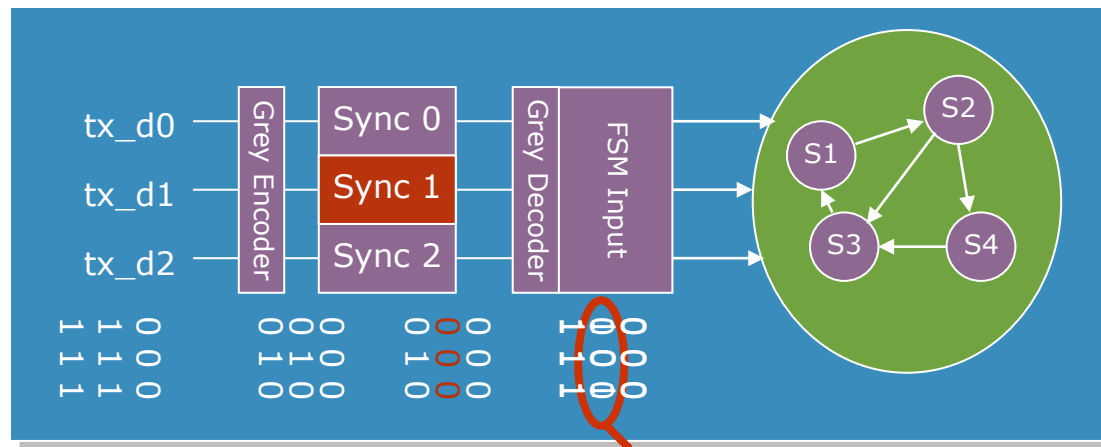
- CDC signals cross with an assumed relationship
- Can be combinational, sequential, or deeply sequential
- Unpredictable delays on CDC paths lead to reconvergence errors
 - Designs need logic to correctly handle reconvergence
 - Can occur on single-bit or multiple-bit signals



Invalid Command
Valid Command - but delayed


And, Synchronizers Fail if Misused

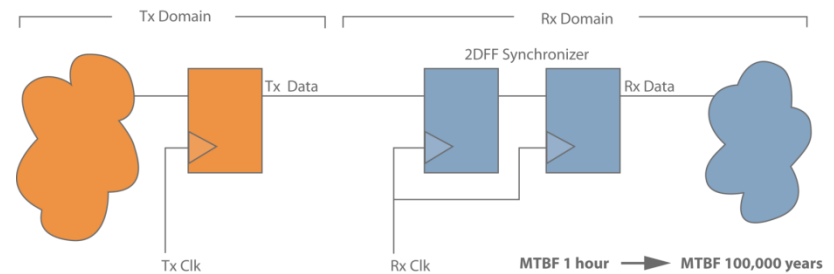 - Synchronization between clock domains *requires* a transfer protocol
 - Ensures data is *predictably* transferred between domains
- These protocols *must* be verified
- When protocol is violated
 - Data is lost
 - Simulation *may not* show a failure
 - Silicon *will* eventually show a functional error



Synchronizer won't function properly if the required Transfer Protocol is violated

 Verification Must Cover All Three CDC Problems



Clock domain crossings need:

- Structured synchronization
- Transfer protocols
- Global reconvergence checking

Mitigating Clock Domain Crossing Issues

■ Problem:

- Signals crossing a clock domain will violate set-up/hold
- **Impact:** Control/data signals will be dropped/corrupted

■ Approaches:

- Avoid having systems that have multiple clocks
- Designer can add “synchronizers” to the design
- **Designer-added synchronizers + full CDC verification**
 - Assures synchronizers are present and used correctly




Recommendations

During design planning

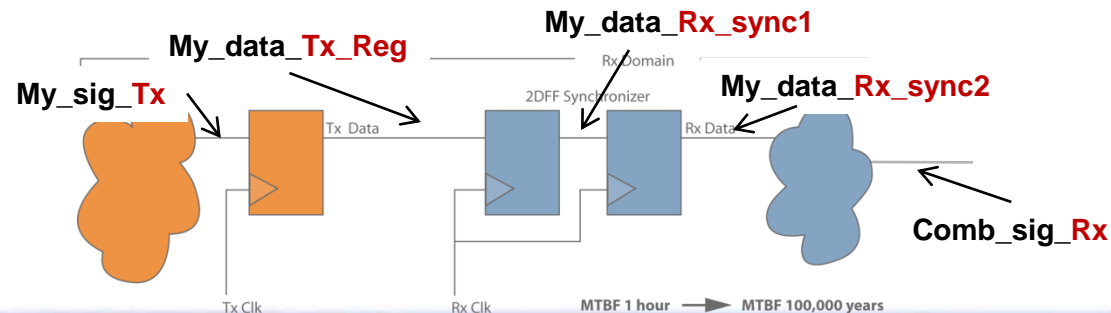1. Create systems/designs using 1 clk, 1 edge when possible
2. If multiple clocks are required, try to use 1 designer for both clock domains, and use coding guidelines
 1. Use signal naming conventions
 2. Many clock domain errors come from design changes, not the initial design

For Example:

- Append “_A_reg” to signals leaving A-clk register, “_A” for A-clk combo signals
- Leverage during code reviews - help identify missing synchronizers
- Make sure ONLY _A_reg signals go to synchronizers (no combo logic)



Verifying CDC Synchronization

■ Problem:

- Missing synchronizers will create metastability
- Correctly placed but misused synchronizers won't work
- Reconvergence of synchronized signals can create unexpected behavior


■ Approaches:

— Simulation

- Digital logic simulators do NOT model transistor behavior
- Do not model “metastability”


For example ...

Setup Violation

 

Simulation captures a '1' while silicon produces either a '1' or '0'

Hold Violation

 

Simulation captures a '0' while silicon produces either a '1' or '0'

Simulation Does NOT Reflect Silicon Behavior

Verifying CDC Synchronization

■ Problem:

- Missing synchronizers will create metastability
- Correctly placed but misused synchronizers won't work
- Reconvergence of synchronized → Control logic bugs

■ Approaches:

— Simulation

- Won't model CDC's correctly to detect errors

— Static Timing Analysis

- Can be used to identify signals that cross domains
- Can be used as input for a manual review
- But... Won't detect missing or incorrectly used synchronizers, or reconvergence

Verifying CDC Synchronization

■ Problem:


- Missing synchronizers will create metastability
- Correctly placed but misused synchronizers won't work
- Reconvergence of synchronized → Control logic bugs

■ Approaches:

- **Simulation**
 - Won't model CDC's correctly to detect errors
- **Static Timing Analysis**
 - Identifies signals for manual review, but otherwise useless
- **Manual Design Reviews**
 - Error prone (and very time consuming)
 - Typically only identifies synchronizer structures, misses reconvergence and invalid sync protocol usage
 - Evidence suggests at least some synchronizers will be missed

For Example...

Trivial Reconvergence Error

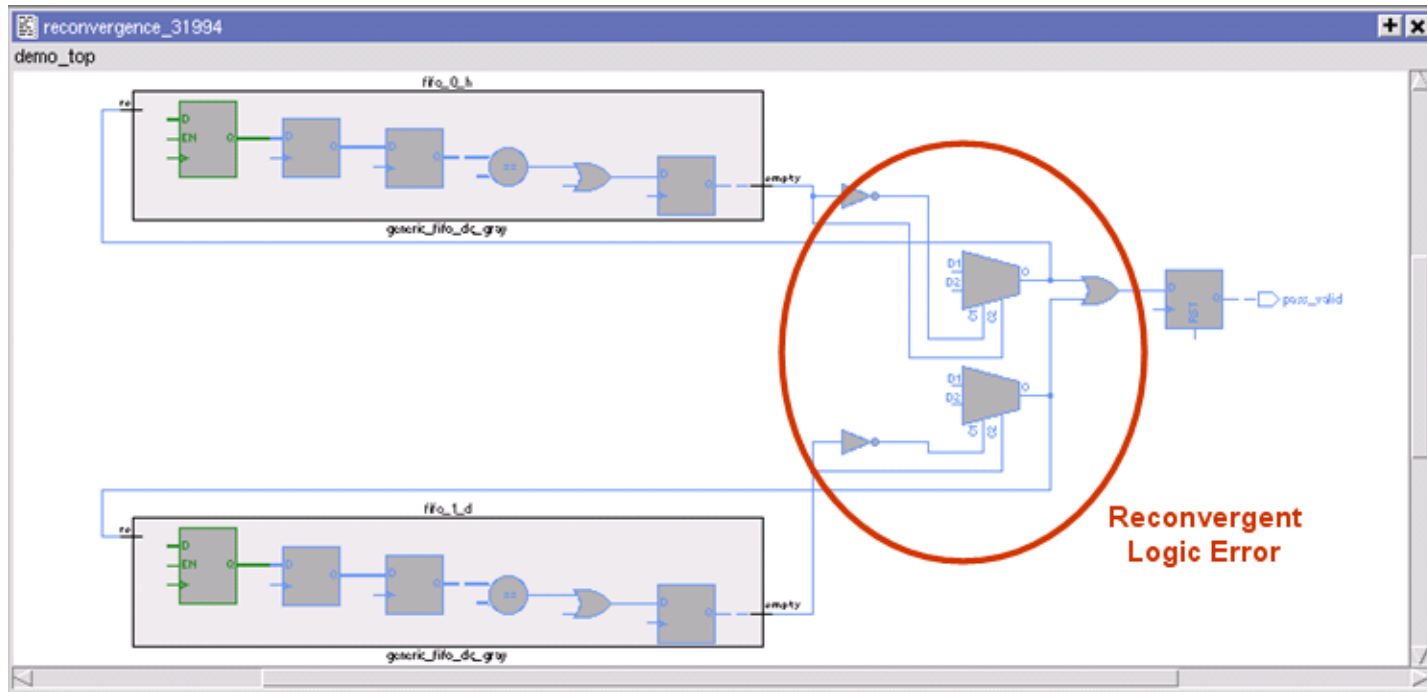

- **Reconverging synchronized CDC signals - timing is unpredictable.**
- **Need to verify the downstream logic can handle variations**
 - Manually identifying the reconvergence is very hard
 - Manually identifying all possible behaviors is harder
 - Manually assuring logic will behave correctly – typically intractable

Verifying CDC Synchronization

■ Problem:

- Missing synchronizers will create metastability
- Correctly placed but misused synchronizers won't work
- Reconvergence of synchronized → Control logic bugs

■ Approaches:

- **Simulation** - *Won't model CDC's correctly to detect errors*
- **Timing Analysis** - *Identifies signals for review, but otherwise useless*
- **Manual Design Reviews** - *error prone, incomplete*
- **Lab Verification?**
 - Problem is intermittent, debug is impossible
- **Spice simulation?** – It **does** model transistors, but...
 - Where will you get the “Spice deck”? (transistor level model)
 - Would be far too slow on a large FPGA



Verifying CDC Synchronization

■ Problem:

- Missing synchronizers will create metastability
- Correctly placed but misused synchronizers won't work
- Reconvergence of synchronized → Control logic bugs

■ Approaches:

- So - we need a new method that reliably:

- Identifies ALL CDC signals, structures, reconvergence
- Assures ALL connected, functioning correctly
- Creates reports for manual reviews

➔ The EDA industry has responded

- 6 commercial tools now available...and counting
- **But...most won't identify all 3 of our CDC issues**



Mentor's CDC Verification Technology

Who's using our technology?

■ Mil-Aero

- Honeywell, Inc.
- L-3 Communications
- Lockheed Martin Co
- Ministry of Aerospace & Aeronautics
- Northrop Grumman Corp
- Raytheon
- Rockwell Collins Inc.
- SAAB Group
- Thales

■ Commercial

- Widely used in commercial space

■ *The market leader in CDC verification*

Example Value from One Customer

■ Design

- IEEE standard serial communications core
- Used in 50-60 other COMMERCIAL ASIC products
- *Widely* deployed (millions in use daily)

■ Placed core in a sensor guidance system


- Found issues in the lab
- Debugged FPGA for weeks
- Suspected a CDC issue, but not sure...

■ Deployed Mentor's CDC solution

- Results same day
- ***Found 199 serious CDC bugs!***
 - 45 Missing Synchronizers
 - 83 Incorrect Synchronizers
 - 76 Reconverging Signals
 - 11 other problems
- ***Most resulting from “more stressful” usage***

■ In production:

 - *Commercial ASIC : Customer issue – device is erratic, locks up*
- ***Avionics: Could result in an Airworthiness Directive***



Summary

Recommendations



During design planning

1. Create systems/designs using 1 clk, 1 edge when possible
2. If multiple clocks are required, try to use 1 designer for all clock domains
3. When multi-clock design is required, plan for proper verification



During verification

1. Watch for multiple clocks in designs (*Tip – Count PLLs*)
2. Ask how CDC issues are mitigated (remember there are 3)



Utilize commercial tools designed for detecting these problems

1. Verify all 3 classes of CDC problems
 1. Structural Verification
 2. Protocols Verification
 3. Reconvergence Verification
2. Use reports to aid manual reviews
3. Use CDC tools to support ROBUSTNESS

In Conclusion ...

- **Every multi-clock design is subject to metastability**
- **Traditional verification methodologies CANNOT assure robustness**
- **To properly mitigate the dangers of CDC, we strongly recommend a solution that... :**
 - Supports Manual Reviews
 - *Automatically* reports all sources of CDC problems
 - Has a proven CDC verification methodology & customer success

The background is a deep blue with a complex pattern of glowing white lines that resemble circuit traces or data paths. These lines form various geometric shapes, including rectangles, circles, and spirals, creating a sense of depth and technological sophistication. The Mentor Graphics logo is centered in the upper half of the image.

Mentor Graphics®

www.mentor.com