

 
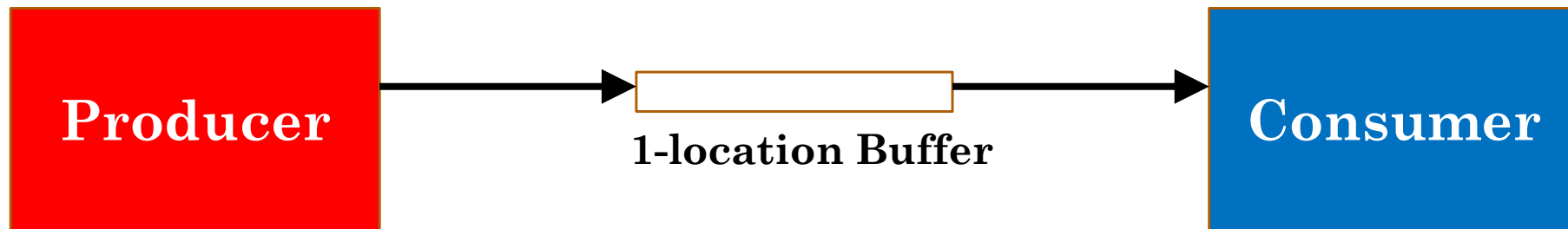


FIFO:

1-clock FIFO and 2-clock FIFO

 

 

A water tank delinks the pumping of water by the city and consumption of water by the residents.


In the same fashion a FIFO delinks the producer of data and the consumer of data by holding the excessive production in the FIFO.

FIFO

Delinks the producer and the consumer

PRODUCER


- Writer
- Deposits Data into the FIFO.

 


CONSUMER

- Reader
- Reads Data from the FIFO.


Data Plumbing:

 

 Matched flow schedules require no buffering



 Unmatched flow schedules require buffering



Capacitor on circuit boards




Connecting data with different bit-widths is like trying to drink water from a fire hose.


We need an adapter.

FIFOs with “aspect ratio” are used to go from, say, a 32-bit data producer to an 8-bit data consumer. Here, we are covering FIFOs with same size data.

 
Let us use an 8-location FIFO for our design example



 
- The FIFO has two pointers to denote the locations to write and read:
 - Write Pointer (WP): The location pointed to by the WP is where producer deposits data.
 - Read Pointer (RP): The location pointed to by the RP is from where consumer reads data.
- Initially the FIFO is empty. Both WP and RP point to location 0 of the FIFO.



 
Say the producer starts depositing the data.





 



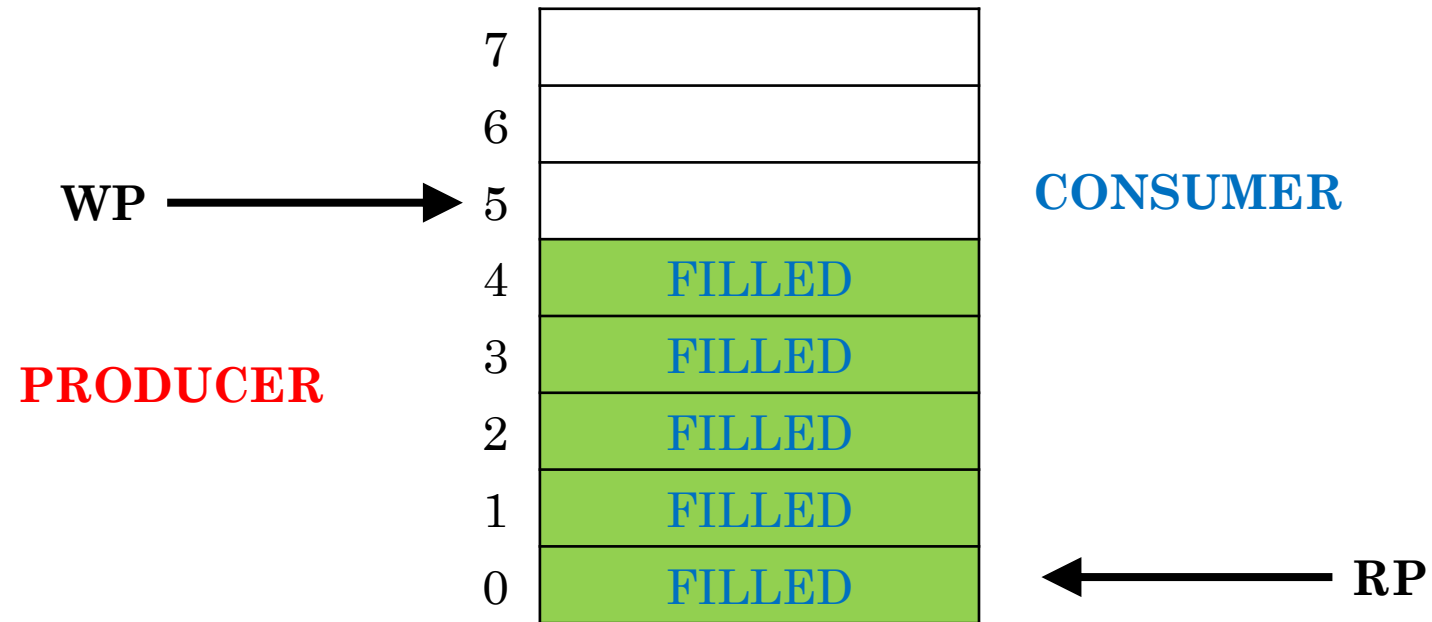

Now if the reader starts reading from this cycle.

Points to the location
to be written



WP



PRODUCER

7

6

5


4

3

2

1

0

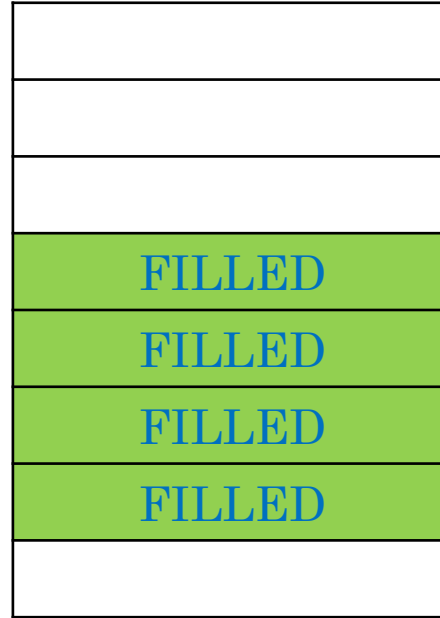


CONSUMER


RP




Points to the location
to be read



 


 

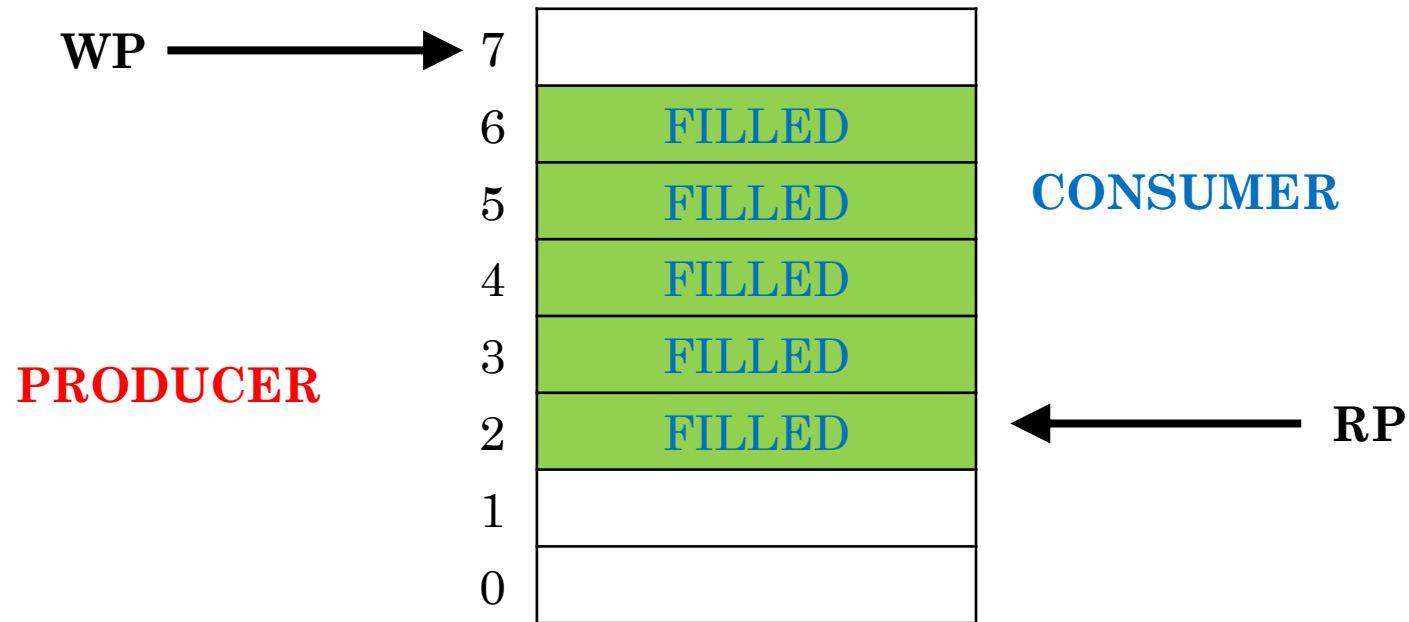

Now if we write to location 7, should the WP be incremented and be allowed to point to location 0?

FIFO (= a Circular Buffer)

 


Depth (i.e. # of filled locations) = WP - RP


Computing Depth (# of filled locations)

- Depth = $(WP - RP) \bmod 8$

 
FIFO Initially Empty
 $D = WP - RP = 0 - 0 = 0$



 
FIFO Depth = 4
 $D = WP - RP = 4 - 0 = 0$




 FIFO Depth = 1
 $D = WP - RP = 4 - 3 = 1$



 FIFO Depth = 7
 $D = WP - RP$
 $= (2 - 3)_{\bmod 8} = 7$



 

$WP - RP = 0$

- **EMPTY** (if most recently it was almost empty)
- **FULL** (if most recently it was almost full)

Example Thresholds for Almost Empty and Almost Full:

- Almost Empty if depth is less than or equal to 2
- Almost Full if depth is greater than or equal to 6

We need a flip-flop to record whether most recently it was running **almost empty** or **almost full**.

**Otherwise, when $WP=RP$ you can't tell
if the FIFO is Empty or Full!!**


FOR AN 8-LOCATION FIFO:

POSSIBLE DEPTH VALUES ARE 9 (NOT 8):

0, 1, 2, 3, 4, 5, 6, 7, 8

BUT $|WP - RP|_{MOD\ 8}$ EXPRESSION YIELDS ONLY 8 VALUES

0, 1, 2, 3, 4, 5, 6, 7

 

EMPTY

(If it was seen running
almost empty most recently)

FULL

(If it was seen running
almost full most recently)

MOD SUBTRACTOR

How do we design a MOD Subtractor?

We are all taught in our elementary school how to do subtraction but do you think subtractors are built using that very technique?

What is a posted-borrow subtraction?

MOD SUBTRACTOR

★ EXERCISE

A digital SUBTRACTOR uses a
POSTED BORROW Technique



$$\begin{array}{r}
 4 \ 0 \ 0 \ 2 \\
 -1 \ 2 \ 3 \ 4 \\
 \hline
 2 \ 7 \ 6 \ 8 \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 4 \ 0 \ 0 \ 2 \\
 -1 \ 2 \ 3 \ 4 \\
 \hline
 2 \ 7 \ 6 \ 8 \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 4 \ 0 \ 0 \ 2 \\
 -7 \ 2 \ 3 \ 4 \\
 \hline
 6 \ 7 \ 6 \ 8 \\
 \hline
 \end{array}$$

SUMMARY

An ordinary n-bit subtractor with its borrow output ignored is a Mod-2ⁿ subtractor.

MOD SUBTRACTOR

★ SOLUTION

A digital SUBTRACTOR uses a
POSTED BORROW Technique

$$\begin{array}{r}
 99 \\
 3\cancel{10}\cancel{10}10 \\
 \underline{402} \\
 -1234 \\
 \hline
 2768 \\
 \hline
 \end{array}$$

SUMMARY

An ordinary n-bit subtractor with its borrow output ignored is a Mod-2ⁿ subtractor.

$$\begin{array}{r}
 1010 \\
 -0-1-1-110 \\
 \underline{402} \\
 -1234 \\
 \hline
 2768 \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 101010 \\
 -1-1-110 \\
 \underline{402} \\
 -7234 \\
 \hline
 6768 \\
 \hline
 \end{array}$$

FIFO is like a queue:

Next Empty Slot
in the queue.
(Tail of the queue)

Similar to WP

WP




Senior-most person in
the queue
(Head of the queue)

Similar
to RP


RP

7	
6	
5	
4	FILLED
3	FILLED
2	FILLED
1	FILLED
0	FILLED

FIFO PIN-OUT

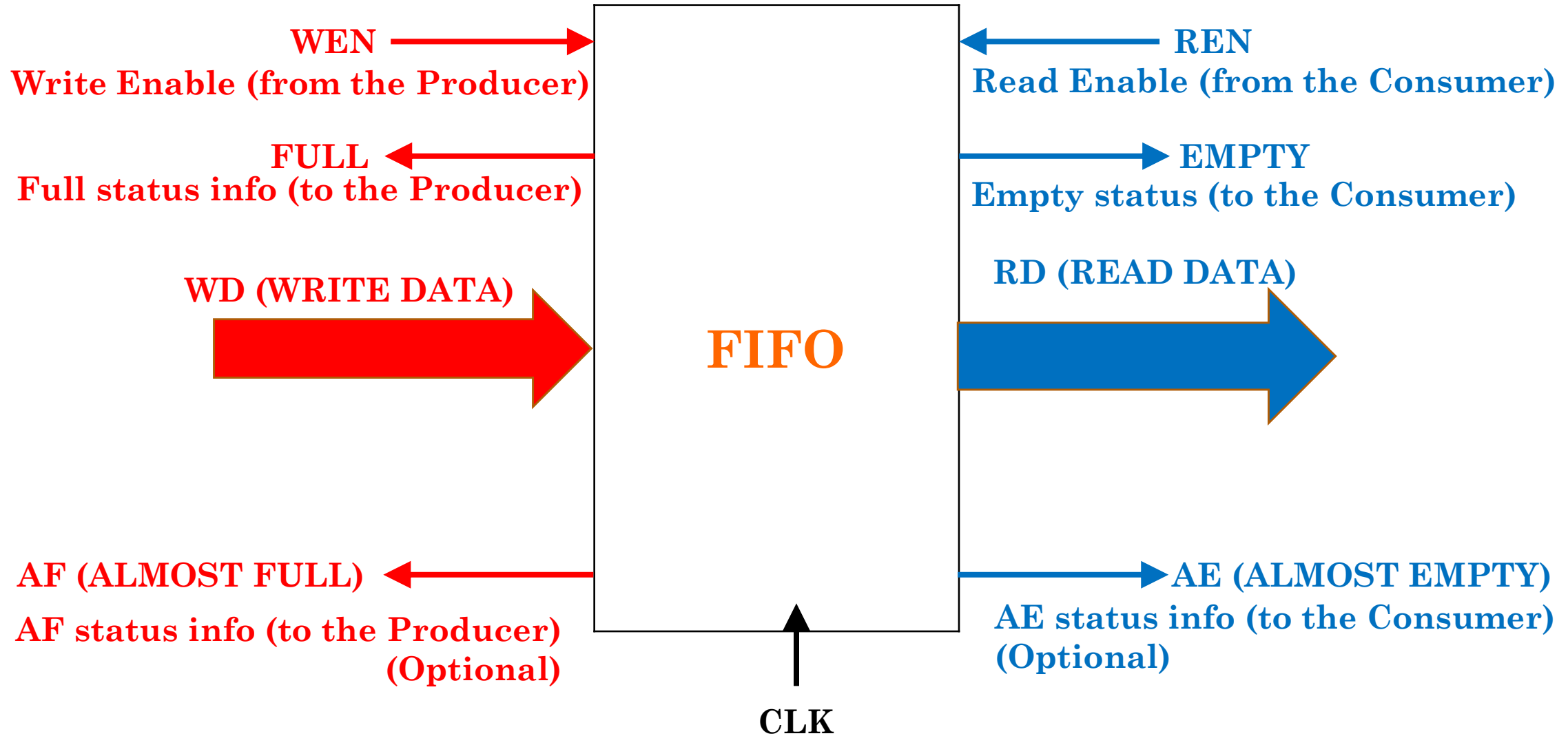

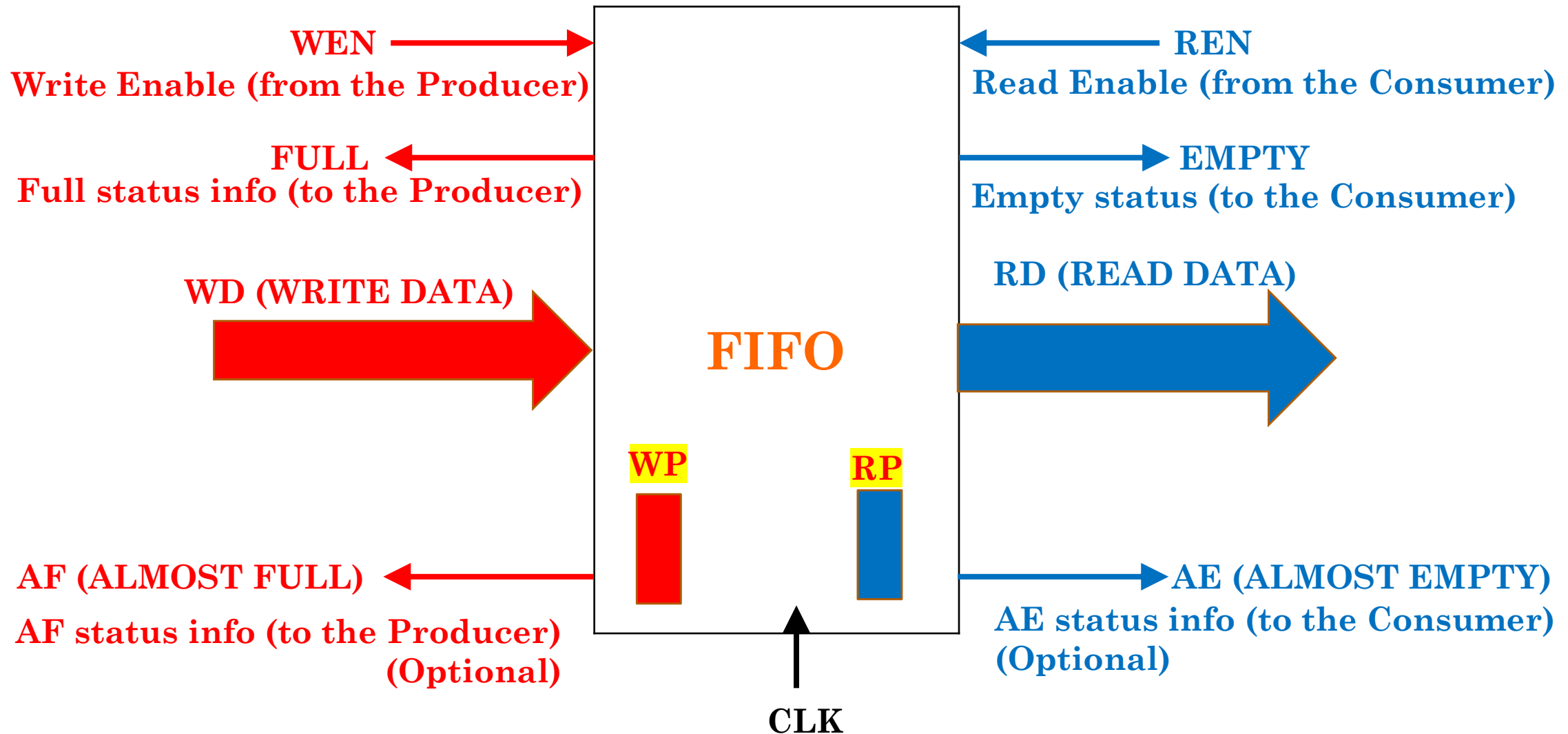Since the WP and RP are part of the FIFO, the FIFO PIN-OUT does not change if we change the FIFO depth from 8 locations to 8K locations!




DETAILED DESIGN OF A SINGLE-CLOCK 8X4 FIFO

We illustrate a detailed design using schematic components .

We use here


- an 8x4 register array for the FIFO storage,
- two 3-bit counters for the WP and RP pointers, and
- a 3-bit subtractor.

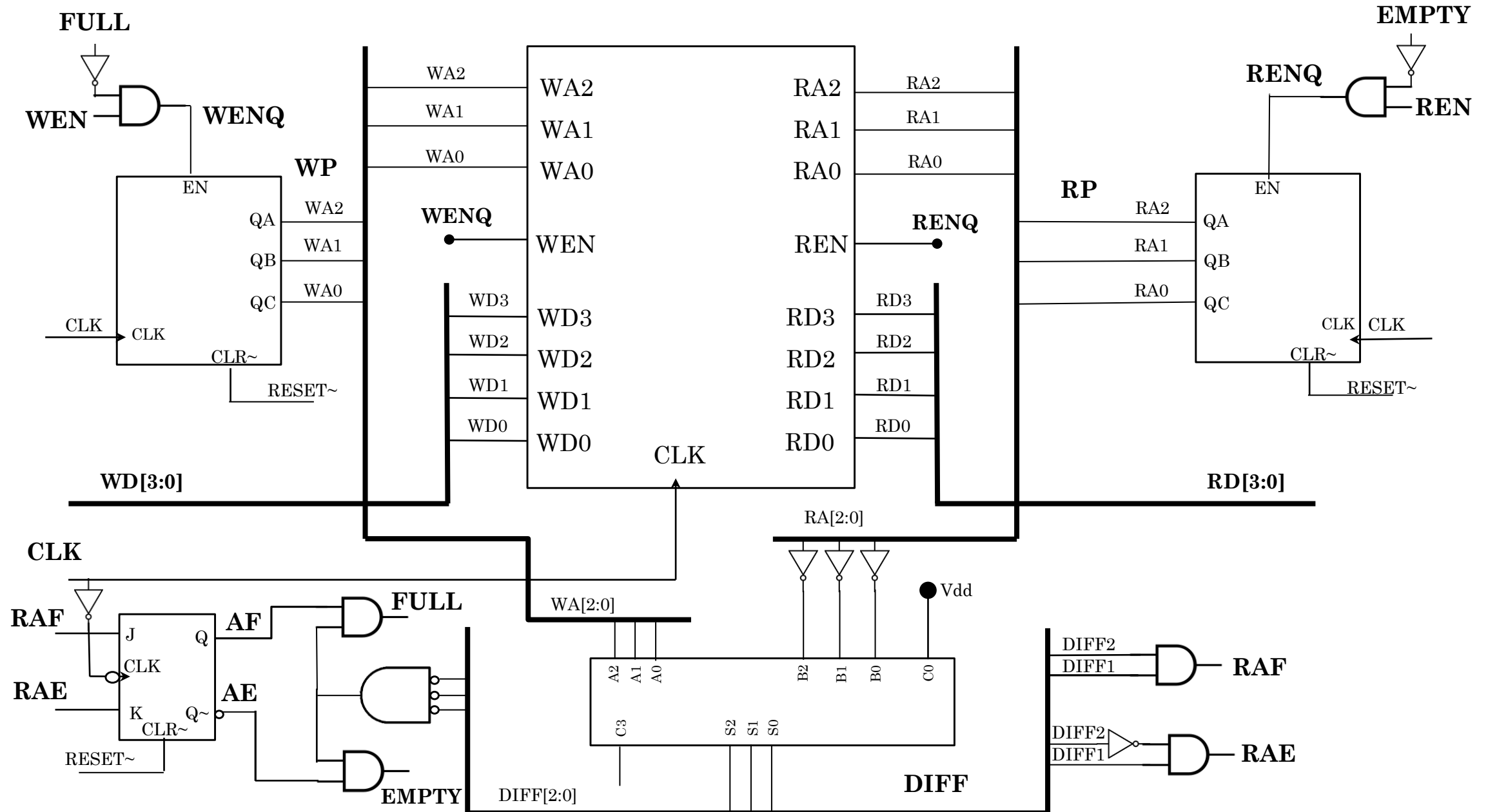Synchronous FIFO (Common clock for WRITE & READ)




FIFO Storage

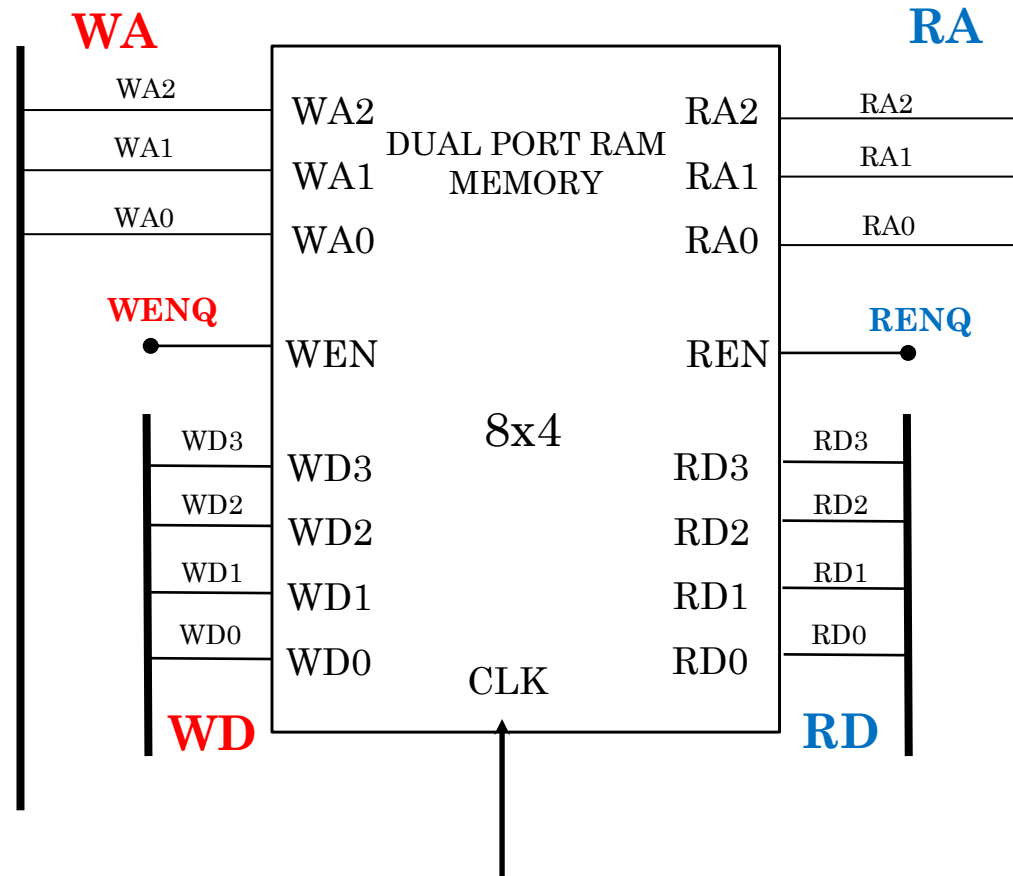Register Array acting as a Dual Port Memory
(a **write-only (WO)** port and a **read-only (RO)** port)




WP and RP pointers – when to increment them

WP

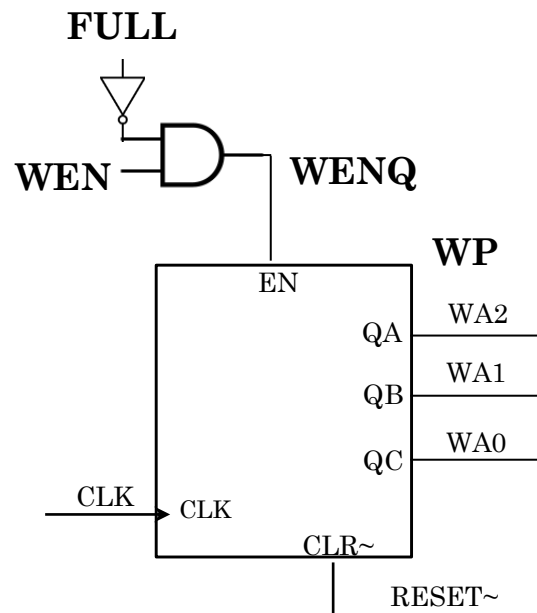

RP

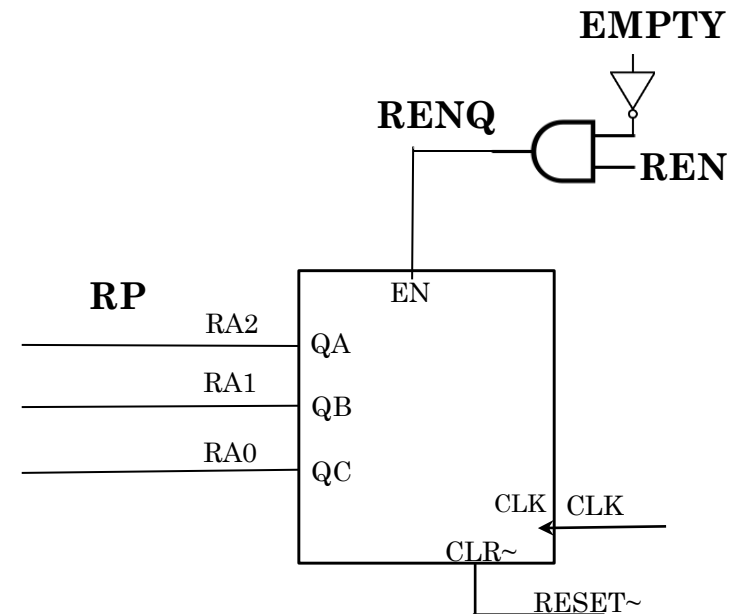


Computing Depth


A ripple carry adder turned into a subtractor

$$X - Y = X + Y' + 1$$
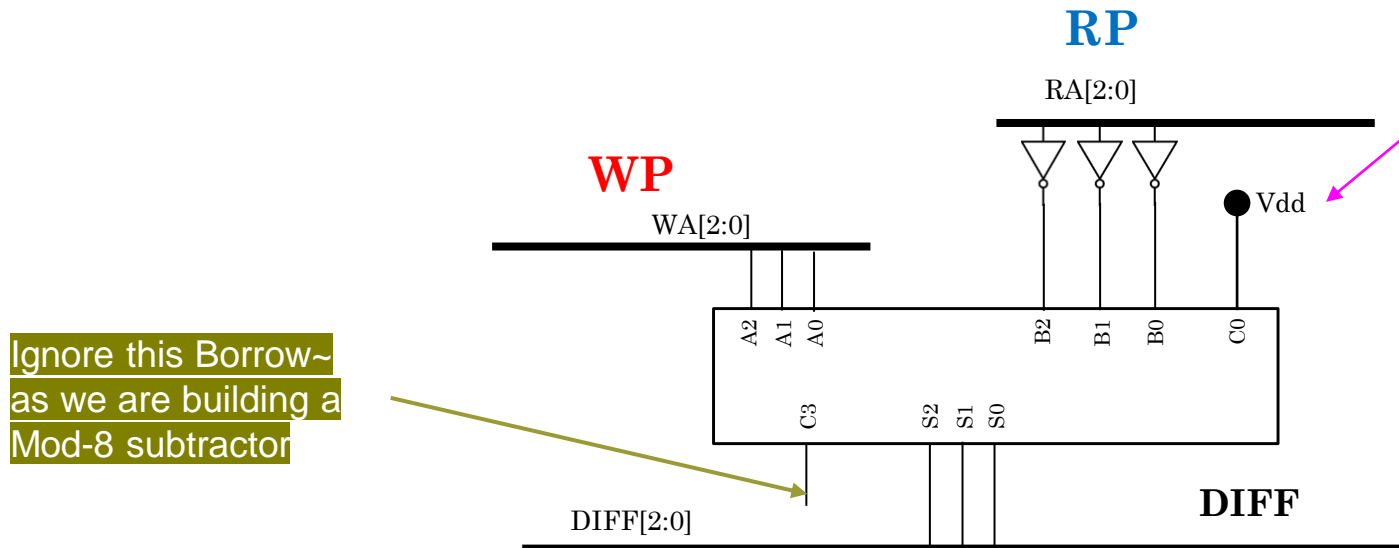
$$\text{WA}_2 \text{ WA}_1 \text{ WA}_0 - \text{RA}_2 \text{ RA}_1 \text{ RA}_0$$




RAF and RAE

 

Notice that “000” is excluded from activating **RAF** or **RAE**, as DIFF = 000 is the ambiguous situation that we are trying to disambiguate.


- We need to record (register) the RAF and RAE to form registered AF and registered AE.
- **AF = Almost Full = MRSAF =
Most Recently Seen the FIFO running Almost Full**
**AE = Almost Empty = MRSAE =
Most Recently Seen the FIFO running Almost Empty**
- We need a 2-state state machine, which can be implemented using either one FF (using the encoded state assignment method) or two FFs (using the one-hot coded state assignment method).

 The state diagram is the same irrespective of the implementation method.



Please notice that the FIFO may be half-full and it is possible that you had seen most recently the depth crossing (lingering around) the low-threshold or the high-threshold. This (in itself) does not create any ambiguous situation. We make use of AE/AF information when the ambiguous depth situation ($WP-RP = 0$) arises. Before the FIFO becomes FULL, it would be almost full a little before. Before the FIFO becomes empty, it would be almost empty a little before.

 By using a JK FF and the encoded state assignment method,
we can arrive at the NSL heuristically. It's very simple.
Just connect RAF to J and RAE to K.



N-bit pointers vs (N+1)-bit pointers

Another method [called the (n+1)-bit method] to remove (instead of solving) the ambiguity caused by $WP-RP=0$

- Instead of remembering whether most recently the depth was lingering around the almost empty threshold or the almost full threshold, in order to disambiguate the ambiguous situation caused by $WP-RP = 0$, we can avoid the ambiguous situation totally as follows.
- For the 8-location FIFO, we used 3-bit pointers for the WP and the RP. And the 3-bit subtraction $(WP-RP) \bmod 8$ produced an 8-valued result $[0, 1, 2, 3, 4, 5, 6, 7]$, where as the depth has nine values, namely $[0, 1, 2, 3, 4, 5, 6, 7, 8]$. This led to the ambiguous situation.
- Now suppose we deliberately use a 4-bit pointer for the WP and a 4-bit pointer for the RP. Then the 4-bit subtraction $(WP-RP) \bmod 16$, which can potentially produce 16 values (0-15), will produce all the 9 legal values (0-8) and will never produce the 7 illegal values (9 through 15). There is no ambiguity to be resolved now!

Mod_16 or Mod_8 for the 8-location FIFO?

- To understand the need to do mod_16 subtraction, consider a slow producer and a fast consumer. The consumer would wait for the producer to deposit one item and he would consume it in the very next clock. So, the WP would be one step ahead of the RP for just one clock. Most of the time the WP is equal to the RP. A few examples are given below.

WP = 1; RP = 0; WP-RP = 1 - 0 = 1;
WP = 1; RP = 1; WP-RP = 1 - 1 = 0;

WP = 5; RP = 4; WP-RP = 5 - 4 = 1;
WP = 5; RP = 5; WP-RP = 5 - 5 = 0;


WP = 8; RP = 7; WP-RP = 8 - 7 = 1;
WP = 8; RP = 8; WP-RP = 8 - 8 = 0;

WP = 13; RP = 12; WP-RP = 13 - 12 = 1; WP = 15; RP = 14; WP-RP = 15 - 14 = 1;
WP = 13; RP = 13; WP-RP = 13 - 13 = 0; WP = 15; RP = 15; WP-RP = 15 - 15 = 0;

WP = 0; RP = 15; WP-RP = 0 - 15 = -15; mod16 = 1;
WP = 0; RP = 0; WP-RP = 0 - 0 = 0;


Note! Hence, we need to perform mod 16.

WEN = Write Enable

 

WENQ = Write Enable Qualified
(Qualified by FULL=0)

REN = Read Enable

 

RENQ = Read Enable Qualified
(Qualified by EMPTY=0)

It looks like we the FIFO-designers, do not have faith in the producer designer and the consumer designer.

We provided the producer the FULL information. So, when he says "write" (by activating WEN), he must have checked to see that we are not running FULL.

Similarly, since we provided EMPTY information to the consumer designer, a responsible consumer designer would have checked to see that we are not running EMPTY before he tells us to "read" (by activating REN).

If so, why are we double-checking Full and EMPTY as shown above before activating WENQ and RENQ?

So, should we require that

the producer requests to write (makes $WEN=1$)
only after ascertaining that FIFO is not full
($FULL=0$)?

And similarly, should we require that

the consumer requests to read (makes $REN=1$)
only after ascertaining that the FIFO is not empty
($EMPTY=0$)?

YES and NO!!

YES and NO

CRITICAL PATH

At the beginning of a clock, DIFF is produced, and FULL & EMPTY are updated by the FIFO. This info is to be relayed to the PRODUCER and CONSUMER who will then activate WEN and REN. Let us try to avoid this round trip.

Because if FIFO is FULL it should not be written.
And if FIFO is EMPTY it should not be read.


Because we can do better in Timing Design.

Suggestion for a better timing outcome

The producer sends a request to write (WEN=1) if he has something to write without waiting to check to see if FULL=1. Later in the clock if he finds that FULL is true, he will **RETRY** to write the same data again.

LONG round Trip

★ EXERCISE

 


Two one-way SHORT Trips




LONG round Trip

★ SOLUTION

 


Two one-way SHORT Trips

 


CDC (Clock Domain Crossing)

 - Clock Domain Crossing (CDC) is a very common situation every digital designer encounters.
- On a mother board of a computer, you can easily find 4 to 10 different subsystems working on different clocks. Example: A processor may be working at 3 GHz, DDR4 at 1GHz, EPROM at 400MHz and the PCI Bus may be working at 66MHz etc.




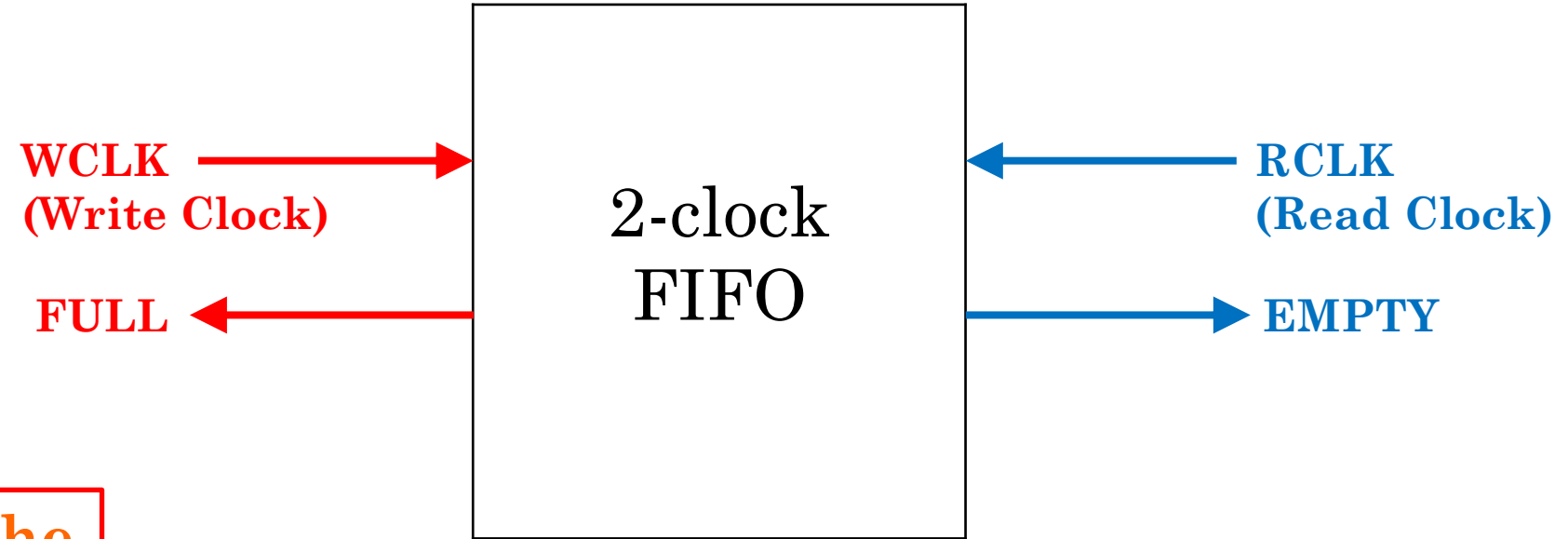- The **Robust** method of CDC is to use a 2-clock FIFO.




FIFO is used to bridge the separately clocked domains

An asynchronous FIFO = A two-Clock FIFO

 


Depth Calculation for 2-clock FIFO

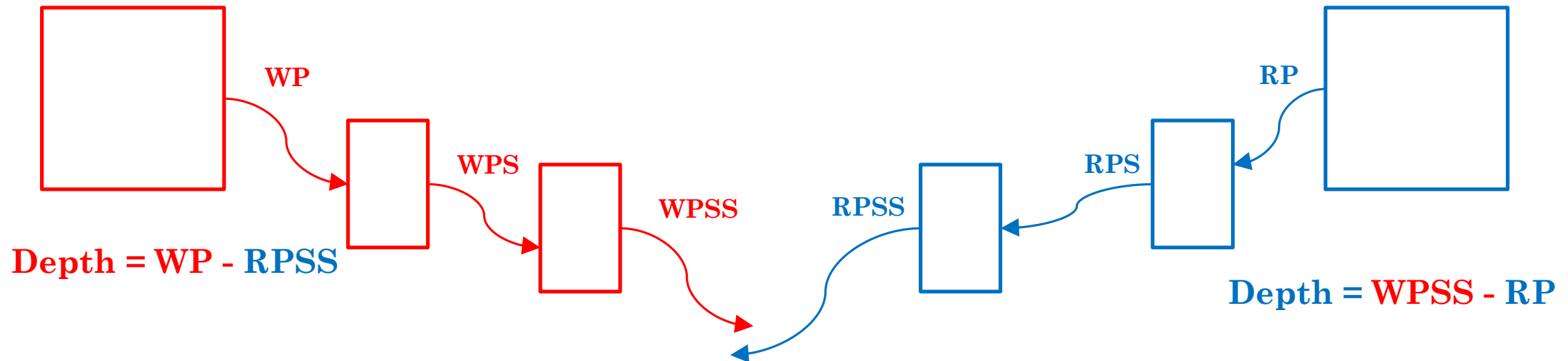We just can't do $(WP - RP)_{\text{mod } <\text{FIFO Depth}>}$ to generate depth value as they are generated in different clock domains. Also, we can't say when (even for a short moment) the WP and RP values are stable and valid together.




DELAY: Safe or Unsafe?

 
Never ever try to synchronize a multibit data item when you are crossing a clock domain



BAD IDEA!!

 

 For SEQUENTIALLY changing data such as **WP** and **RP** use
GRAY CODE




Since only 1-bit changes at most in **WP**, the **WPSS** will either be the **old WP** or the **new WP** and **will never be an absurd value!**

GRAY CODE:

0	0	0
		1
	1	1
1	1	0
		1
	0	1
		0

SYNCHRONIZATION using GRAY CODE

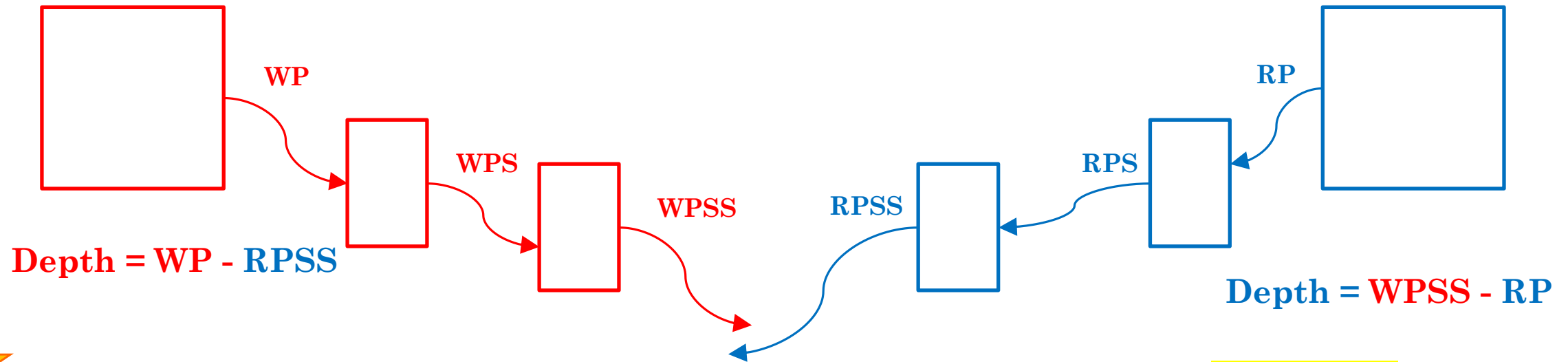

EXERCISE:

Try to write a similar paragraph for a faster writer.

DELAY: Safe or Unsafe? → Safe!!

Say the consumer is faster and the FIFO is running empty for a long time. Now the **WRITER** just wrote a data item



The incremented **WP** takes 1 or 2 clocks to reach the **Read Clock domain** and until that time the **reader** continues to believe that the FIFO is still **empty**.

So, he will delay **consuming** the data and this is safe! As long as the **consumer** does not **consume** from an **empty** FIFO, it is safe!

The (n+1)-bit pointer method for the 2-clock FIFO

On the next slide, we have an 8-location 2-clock FIFO with two 4-bit gray-code counters (WP_G and RP_G), two 4-bit binary counters (WP_Bin and RP_Bin), and two depth producing 4-bit subtractors (one in each of the two clock domains).

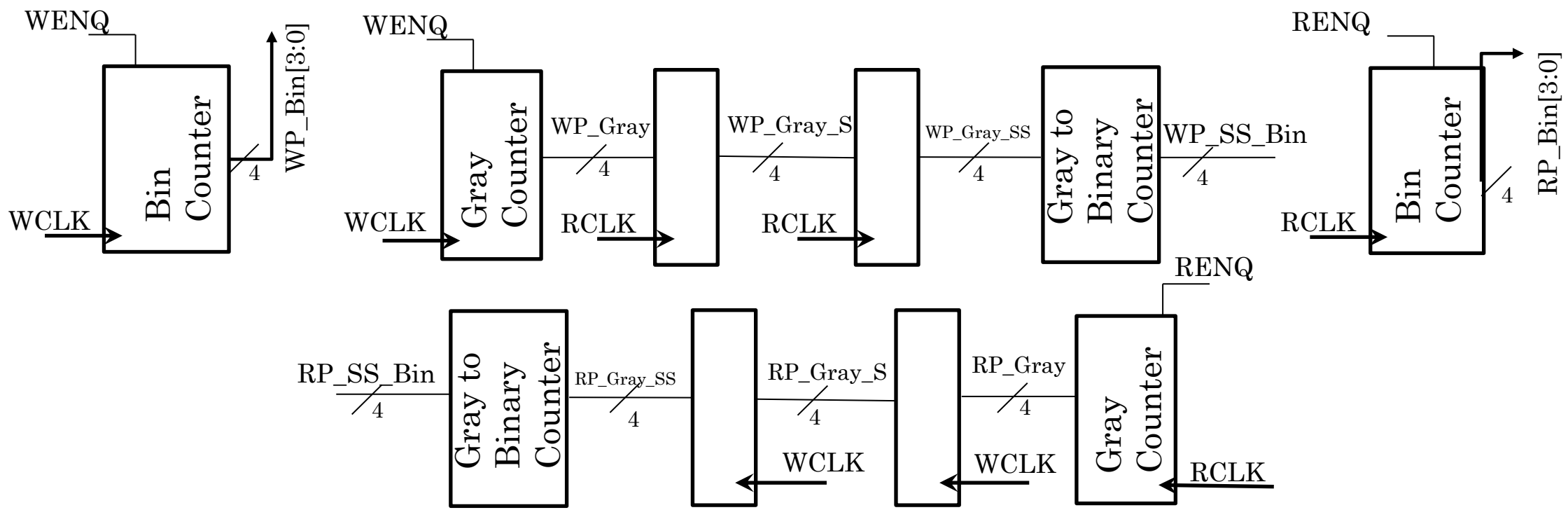
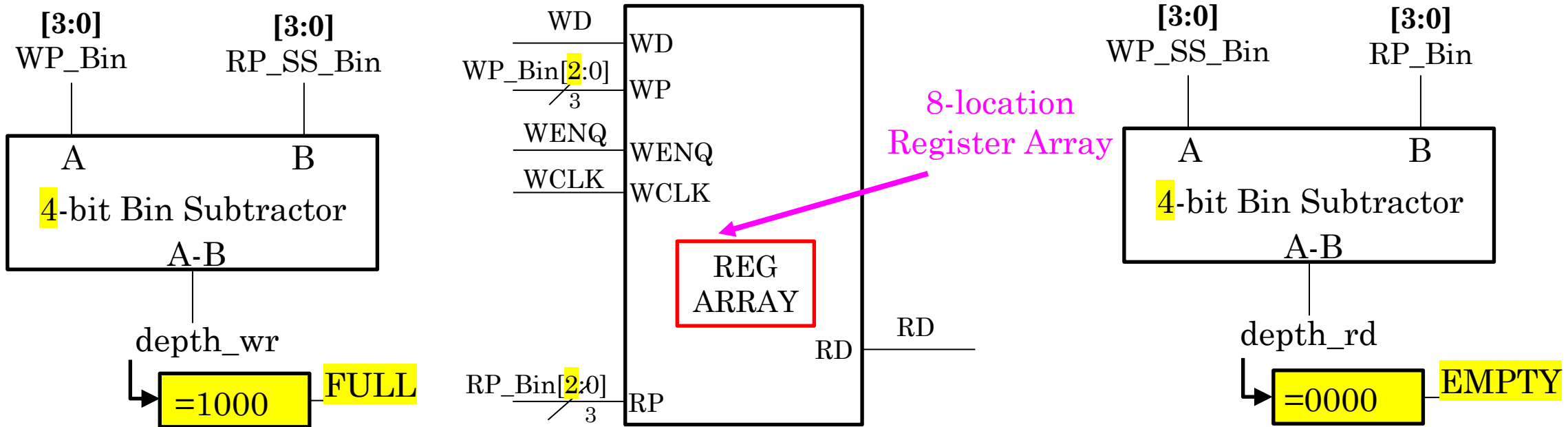
Note: The depth inferred in the write-clock domain (depth_wr) and the depth inferred in the read-clock domain (depth_rd) can differ substantially *tentatively* because of the lag in pointer exchange, but it is all on safe side!





A junior engineer offers an alternative design. He says he would change all the 4-bit items to 3-bit (i.e., the counters, synchronizing registers, code converters, subtractors, etc.). In each of the two clock domains, he will have a JK flip-flop (or something similar) to remember if most recently the FIFO was running almost empty (AE) or almost full (AF) and accordingly interpret a depth of 000 as zero (Empty) or eight (Full), like what was done in a single-clock FIFO.



He says that this is cheaper so why not use this alternative?

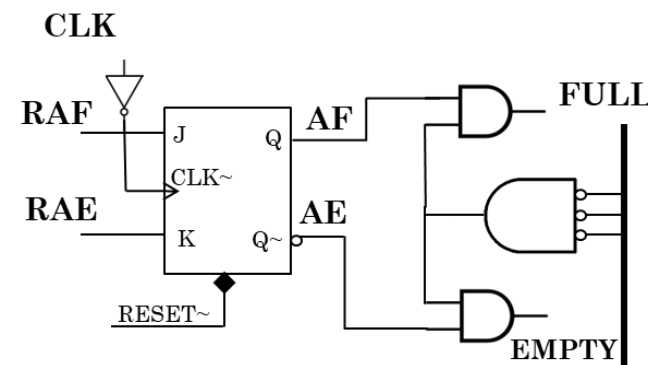 The junior engineer changed all [3:0] on the previous page to [2:0] as shown on the next slide and is about to add on each side one set of "JK FF and related circuitry" (Similar to the single clock FIFO).



  

8-location
Register Array

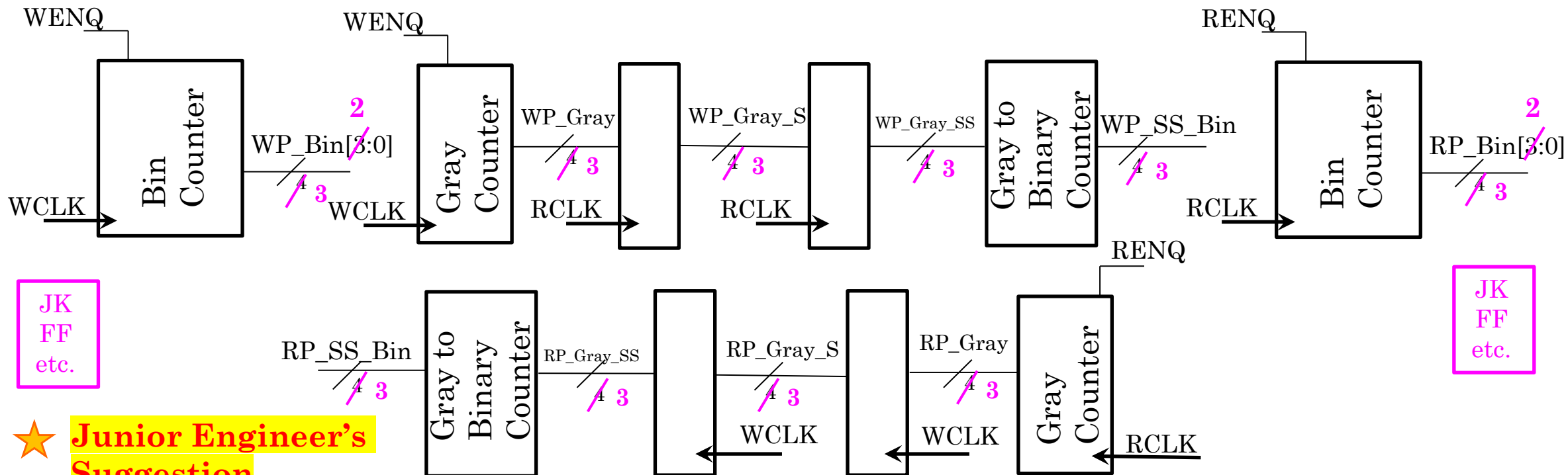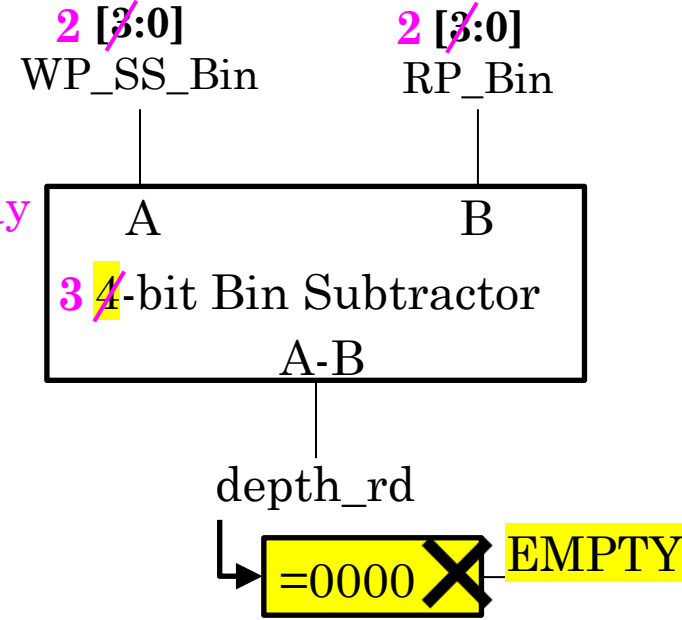


JK
FF
etc.

JK
FF
etc.

★ Junior Engineer's
Suggestion

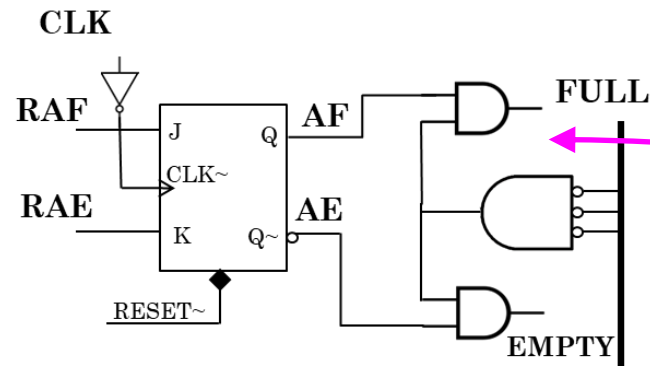The senior engineer told him not to do that as that would create a deadlock!



DON'T
DO
THIS

$WP - RP = 0$


→ EMPTY (if most recently it was almost empty)

→ FULL (if most recently it was almost full)


For a 2-clock FIFO, use the (n+1)-bit counter method only!

But WHY?! How can it cause a deadlock?


Say $F_{WCLK} \gg F_{RCLK}$

 

 - Consider the junior engineer's design with AE and AF.
- $AE == 1$ when $(WP - RP)_{\text{mod}8} = 2$
 $AF == 1$ when $(WP - RP)_{\text{mod}8} = 6$




WP →

 


- FIFO is initially empty.
 So $FULL = 0$ and $ALMOST_FULL = 0$;
 $EMPTY = 1$ and $ALMOST_EMPTY = 1$





← RP

 


 
- Suppose the producer starts writing the data after the 1st clock edge of WCLK for 8 consecutive clocks.




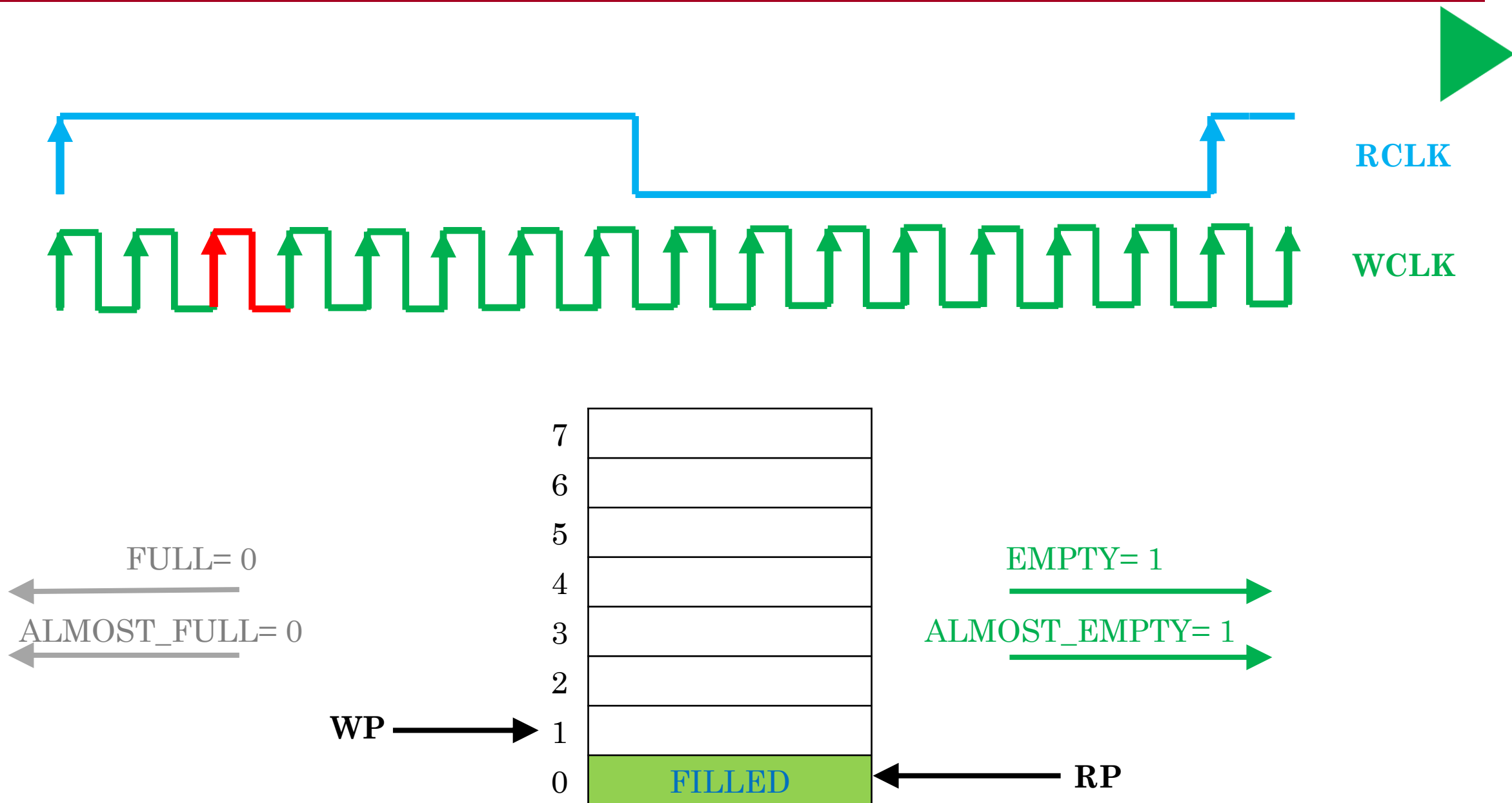


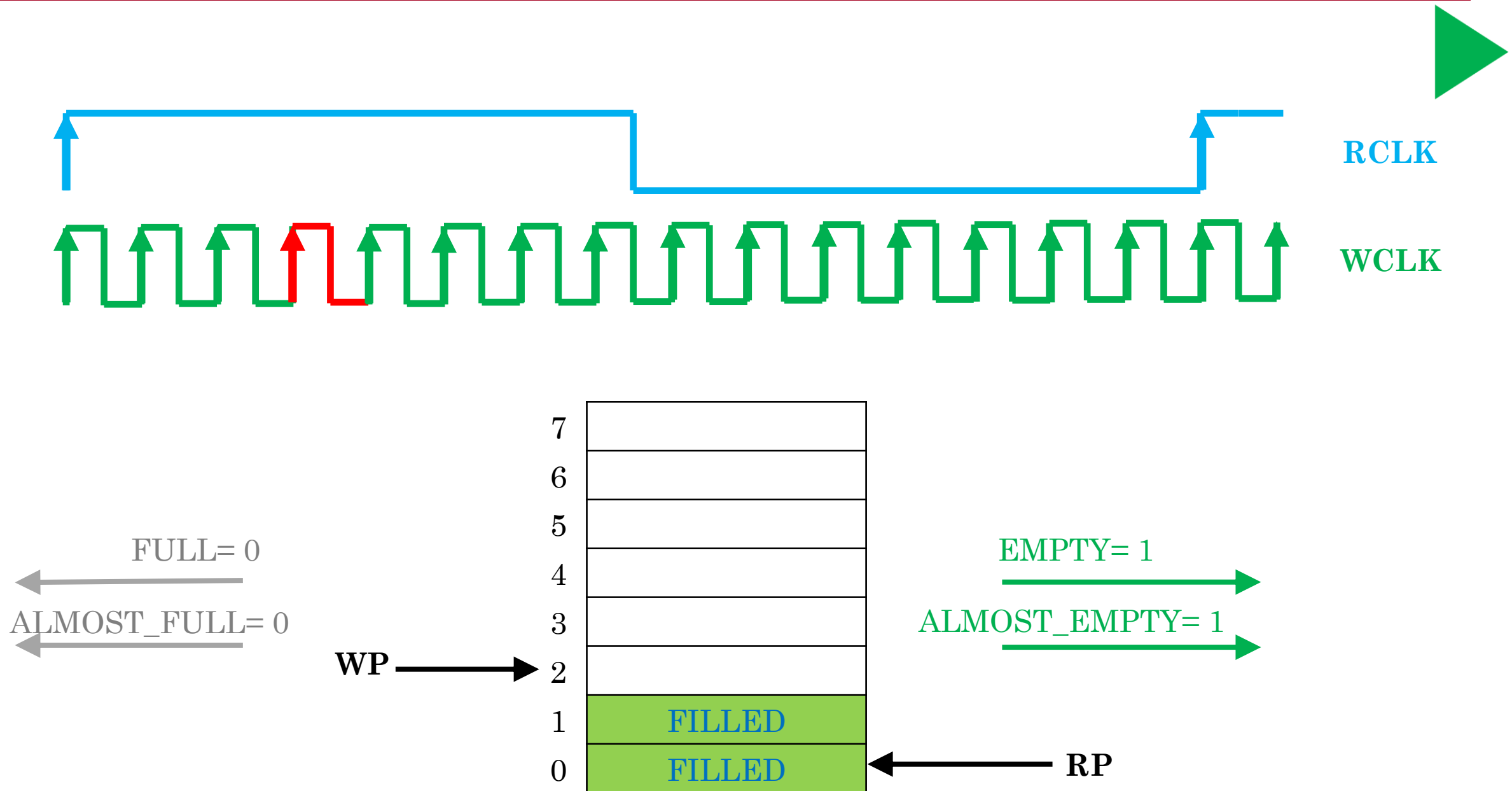

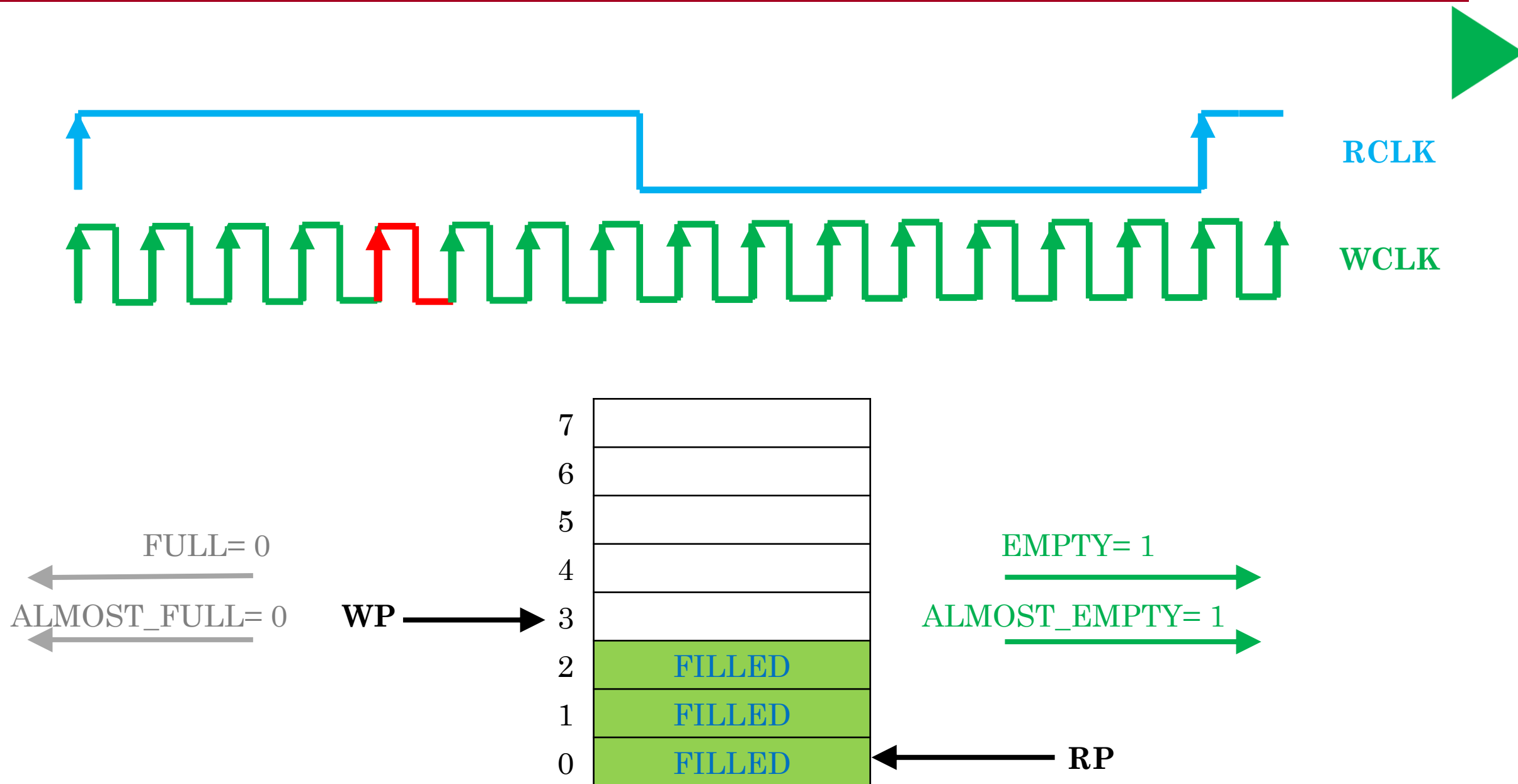


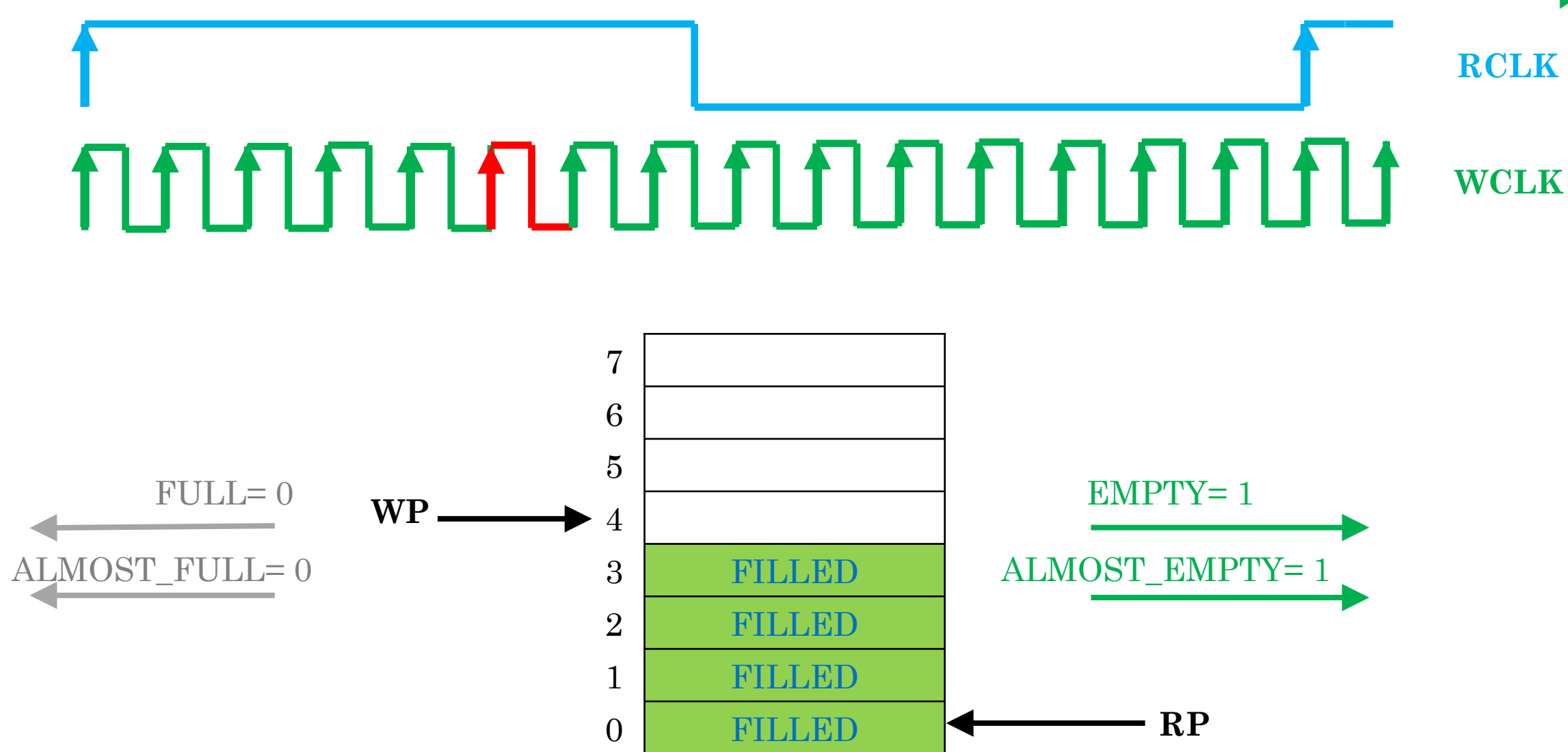


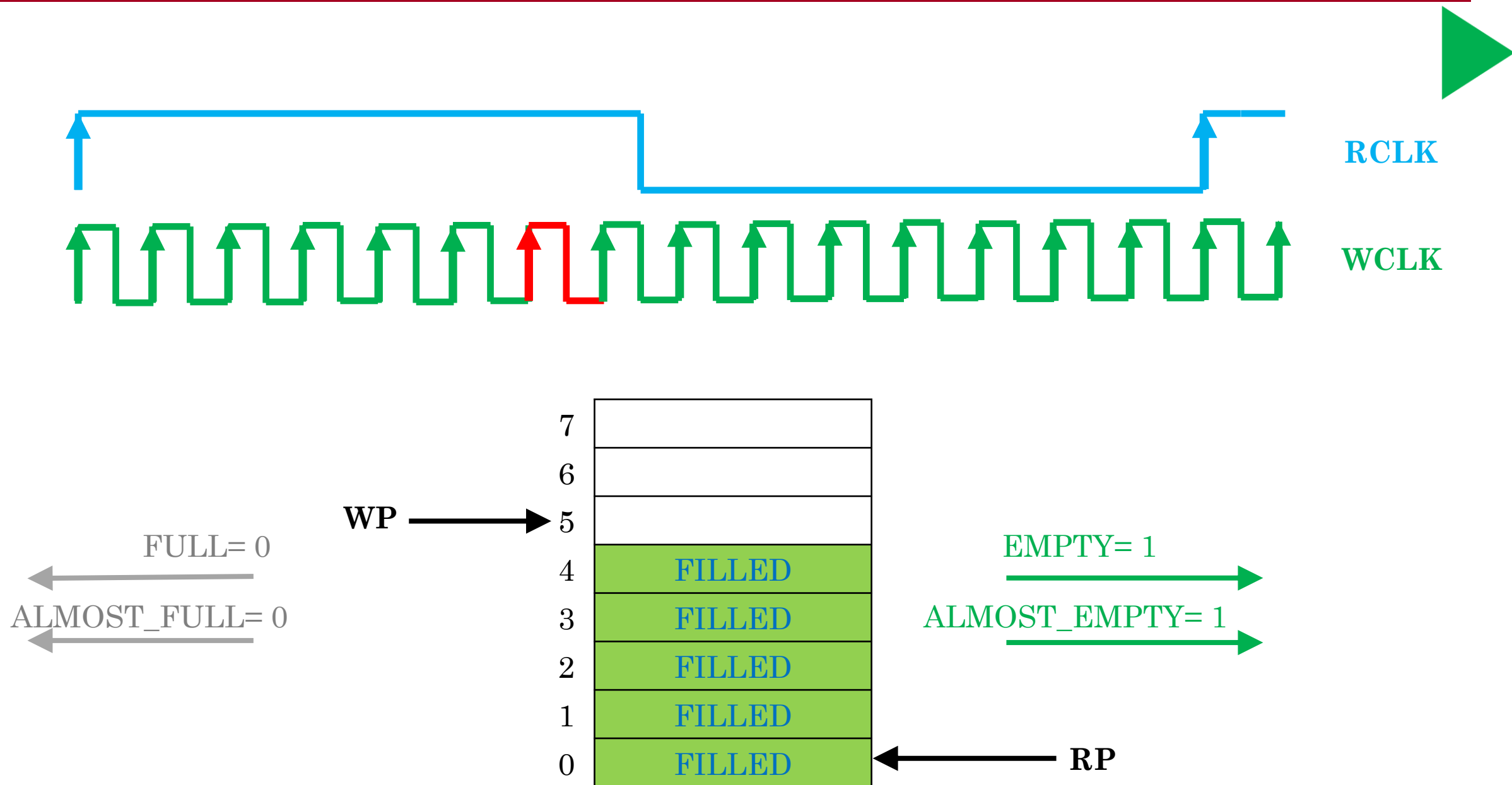


 


➤ $ALMOST_FULL=1$ as $WP-RP=6$

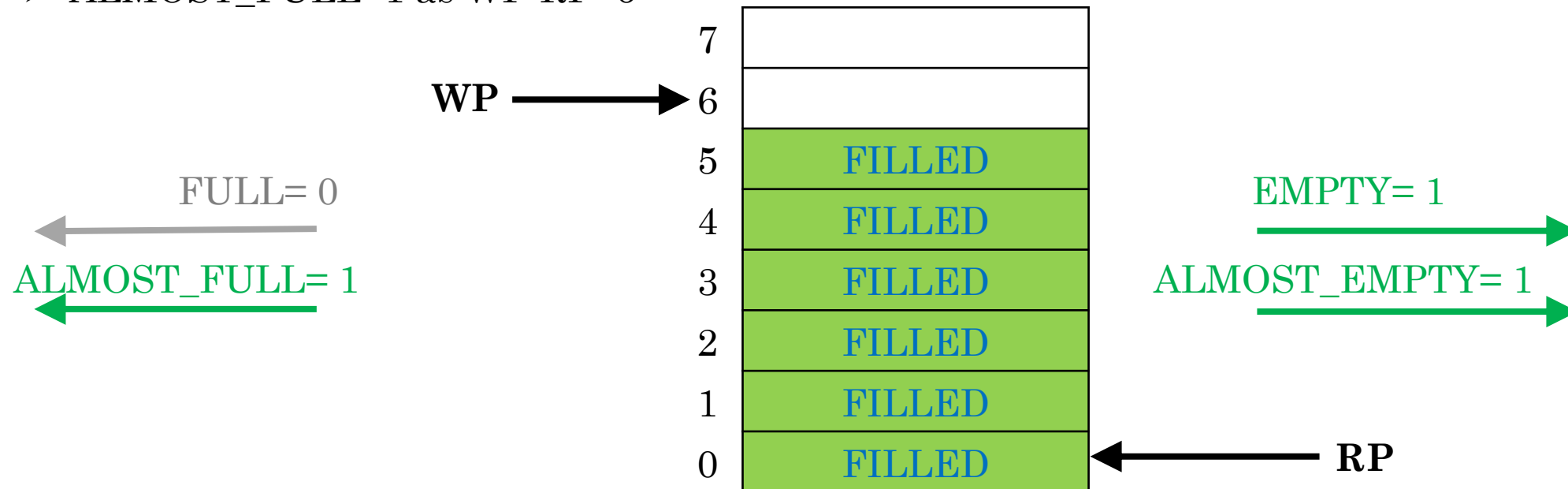

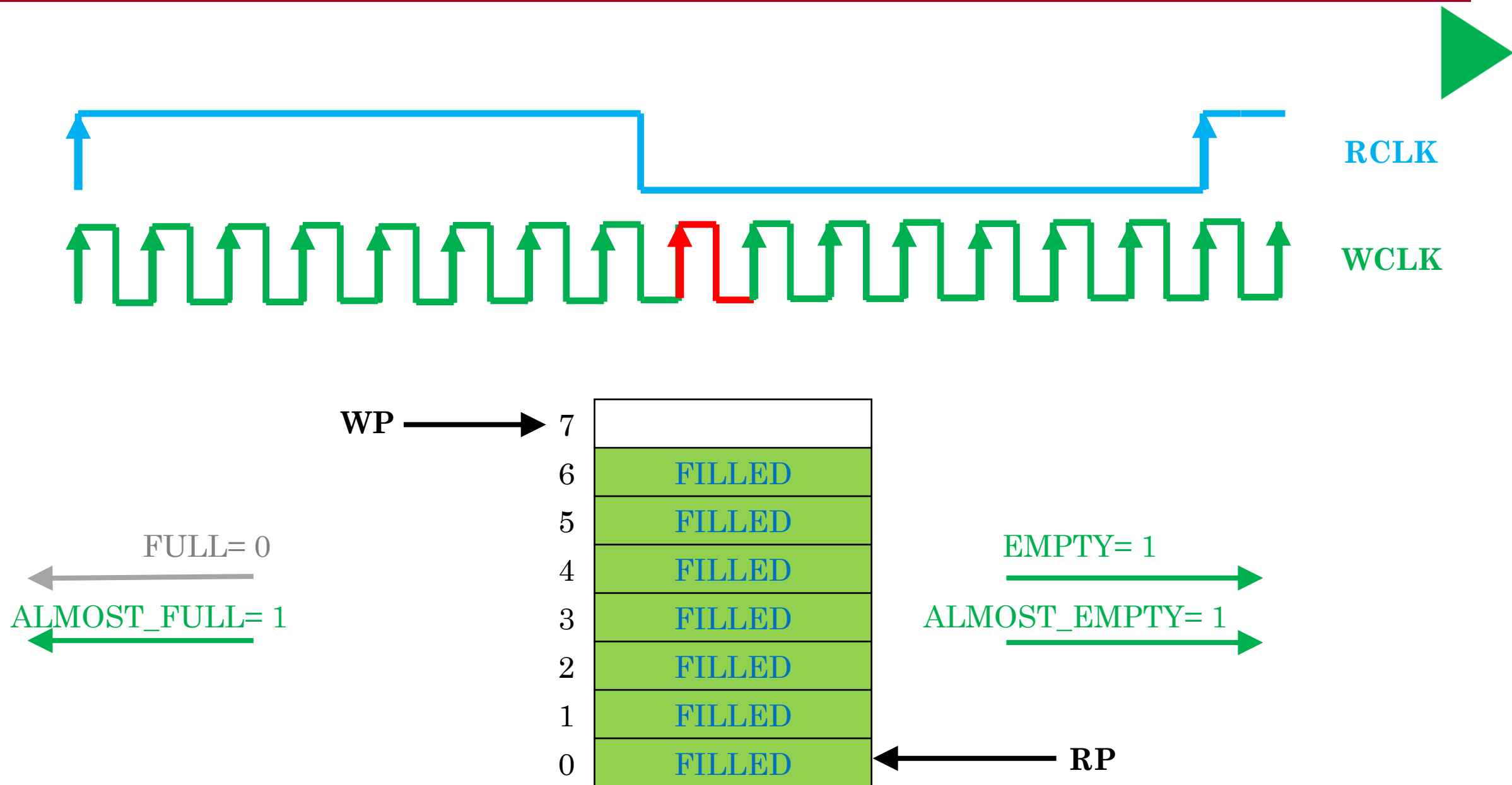


 

➤ FIFO becomes full.

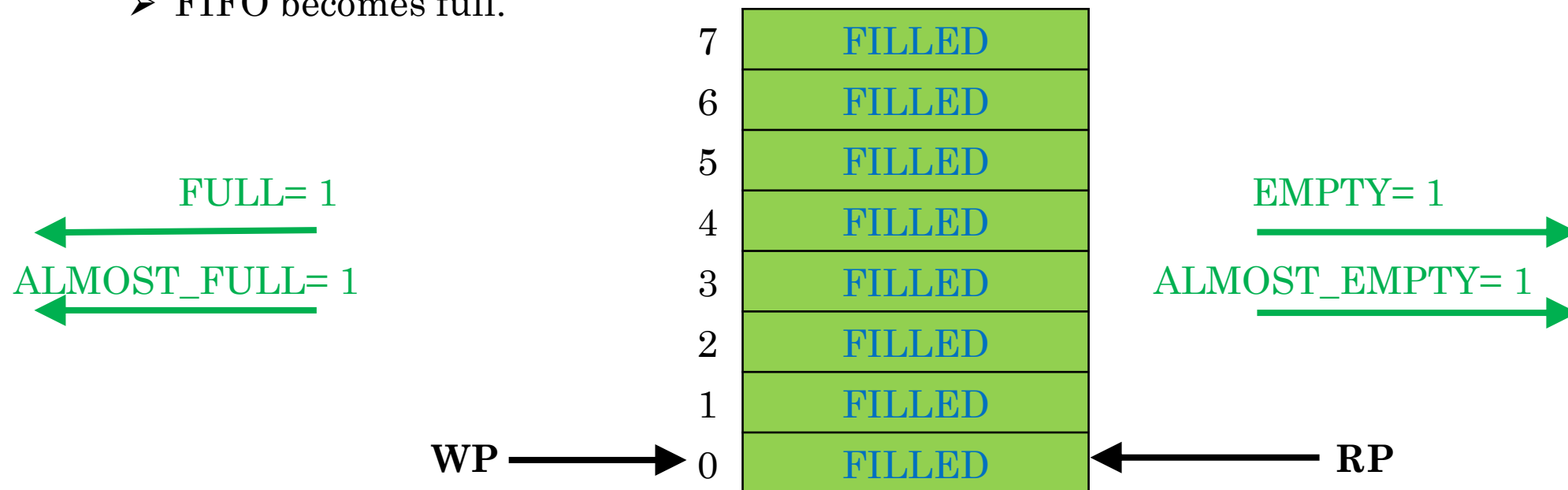


What happens here?!

 

The producer sees the AF and Full flag asserted. He infers that the FIFO is FULL because $(WP-RP)=0$ and $AF=1$. So, he wouldn't write into the FIFO any more. This is correct!

$FULL=1$
 $ALMOST_FULL=1$

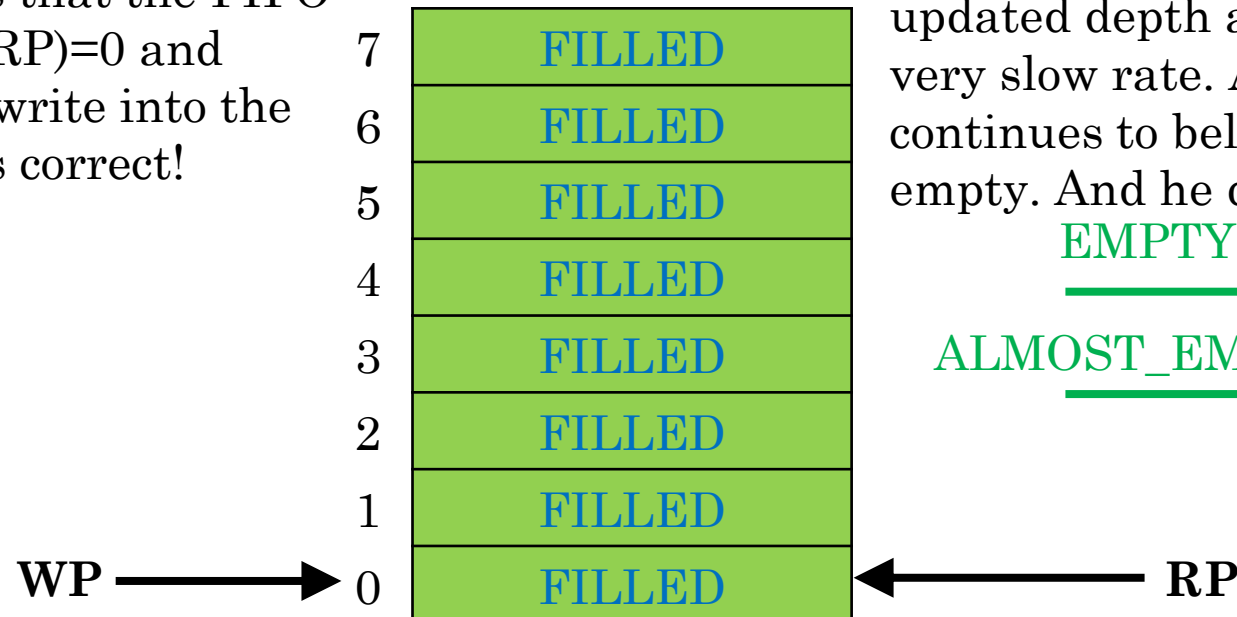

The consumer sees the old $(WP-RP)=0$ and doesn't see the updated WP or updated depth as he samples at a very slow rate. As a result, he continues to believe that the FIFO is empty. And he doesn't read either.

$EMPTY=1$
 $ALMOST_EMPTY=1$

This is a deadlock as both the Full flag and the Empty flag are high together and neither the producer nor the consumer is going to take a step!!

The vice versa holds true as well if $F_{RCLK} \gg F_{WCLK}$