

**IN3160 IN4160**

# Metastability and Clock domain crossing



In this course you will learn about the **design of advanced digital systems**. This includes programmable logic circuits, a hardware design language and system-on-chip design (processor, memory and logic on a chip). Lab assignments provide practical experience in how real design can be made.

*After completion of the course you will:*

- understand important principles for design and testing of digital systems
- **understand the relationship between behaviour and different construction criteria**
- be able to describe advanced digital systems at different levels of detail
- be able to perform simulation and synthesis of digital systems.

# Course Goals and Learning Outcome


<https://www.uio.no/studier/emner/matnat/ifi/IN3160/index-eng.html>

*Goals for this lesson:*

- be able to explain
  - how metastability occurs
  - how to deal with metastability in digital designs
- be able to calculate
  - error frequency for clock domain crossing
  - mean time between failure (MTBF) for brute force synchronizers
- know some common ways to safely transfer data between clock domains.
-


 
## Contamination & Propagation delay

- Contamination delay is the minimum time from the first input bit changes to the first output bit changes.
- Propagation delay is the time from the last input bit changes until the last output bit changes


  
# Flipflops, setup & hold

- A flipflop is 2 latches
  - EN on negated clock edge
- the input to the first latch must be ready before clock edge ( $T_{\text{setup}}$ )
- the first latch may become metastable even if the input changes shortly after the clock edge ( $T_{\text{hold}}$ )
- Transitions or metastability in the first latch will likely cause the second latch output to become metastable for an unpredictable amount of time before it settles at an arbitrary state.



# Clock domain crossing

- Two unsynchronized systems interchanging data, will cause metastability
- Random asynchronous signal into clocked domain:


$$P_{error} = \frac{t_s + t_h}{t_{clk2}} = f_{clk2}(t_s + t_h)$$

- For domain crossing:

$$f_{error} = f_{clk1} \cdot P_{error} = f_{clk1} \cdot f_{clk2}(t_s + t_h)$$

Ex: 25 MHz and 100MHz,  $t_s = t_h = 100ps$
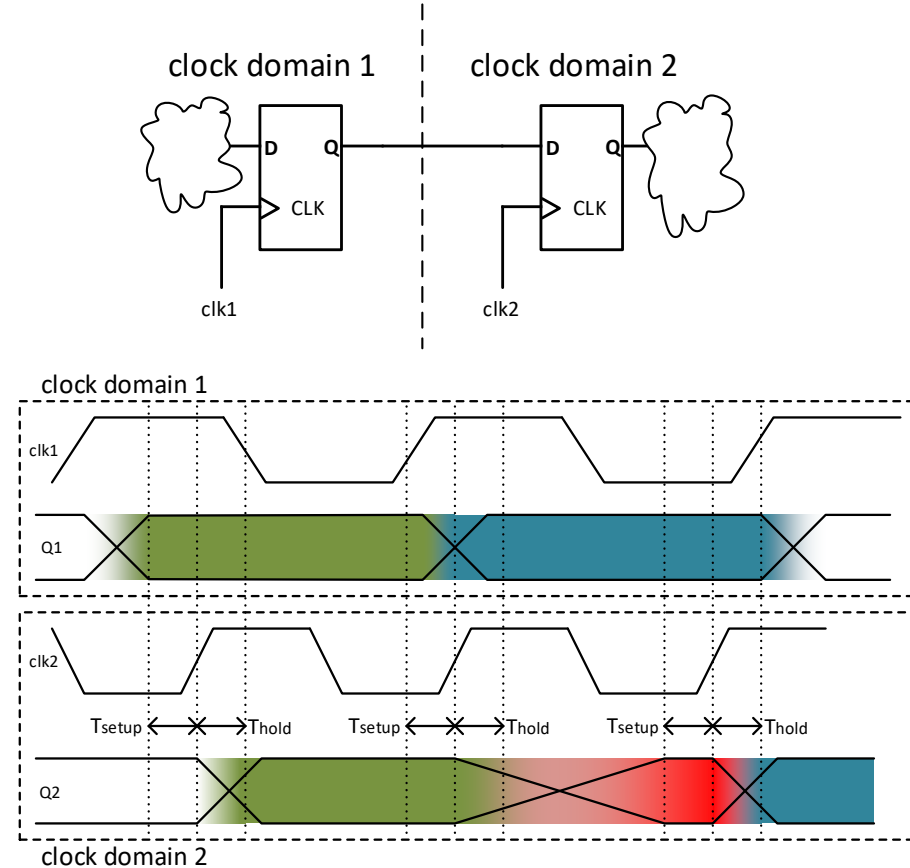
$$\begin{aligned} f_{error} &= 25MHz \cdot 100MHz \cdot (0.1 + 0.1)ns \\ &= 500 \cdot 10^3 Hz \\ &= 500kHz \end{aligned}$$





# Brute force synchronizer: Probability of stability ( $P_S = 1/P_U$ )

- The odds of an FF being unstable after waiting for a certain time window ( $t_w$ ) when metastable is given by the probability distribution function:

$$P_U = e^{\left(\frac{-t_w}{\tau_s}\right)}$$

  - $\tau_s$  is the time constant for the CMOS technology in use
  - $\tau_s$  is typically in the range of 100ps




Using a 100 MHz brute force synchronizer, with  $T_c = 200$  ps,  $\tau_s = T_s = T_h = 100$ ps we get

$$T_w = 10ns - (t_s + t_h) = 10ns - 200ps = 9.8ns \Rightarrow$$

The probability of failure is  $P_U = e^{\left(\frac{-9.8}{0.1}\right)} = e^{(-98)} = 2,7 \cdot 10^{-43}$

# MTBF in a brute force synchronizer

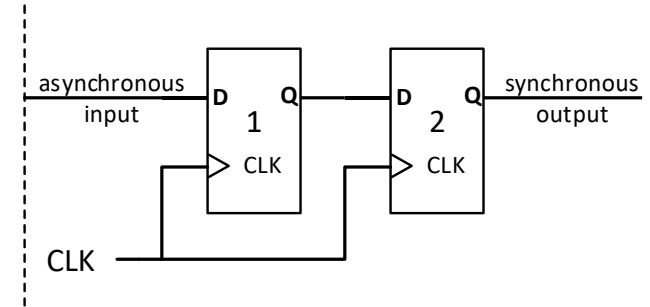


- Mean Time Between Failure (MTBF)  
=  $1/(\text{Metastability frequency})$ :

Metastability frequency = Prob. of failure \* error frequency  $\Rightarrow$

$$MTBF = \frac{1}{f_{error} \cdot P_U}$$

- MTBF for our 25-100 MHz clock domain crossing  
( $P_U = 2,0 \cdot 10^{-42}$ ,  $f_{error} = 500\text{kHz}$ ) becomes
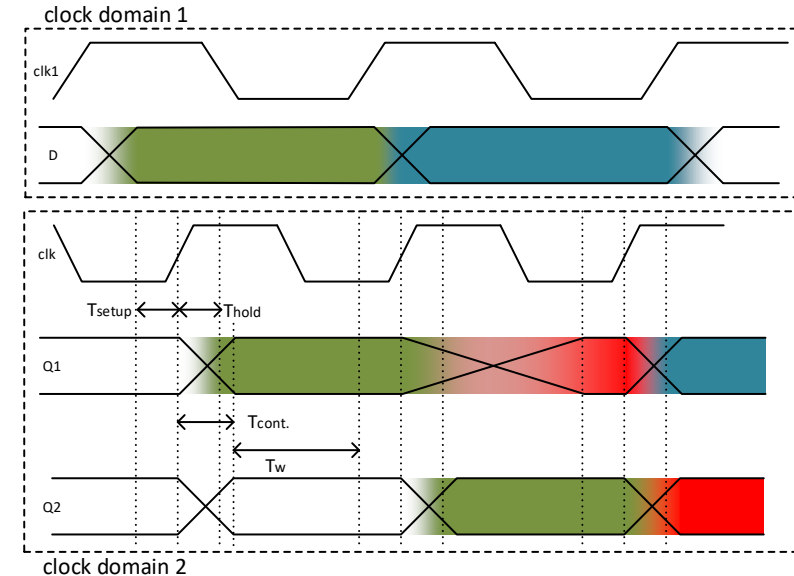
$$\frac{1}{2,7 \cdot 10^{-43} \cdot 500\text{kHz}} = 7,3 \cdot 10^{39}\text{s} = 2,3 \cdot 10^{32}\text{years}$$





# Summary

- $f_{error} = f_{clk1} \cdot P_{error} = f_{clk1} \cdot f_{clk2}(t_s + t_h)$ 
  - Der  $P_{error} = \frac{t_s + t_h}{t_{clk2}} = f_{clk2}(t_s + t_h)$
- $P_U = e^{\left(\frac{-t_w}{\tau_s}\right)}$ 
  - $T_w = T_{cycle} - (t_{hold} + t_{setup})$ 
    - $T_{cycle} = \frac{1}{f_{clk2}}$ ,  $\tau_s$  -tidskonstanten er teknologiavhengig
- $MTBF = \frac{1}{f_{error} \cdot P_U}$
- Note: we assume  $f_{clk2} > f_{clk1}$

Domain 1

Domain 2

 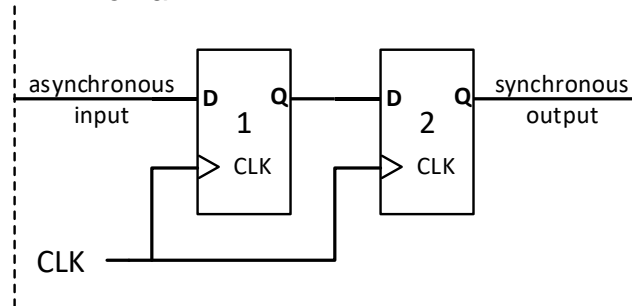



## Brute force synchronizer

- The goal is to avoid propagating metastability
  - It is not to ensure correct data
  - brute force synchronizer ensures longest possible settling time
- Can not be used for multiple bits...
  - metastability ensures data arrives at different clock edges
- ... unless data is sent using Gray code.
  - only one data bit changes at a time

## How to ensure data travels safely between clock domains

- Handshake (only using brute force on control signal)
- Use of FIFOs ()

**INF3430 / 4431**

## **Metastability**

Synchronization of n-bit data bus

Convergence and divergence in CDC path





# Outline


- Multiplexer-based and enable synchronizer
- Handshake synchronizer
- FIFO synchronizer
- Memory synchronizer
- Example design with enable synchronizer
- Convergence and divergence in CDC
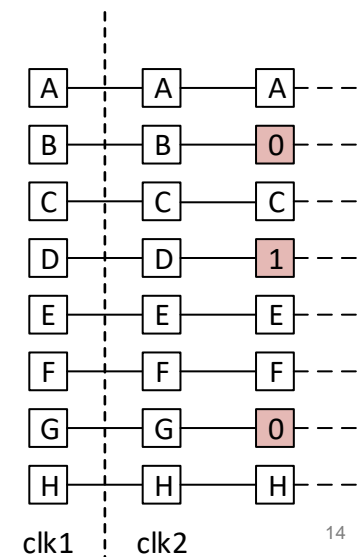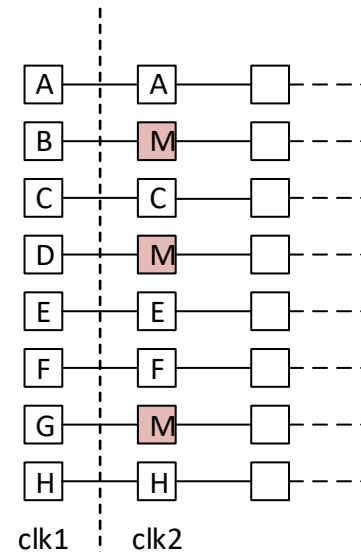
## The N-bit problem

- 2DFF (double flopping) synchronizer used to synchronize data wider than 1-bit may lead to functional error.
  - (Some bits arrive before others)
- Synchronizers based on:
  - Multiplexer or enable signal
  - Handshake
  - FIFO



## ***Multiplexer-based Synchronizer***

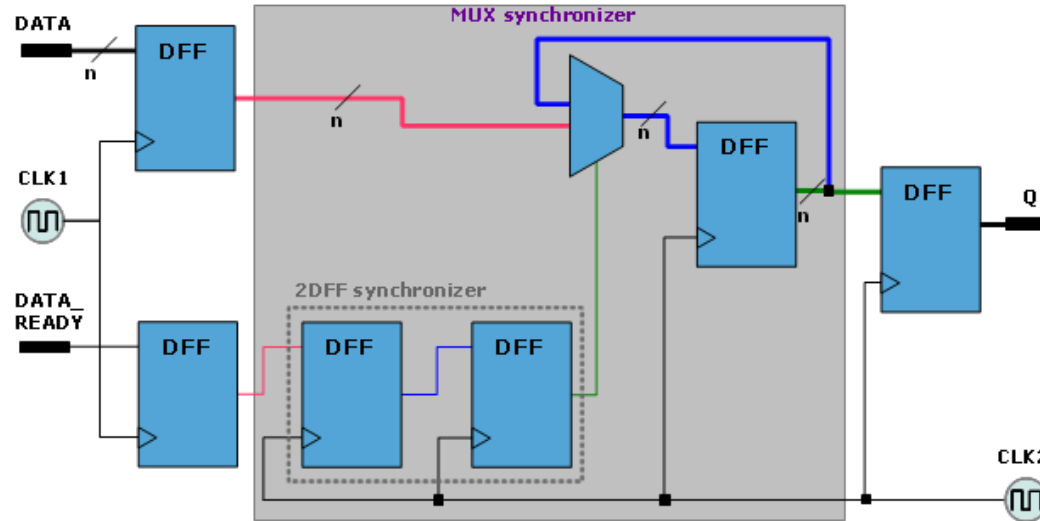


"DATA\_READY" from the source domain is synchronized using a 2DFF synchronizer. Then the synchronized control signal enables the select pin of the multiplexer.

"DATA\_READY" arrives with a delay which is sufficient for the data to get stable, it signals to the multiplexer that the "DATA" is ready to be transferred to the destination domain.

The source domain *must* keep the data constant when the "DATA\_READY" signal is active.

## Enable Synchronizer

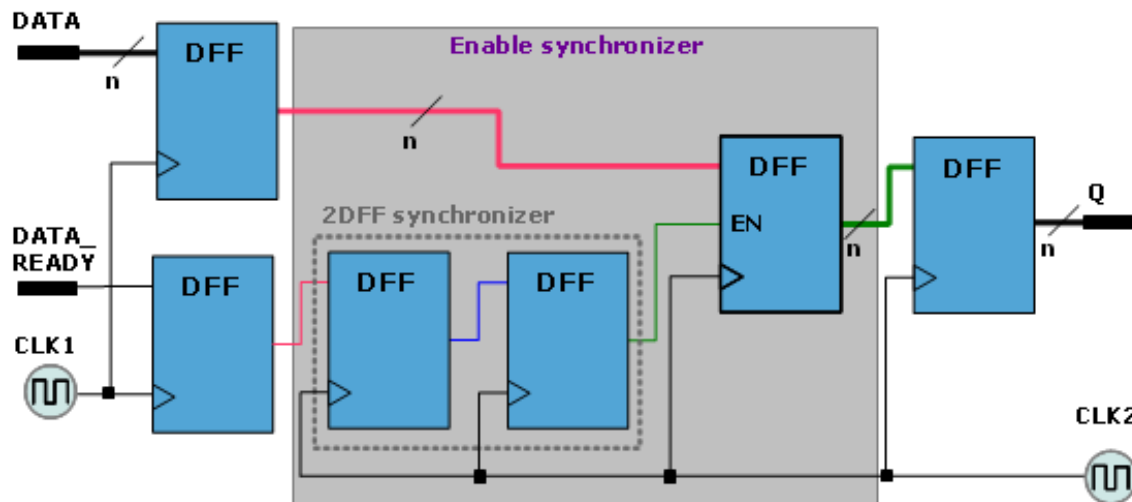

In the enable scheme a control signal "DATA\_READY" from the source domain is synchronized using a 2DFF synchronizer.

Then the synchronized control signal drives the enable pin of the first flip-flop of the destination domain.



This is essentially the same solution as the previous, using built-in ENABLE multiplexer in each DFF rather than an external

# Design Principles

- Both synchronizers follow essential principles:
  - The select input of the MUX or enable input should be driven by the synchronized control signal (from a destination domain). This input should be driven by the destination domain.
  - The other input (i.e. the n-bit data) should be a static signal from a source domain or user-specified.
- Using of such synchronizers allows to control the data transfer for all bits of the bus (individual bits of the data bus are not synchronized separately), that in turn allows to ensure that there is no data incoherency.



# Handshake Synchronizer

 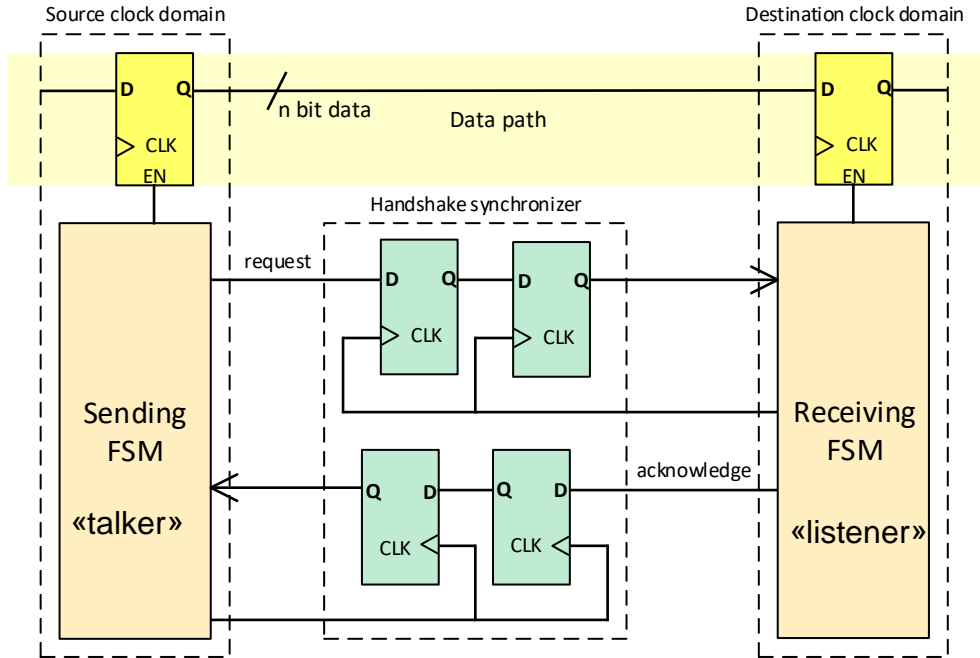


When data are available (start):

1. The talker asserts the request signal
2. When the request signal is synchronized by the listener
  - It asserts enable and acknowledge when the synchronized request signal arrives
3. When the talker receives the synchronized acknowledge signal
  - It deasserts the request signal and waits until it is deasserted
4. The listener deasserts acknowledge when it receives the deasserted request
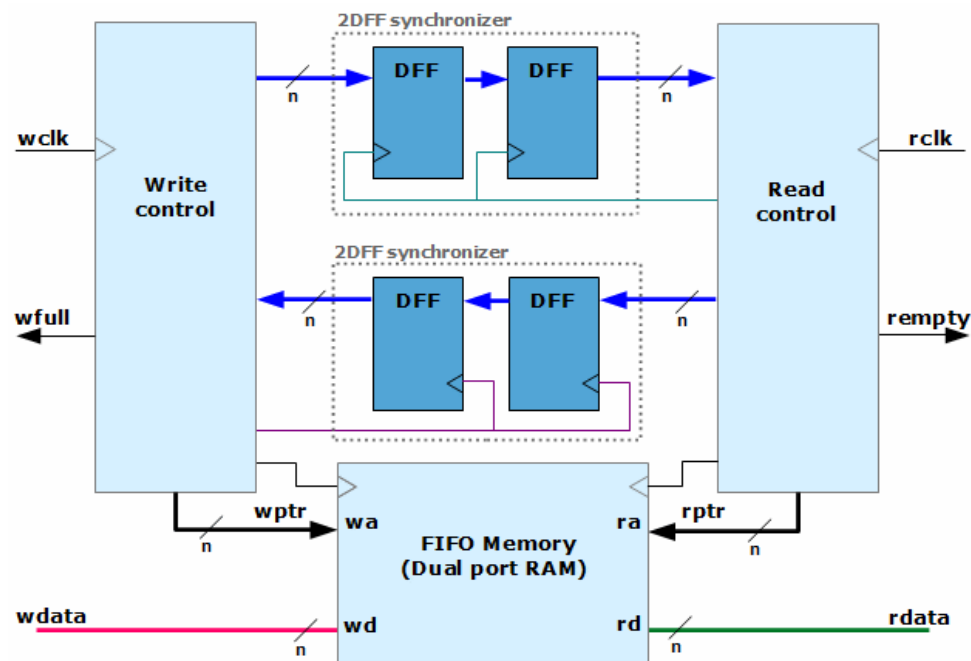
# FIFO Synchronizer


When the handshake synchronization cannot be applied, FIFO synchronizer may be used.

- Faster, burst type sending
- multiple signals are passed between clock domains;
- gray code counters are used to detect full and empty state;
- signals released by these counters are synchronized via 2DFF synchronizers;
- the read and write pointers are passed to the corresponding address pins of the FIFO;
- the producing clock-domain logic never writes when the FIFO is full;
- the receiving clock-domain logic never reads when the FIFO is empty.



 
# First In First Out (FIFO) synchronizer

- FIFO is clocked by both sides...
  - Details on next slide(s)
- ...Either side can have the fastest clock period
  - within the FIFO capabilities
- Data is buffered in a dual port RAM
  - Enables burst read and write
  - The FIFO maintains pointers to the data
- More complex than a simple handshake
  - Details on next slide(s)
- Large buffers may be less suitable for real-time data
  - Small FIFOs can be useful...



 
## Unwrapping the FIFO synchronizer: *Dual port RAM*

- RAM is asynchronous..
  - Data is latched, not FlipFlop'ed
  - Read and write can be done simultaneously...
    - Data should not be changed while being read
  - The FIFO makes sure..
    - Separate read- and write- address-pointers are used
      - Ensures data out is stable
    - Writing cannot be done if the RAM is full
    - Reading is prohibited if the RAM is empty


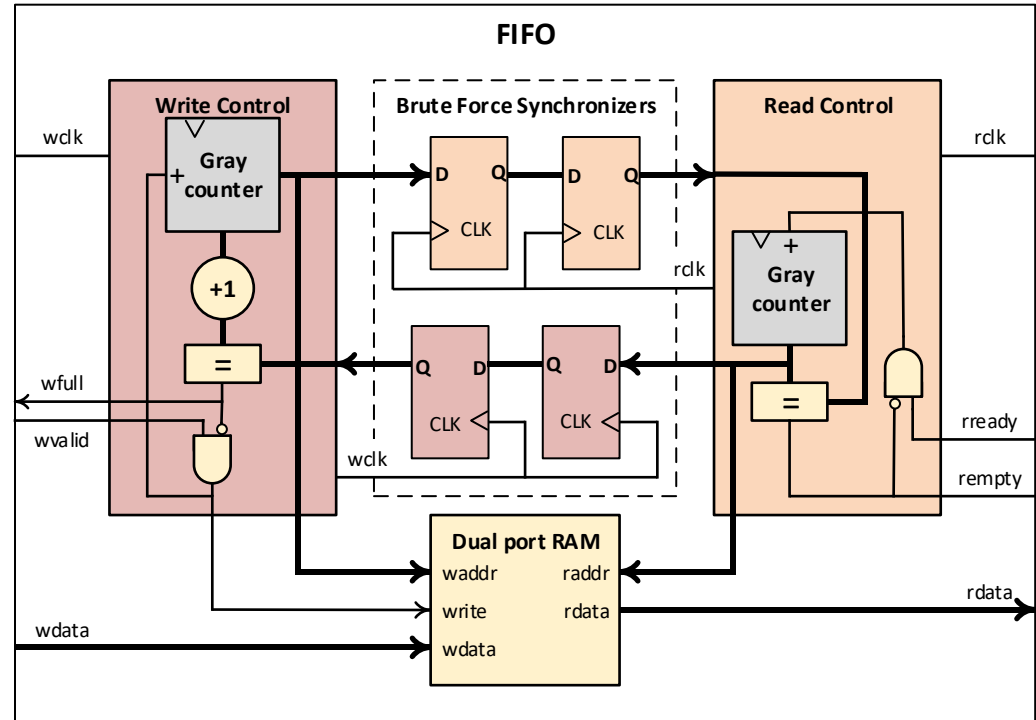
## Unwrapping the FIFO-synchronizer: Read and write control


- Write control
  - Gray counter
    - Counts up on wvalid
      - Except when wfull
    - Write address is count value
  - FIFO is full when write address is one step behind read address
- Read control
  - Gray counter
    - Counts up for every rready
      - Except when empty
    - Read address is count value
  - FIFO is empty when read address is the current write address.
- The gray code sequence must be the same in both counters



## Unwrapping the FIFO-synchronizer: Gray code / Gray counters

- Gray code changes only one bit at a time
  - Example sequences:
    - 00-01-11-10
    - 000-001-011-111-110-100
    - 000-001-011-010-110-111-101-100
  - the «n-bit problem» of synchronization is not an issue
- Gray code *can* be used for fault detection
  - Check if more than one bit is flipped.
    - *This is not needed* in a FIFO
      - we can only have metastability in the last bit being flipped (assuming all FFs are made with the same technology)
      - The read count will never be worse than one behind actual count.
  - Ex. Usage: Discovering errors in rotary encoders (Gray/ Quadrature)
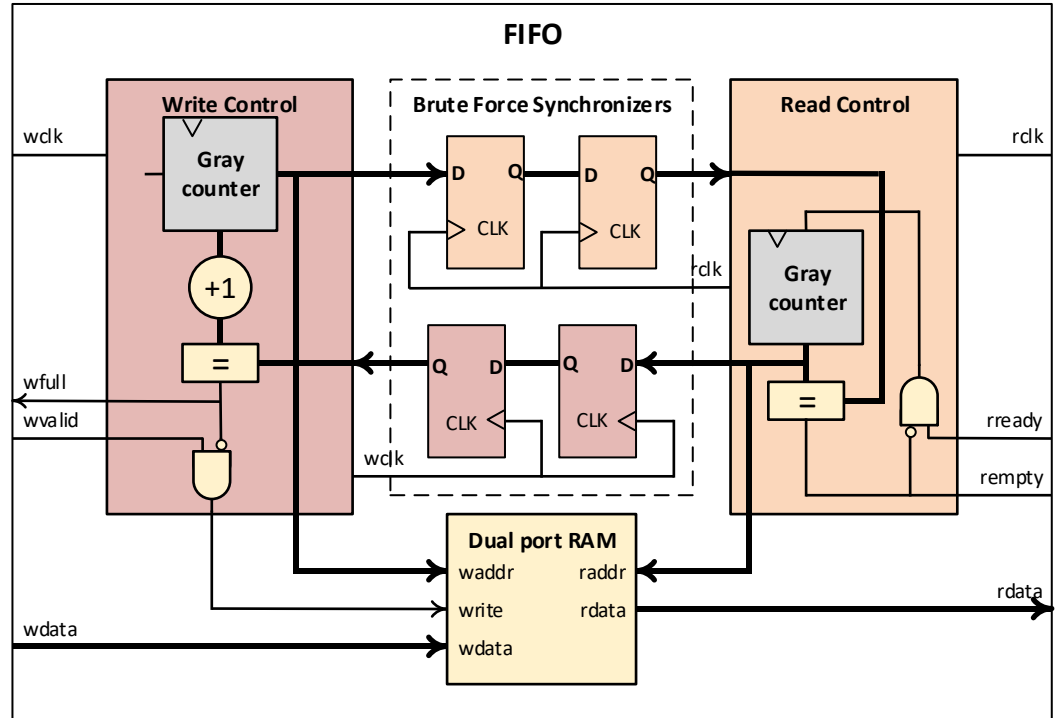
# FIFO that blocks writing and reading when full/empty




# Keeping track of large designs

- Problems that may arise when
  - Using combinational logic... (Hazards)
    - ...before storing asynchronous input in flipflops
    - ...driving output signals
  - Using two external signals in a module
    - Convergence in clock domain crossing (CDC) path
  - Using the same external signal in multiple modules (N-bit problem)
    - Divergence in clock domain crossing path


 
# Convergence in CDC path problem (=Hazards)




Convergent logic in the source domain may cause glitch to be passed to the destination clock domain.

Though both flip-flops of the source clock domain (CLK1) may sample the output signals at the same moment, the incorrect signal may be transferred to the destination clock domain (CLK2) because the propagation delay of the comb\_logic1 may differ from the delay of the comb\_logic2.

Thus, it is impossible to ensure that glitch is not propagated to the destination clock domain.


This may be obscured by multiple layers - if we allow CL in structural modules
 
# Convergence in CDC path solution: Always store output values using FFs



To avoid such problems the convergent output data from the combinational logic should always be registered in the source domain first.

 
# Convergence with synchronized signals problem = The N-bit signal problem



When two signals are synchronized independently and then come to the same combinational logic in the destination domain, functional errors may occur.


Both Q1 and Q2 signals from the CLK1 source domain are synchronized in the CLK2 domain. However, after the synchronization these signals converge on combinational logic. Due to different meta-stable settling times data coherence can be lost and incorrect combination of the Q1 and Q2 values can reach the combinational logic leading to functional errors.

## Convergence in CDC path solution

 

If reconvergence is detected the design should be reviewed to fix the dangerous CDC transfer. One of possible decision is to move combinational logic into source clock domain and then pass the resulting signal to the destination domain.
 
# Divergence in CDC path => N bit problem



Here the output signal Q from the source clock domain (CLK1) is used to activate the comb\_logic1 and the comb\_logic2 in the destination clock domain (CLK2). For proper clock domain crossing it is fanned-out through two synchronizers each of which is connected to the corresponding destination domain logic.

**However, because of the propagation delay and different meta-stable settling times, the output signals from the synchronizers may reach the corresponding destination logics at different times, and in turn these logics will also start at different times leading to functional errors.**

In order to avoid such situations the output signal from the source clock domain should be synchronized at first (double flopping) and then fanned-out to the corresponding destination logics.

## Suggested reading

- D&H
  - 15.2 p 331
  - 28.1- 28.3 p580-585
  - 29 p 592-605